

Enrollment No.....



Faculty of Engineering  
End Sem (Even) Examination May-2022  
EN3ES17 Basic Electrical Engineering

Programme: B.Tech.

Branch/Specialisation: All

**Duration: 3 Hrs.****Maximum Marks: 60**

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.


- Q.1 i. A closed path made by several branches of the network is known as- **1**  
(a) Branch (b) Loop (c) Circuit (d) Node
- ii. While Thevenizing a circuit between two terminals,  $V_{th}$  is equal to- **1**  
(a) Short-circuit terminal voltage  
(b) Net voltage available in the circuit  
(c) Open-circuit terminal voltage  
(d) E.M.F. of the battery nearest to the terminals
- iii. In a pure inductive circuit- **1**  
(a) The current is in phase with the voltage  
(b) The current lags behind the voltage by  $90^\circ$   
(c) The current leads the voltage by  $90^\circ$   
(d) The current can lead or lag by  $90^\circ$
- iv. The term "RMS" stands for\_\_\_\_. **1**  
(a) Root-Mean-Square (b) Read Only Memory  
(c) Random Machine System (d) None of these
- v. The brushes of electrical machines are made of- **1**  
(a) Copper (b) Cast iron (c) Carbon (d) Steel
- vi. The transformer ratings are expressed in terms of- **1**  
(a) kW (Kilowatt)  
(b) Volts  
(c) kVAR (Kilo-Volt-Ampere-Reactive)  
(d) kVA (Kilo-Volt-Ampere)
- vii. What are the Main Parts of SMPS? **1**  
(a) AC Output (b) High efficiency  
(c) Increase back up time (d) Multi-tasking

P.T.O.

[2]

- viii. The primary function of a fuse is to- **1**  
 (a) Open the circuit  
 (b) Protect the appliance  
 (c) Prevent excessive currents from flow through the circuit  
 (d) Protect the line
- ix. What are the applications of dielectric heating? **1**  
 (a) Preheating of Plastic Upgrades (b) Wood Gluing  
 (c) Baking of Foundry Cores (d) All of these
- x. Hydro power plants generate electricity using- **1**  
 (a) Chemical energy (b) Mechanical energy  
 (c) Nuclear energy (d) None of these

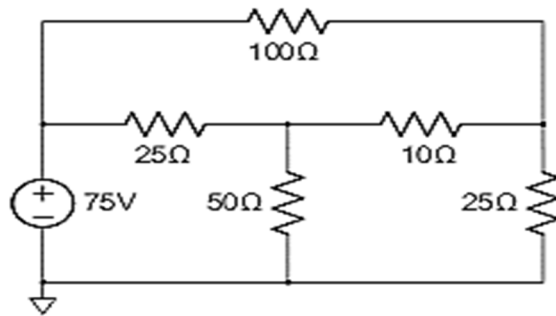- Q.2 i. Define ideal and practical voltage and current source. **2**  
 ii. State and explain the Kirchhoff's laws. **3**  
 iii. Determine current in 50-ohm resistor by using nodal analysis in the circuit shown in figure below. **5**



- OR iv. Obtain equivalents Star from Delta in Star-Delta transformation. **5**

- Q.3 i. Explain the True power, Reactive power and Apparent power. **2**  
 ii. A coil having a resistance of 30 Ω and inductance of 0.05 H is connected in series with a capacitor of 100 μF. The whole circuit has been connected to a single phase 230 V, 50 Hz supply. Calculate impedance, current, power factor, power and apparent power of the circuit. **8**
- OR iii. Derive the expression for resonant frequency & quality factor for an AC circuit under the condition of series resonance. **8**

- Q.4 i. Write application of Single-Phase Induction Motor. **3**

[3]

- ii. Explain the principle of operation of a single-phase transformer. **7**  
 Develop EMF equation for a single-phase transformer.
- OR iii. List all the important parts of a D. C. Motor and explain the importance of each one. **7**
- Q.5 i. What are the main parts of SMPS? **4**  
 ii. Explain different types of wires and cables. **6**
- OR iii. Explain the following: **6**  
 (a) Need of Earthing (b) MCB
- Q.6 Attempt any two:  
 i. Briefly describe the main parts and the working of a thermal power **5**  
 plant.  
 ii. Draw the single line diagram of a power system network showing **5**  
 various voltage levels.  
 iii. What is electric heating? Also write its advantages. **5**

\*\*\*\*\*

**Marking Scheme**  
**EN3ES17 Basic Electrical Engineering**

Q.1	i.	A closed path made by several branches of the network is known as-	1
		(b) Loop	
	ii.	While Thevenizing a circuit between two terminals, $V_{th}$ is equal to-	1
		(c) Open-circuit terminal voltage	
	iii.	In a pure inductive circuit-	1
		(b) The current lags behind the voltage by $90^\circ$	
	iv.	The term "RMS" stands for_____.	1
		(a) Root-Mean-Square	
	v.	The brushes of electrical machines are made of-	1
		(c) Carbon	
	vi.	The transformer ratings are expressed in terms of-	1
		(d) kVA (Kilo-Volt-Ampere)	
	vii.	What are the Main Parts of SMPS?	1
		(a) AC Output                      (b) High efficiency	
		(c) Increase back up time      (d) Multi-tasking	
	viii.	The primary function of a fuse is to-	1
		(c) Prevent excessive currents from flow through the circuit	
	ix.	What are the applications of dielectric heating?	1
		(d) All of these	
	x.	Hydro power plants generate electricity using-	1
		(d) None of these	
Q.2	i.	Define ideal and practical voltage	2
		Current source	
	ii.	State and explain the Kirchhoff's laws.	3
		KCL	
		KVL	
	iii.	Nodal analysis	5
		Current in 50-ohm resistor	
OR	iv.	Obtain equivalents Star from Delta in Star-Delta transformation.	5
		As per the explanation	
Q.3	i.	True power, Reactive power and Apparent power.	2

	ii.	Calculate impedance	2 marks	8
		Current	2 marks	
		Power factor	2 marks	
		Power	1 mark	
		Apparent power of the circuit	1 mark	
OR	iii.	Derivation for resonant frequency	5 marks	8
		Quality factor for an AC circuit	3 marks	
Q.4	i.	Application of Single-Phase Induction Motor		3
		1 mark for each application	(1 mark * 3)	
	ii.	Principle of operation of a single-phase transformer	3 marks	7
		EMF equation for a single-phase transformer	4 marks	
OR	iii.	Construction and parts of a D. C. Motor	2 marks	7
		Explanation of each	5 marks	
Q.5	i.	Main parts of SMPS and explanation		4
	ii.	Types of wires	3 marks	6
		Types of cables	3 marks	
OR	iii.	(a) Need of Earthing	3 marks	6
		(b) MCB	3 marks	
Q.6		Attempt any two:		
	i.	Main parts of a thermal power plant	2 marks	5
		Working of a thermal power plant	3 marks	
	ii.	Single line diagram of a power system network		5
		As per the explanation		
	iii.	Electric heating	2 marks	5
		Its advantages	3 marks	

\*\*\*\*\*