

Enrollment No.....



Faculty of Engineering / Science

End Sem Examination May-2024

EN3ES17 / BC3ES01 Basic Electrical Engineering

Programme: B.Tech./ B.Sc.

Branch/Specialisation: All

**Duration: 3 Hrs.****Maximum Marks: 60**


Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d. Assume suitable data if necessary. Notations and symbols have their usual meaning.

- Q.1 i. The internal resistance of an ideal current source is- **1**  
 (a) Infinite (b) Zero (c)  $10\ \Omega$  (d)  $100\ \Omega$
- ii. Which of the following is not a passive element? **1**  
 (a) Inductor (b) Voltage source (c) Capacitor (d) Resistance
- iii. The power factor at resonance condition in a RLC series circuit is- **1**  
 (a) Zero (b) 0.8 lagging (c) 0.8 leading (d) Unity
- iv. The active power consumed in a pure capacitive AC circuit is- **1**  
 (a) Zero (b) Infinity (c) 100 Watts (d) 1000 Watts
- v. The working principle of a transformer is based on- **1**  
 (a) Self induction (b) Mutual induction  
 (c) Ampere law (d) Coulomb law
- vi. Which part will surely tell that given motor is DC motor and not an AC type? **1**  
 (a) Winding (b) Shaft (c) Commutator (d) Stator
- vii. Fuse wire should possess- **1**  
 (a) High resistance high melting point  
 (b) High resistance low melting point  
 (c) Low resistance low melting point  
 (d) Low resistance high melting point
- viii. Which of the following is a common electric hazard that can result from faulty wiring or electrical equipment? **1**  
 (a) Electromagnetic radiation  
 (b) Electric shock  
 (c) Radioactive contamination  
 (d) Thermal resistance


[2]

- ix. Penstock is a part of which type of power generating plant- **1**  
 (a) Hydroelectric power plant (b) Thermal power plants  
 (c) Nuclear power plant (d) All of these
- x. Which currents are used for inducing heat in the high frequency induction furnace? **1**  
 (a) Alternating primary currents (b) Direct primary currents  
 (c) Alternating secondary currents (d) Direct secondary currents

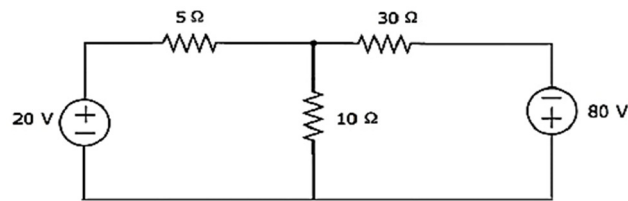- Q.2 i. Explain in brief about active and passive elements. **2**  
 ii. Explain Norton's theorem with the help of an example. Draw the Norton's equivalent circuit. **3**  
 iii. Define Ohms law. Calculate the current through  $10\ \Omega$  resistor using mesh analysis- **5**



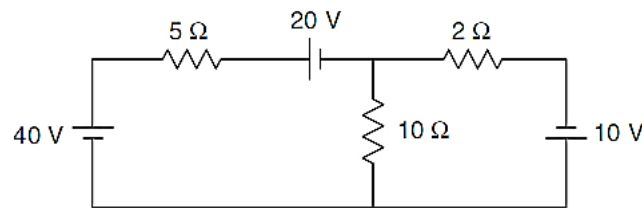- OR iv. Give the statement of Thevenin's theorem. Find the current through the  $2\ \Omega$  resistor using Thevenin's theorem. **5**



- Q.3 i. Draw the power triangle and define its each branch with units and formula. **3**  
 ii. Define for AC circuits with suitable diagram and formulas: **7**  
 (a) Frequency (b) Time period  
 (c) RMS value of voltage (d) Average value of voltage  
 (e) Q factor (f) Active power  
 (g) Power factor.
- OR iii. A resistance of  $20\ \Omega$ , inductance of  $0.2\ \text{H}$  and capacitance of  $100\ \mu\text{F}$  are connected in series across  $220\ \text{V}$ ,  $50\ \text{Hz}$  supply. Determine the following: **7**  
 (a) Impedance (b) Current

[3]

- (c) Power factor angle (d) Power factor  
 (e) Voltage across R, L & C.
- Q.4 i. Write the working principle of a single-phase transformer with suitable diagram. **3**  
 ii. Explain the working principle of three phase induction motor with suitable diagram. What are various types of three phase induction motor? **7**
- OR iii. Explain why single-phase induction motor is not self-starting. List two starting method of single-phase induction motor in detail. **7**
- Q.5 i. Explain different electric hazards. Describe different ways to prevent them. **4**  
 ii. Explain the working of switch mode power supply (SMPS) with the help of block diagram. **6**
- OR iii. Explain the roles of Fuse and Miniature Circuit Breaker (MCB) in electrical protection with suitable diagrams. **6**
- Q.6 Attempt any two: **5**  
 i. Explain electric power generation to distribution through overhead lines with single line diagram in detail. **5**  
 ii. Explain the principle of dielectric heating and write down its two applications. **5**  
 iii. Draw a neat schematic diagram of welding transformer and explain its working. **5**

\*\*\*\*\*

# Marking Scheme

## BC3ES01/EN3ES17 (T) Basic Electrical Engineering

Q.1	i)	A	1
	ii)	B	1
	iii)	D	1
	iv)	A	1
	v)	B	1
	vi)	C	1
	vii)	B	1
	viii)	B	1
	ix)	A	1
	x)	C	1
Q.2	i.	Active, passive elements.	1, 1
	ii.	Give the statement of Norton's theorem, Circuit diagram, An example.	1 1, 1
	iii.	Define Ohms Law. Two Equations, solution, current through 10 $\Omega$ resistor	1, 2,1,1
OR	iv.	Give the statement of Thevenin's theorem. Rth, Vth, current through the 2 $\Omega$ resistor	2 1,1,1
Q.3	i.	Power triangle diagram, define its each branch with, formula.	1,1,1
	ii.	Define for AC circuits with suitable diagram and formulas: (a) Frequency, (b) Time period, (c) RMS value of voltage, (d) Average value of voltage, (e) Q factor, (f) Active power, (g) Power factor.	1 each (1x7)
OR	iii.	A resistance of 20 $\Omega$ , inductance of 0.2H and capacitance of 100 $\mu$ F are connected in series across 220V, 50Hz supply. Determine the following: (a) Impedance, (b) Current, (c) Power factor angle, (d) Power factor, (e) Voltage across R, L & C.	1 each (1x7)
Q.4	i.	Working principle of a single phase transformer, diagram.	2,1
	ii.	Working principle of three phase induction motor, diagram. Also, write three phase induction motor types.	2,2 3
OR	iii.	Explain why single phase induction motor is not self-starting. List two starting method of single phase induction motor in detail.	2 2.5x2

Q.5	i.	Different electric hazards, different ways to prevent them.	2,2
	ii.	Working of switch mode power supply (SMPS), block diagram.	3,3
OR	iii.	Fuse with diagram and Miniature Circuit Breaker with diagram	3x2
Q.6		Attempt any two:	
	i.	Explanation of power generation & distribution, single line diagram.	3, 2
	ii.	Principle of dielectric heating, diagram, its two applications.	2,1, 2
	iii.	Explanation of welding transformer, diagram.	3,2


\*\*\*\*\*

B.E.E

subject code - EN3ES17

solution

Q. 2 (iii)

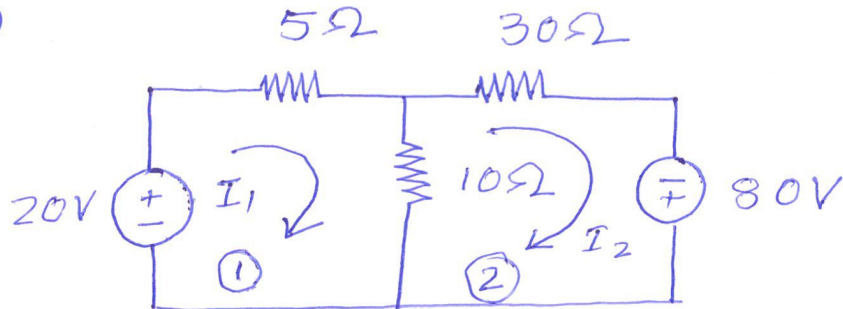

Applying KVL in Loop - I

$$20 - 5I_1 - (I_1 - I_2)10 = 0$$

$$\Rightarrow 20 - 5I_1 - 10I_1 + 10I_2 = 0$$

$$\Rightarrow 20 - 15I_1 + 10I_2 = 0$$

$$\Rightarrow \boxed{-15I_1 + 10I_2 = -20} \quad \text{--- (1)}$$

Applying KVL in Loop - II

$$80 - (I_2 - I_1)10 - 30I_2 = 0$$

$$\Rightarrow 80 - 10I_2 + 10I_1 - 30I_2 = 0$$

$$\Rightarrow \boxed{10I_1 - 40I_2 = -80} \quad \text{--- (2)}$$

from eqn (1) & (2)

$$-3I_1 + 2I_2 = -4$$

$$(-3 \times I_1 - 4I_2 = -8)$$

$$\begin{array}{r} -3I_1 + 2I_2 = -4 \\ -3I_1 + 12I_2 = 24 \\ + \end{array}$$

$$-10I_2 = -28$$

$$\Rightarrow I_2 = \boxed{2.8 \text{ A}}$$

$$\text{so } -3I_1 + 2 \times 2.8 = -4 \Rightarrow -3I_1 = -9.6$$


$$\Rightarrow I_1 = 9.6/3 = \boxed{3.2 \text{ A}}$$

Hence current through  $10\Omega$  resistor is


$$I_1 - I_2 = 3.2 - 2.8 = 0.4 \text{ A}$$

OR


(iv)

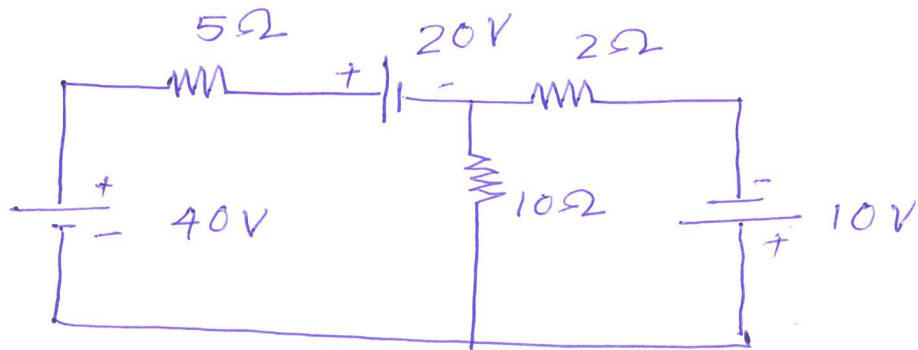

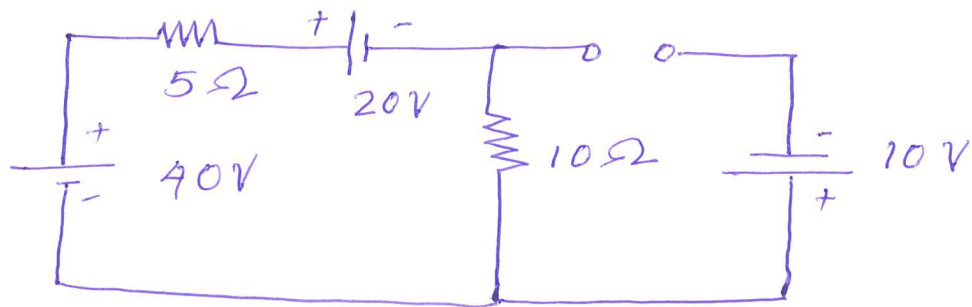\* Load Resistance  $R_L = 2\Omega$   
step-1 open Load




step-2 calculation of  $R_{TH}$

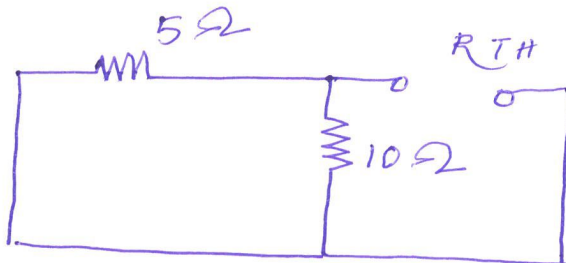

$$R_{TH} = 10\Omega \parallel 5\Omega = \frac{10 \times 5}{10 + 5} = \frac{50}{15} = 3.33\Omega$$

step-3 calculation of  $V_{TH}$

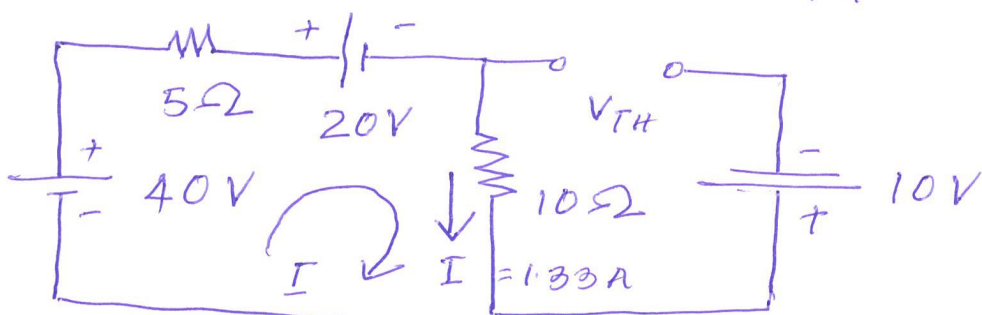

Applying KVL to the close Loop



$$40 - 5I - 20 - 10I = 0$$

$$\Rightarrow 20 - 15I = 0 \Rightarrow I = \frac{20}{15} = 1.33 \text{ A}$$

Applying KVL to  $V_{TH}$  Loop

$$V_{TH} - 10 \times 1.33 - 10 = 0$$

$$\Rightarrow V_{TH} - 13.3 - 10 = 0$$

$$\Rightarrow V_{TH} = \boxed{23.3 \text{ V}} \quad \checkmark$$

step-4 calculation of Load current


$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

$$= \frac{23.3}{3.33 + 2} = \boxed{4.371 \text{ A}} \quad \checkmark$$

Q.3 (iii)

$$R = 20 \Omega, L = 0.2 \text{ H}, C = 100 \mu\text{F} = 100 \times 10^{-6} \text{ F}$$

$$V = 220 \text{ V}, f = 50 \text{ Hz}$$

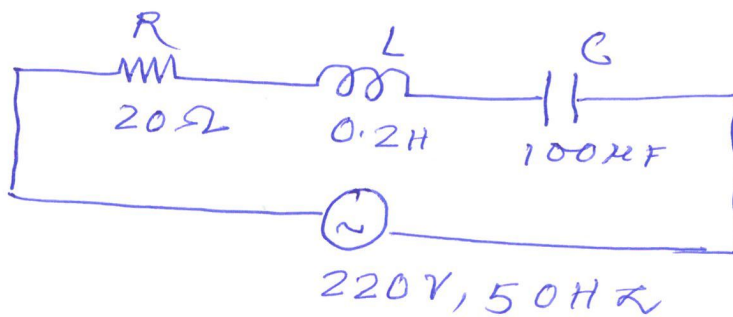

(a)

$$X_L = \omega L = 2\pi f L = 2\pi \times 50 \times 0.2 \Omega$$

$$= \boxed{62.831 \Omega}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}} \Omega$$

$$= \boxed{31.83 \Omega}$$

$$\text{Impedance } Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{(20)^2 + (62.831 - 31.83)^2}$$

$$= \sqrt{1361} = \boxed{36.891 \Omega} \quad \checkmark$$

(b) current  $I = \frac{V}{Z} = \frac{220}{36.891} = \boxed{5.963 \text{ A}} \quad \checkmark$

(c)  $\cos \phi = \frac{R}{Z} \Rightarrow \phi = \cos^{-1}(R/Z)$   
 $\Rightarrow \text{p.f. angle } \phi = \cos^{-1}\left(\frac{20}{36.891}\right) = \boxed{57.17^\circ \text{ (Lag)}} \quad \checkmark$

(d) p.f.  $\cos \phi = \frac{R}{Z} = \frac{20}{36.891} = \boxed{0.542 \text{ (Lag)}} \quad \checkmark$

(e)  $V_R = IR = 5.963 \times 20 = \boxed{119.26 \text{ V}} \quad \checkmark$

$$V_L = I X_L = 5.963 \times 62.831 = \boxed{374.66 \text{ V}} \quad \checkmark$$

$$V_C = I X_C = 5.963 \times 31.83 = \boxed{189.8 \text{ V}} \quad \checkmark$$

— 0 —