

Enrollment No.....



Faculty of Engineering  
End Sem (Even) Examination May-2022  
EN3ES12 Principle of Electronics  
Programme: B.Tech. Branch/Specialisation: CSBS

**Duration: 3 Hrs.****Maximum Marks: 60**

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.

- Q.1 i. N-type silicon is obtained by doping silicon with- **1**  
 (a) Germanium (b) Aluminum  
 (c) Boron (d) Phosphorus
- ii. If the fermi level lies midway between the conduction band and valence band, then the semiconductor is- **1**  
 (a) Intrinsic (b) Extrinsic (c) N-Type (d) P-Type
- iii. When diode is reverse bias, a small current develops which is known as- **1**  
 (a) Forward current (b) Diffusion current  
 (c) Reverse saturation current (d) Active current
- iv. In a full wave rectifier input frequency is 50Hz, then what will be the ripple frequency? **1**  
 (a) 100 Hz (b) 50 Hz (c) 25 Hz (d) 500 Hz
- v. In which following mode BJT works as an amplifier- **1**  
 (a) Cut-off mode (b) Active Mode  
 (c) Saturation Mode (d) Reserve Active Mode
- vi. The alpha  $\alpha$  and beta  $\beta$  of a transistor are related to each other as- **1**  
 (a)  $\alpha = \frac{1+\beta}{\beta}$  (b)  $\beta = \frac{\alpha}{\alpha+1}$  (c)  $\beta = \frac{1+\alpha}{\alpha}$  (d)  $\alpha = \frac{\beta}{\beta+1}$
- vii. MOSFET can be used as- **1**  
 (a) Current controlled capacitor (b) Voltage controlled capacitor  
 (c) Current controlled inductor (d) Voltage controlled inductor

P.T.O.

[2]

- viii. Which one is the types of MOSFET devices available? **1**  
 (a) P-type enhancement type MOSFET  
 (b) N-type enhancement type MOSFET  
 (c) Depletion type MOSFET  
 (d) All of these
- ix. Which of the following electrical characteristics is not exhibited by an ideal op-amp? **1**  
 (a) Infinite voltage gain (b) Infinite bandwidth  
 (c) Infinite output resistance (d) Infinite slew rate
- x. What is Barkhausen criterion for oscillation? **1**  
 A-> gain of amplifier and  $\beta$ -> transfer ratio.  
 (a)  $A\beta > 1$  (b)  $A\beta < 1$  (c)  $A\beta = 1$  (d)  $A\beta \neq 1$
- Q.2 i. Write difference between drift and diffusion current in semiconductor device. **2**  
 ii. What are intrinsic and extrinsic semiconductors give examples? **3**  
 iii. What is energy band? Differentiate conductor, insulator, and semiconductor on the basis of energy band diagram. **5**
- OR iv. Explain how p-type and N-type semiconductors are formed. **5**
- Q.3 i. What is the difference between the Zener breakdown and avalanche breakdown? **2**  
 ii. Compare the full wave bridge rectifier, centre tap rectifier, and half wave rectifier based on different parameters and circuit diagram? **8**
- OR iii. Explain light emitting diode, Zener diode, varactor diode, photo diode based on following point: **8**  
 (a) Working of Diode (b) V-I characteristic of diode  
 (c) Application of Diode
- Q.4 i. Draw and Explain how BJT works as an amplifier. **3**  
 ii. What is BJT? Describe the formation depletion layer of NPN transistor with the suitable diagram. **7**
- OR iii. Compare the CB, CC, CE configuration of BJT based on different parameters and circuit diagram. **7**

[3]

- Q.5 i. Write difference between BJT and FET. **4**  
 ii. Draw and explain the construction and working of a JFET with input output Characteristic. **6**
- OR iii. What is CMOS? Draw inverter using the CMOS. **6**
- Q.6 Attempt any two:  
 i. What is operational amplifier? Write down all the characteristic of ideal OPAMP in detail. **5**  
 ii. How is an integrator made using op-amp? Write its equations. **5**  
 iii. (a) Write down difference between the analog and digital signals. **5**  
 (b) What is Flip-Flop?

\*\*\*\*\*

**Marking Scheme**  
**EN3ES12 Principle of Electronics**

Q.1	i.	N-type silicon is obtained by doping silicon with- (d) Phosphorus	<b>1</b>
	ii.	If the fermi level lies midway between the conduction band and valence band, then the semiconductor is- (a) Intrinsic	<b>1</b>
	iii.	When diode is reverse bias, a small current develops which is known as- (c) Reverse saturation current	<b>1</b>
	iv.	In a full wave rectifier input frequency is 50Hz, then what will be the ripple frequency? (a) 100 Hz	<b>1</b>
	v.	In which following mode BJT works as an amplifier- (b) Active Mode	<b>1</b>
	vi.	The alpha $\alpha$ and beta $\beta$ of a transistor are related to each other as- (d) $\alpha = \frac{\beta}{\beta+1}$	<b>1</b>
	vii.	MOSFET can be used as- (b) Voltage controlled capacitor	<b>1</b>
	viii.	Which one is the types of MOSFET devices available? (d) All of these	<b>1</b>
	ix.	Which of the following electrical characteristics is not exhibited by an ideal op-amp? (c) Infinite output resistance	<b>1</b>
	x.	What is Barkhausen criterion for oscillation? A-> gain of amplifier and $\beta$ -> transfer ratio. (c) $A\beta = 1$	<b>1</b>

Q.2	i.	Differences	2 marks	<b>2</b>
	ii.	Definition Example	2 marks 1 mark	<b>3</b>
	iii.	Definition of energy band Diagram	2 marks 1 mark each	<b>5</b>
	OR iv.	Explanation	3 marks	<b>5</b>

		Diagram	2 marks	
Q.3	i.	Differences	2 marks	<b>2</b>
	ii.	Comparison on each parameter	2 marks each	<b>8</b>
	OR iii.	Explanation of each diode	2 marks each	<b>8</b>
Q.4	i.	Explanation Diagram	2 marks 1 mark	<b>3</b>
	ii.	Definition Diagram	2 marks 2 marks	<b>7</b>
		Explanation	3 marks	
	OR iii.	Explanation Circuit diagrams	4 marks 1 mark each	<b>7</b>
	Q.5 i.	Any four differences	(1 mark * 4)	<b>4</b>
	ii.	Structure Working Characteristic	2 marks 2 marks 2 marks	<b>6</b>
OR	iii.	Definition Inverter	2 marks 4 marks	<b>6</b>
	Q.6	Attempt any two:		
	i.	Definition Diagram Characteristic	1 mark 1 mark 3 marks	<b>5</b>
	ii.	Explanation and Diagram Equations	3 marks 2 marks	<b>5</b>
	iii.	(a) Difference (b) Flip-Flop	2.5 marks 2.5 marks	<b>5</b>

\*\*\*\*\*