

Enrollment No.....



Faculty of Engineering
End Sem (Odd) Examination Dec-2019
EN3ES11 Principles of Electrical Engineering

Programme: B.Tech.

Branch/Specialisation: CSBS

Duration: 3 Hrs.**Maximum Marks: 60**

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.


- | | | | |
|-----|-------|---|---|
| Q.1 | i. | An Electric Current is_____ | 1 |
| | | (a) Flow of Electrons (b) Opposition of Electrons | |
| | | (c) Storage of charge (d) Ionization of atom | |
| | ii. | Which one is the correct expression for ohm's Law. | 1 |
| | | (a) $V = IR$ (b) $I = V^2R$ (c) $V = I^2R$ (d) $R = I^2V$ | |
| | iii. | Which among the following is also regarded as 'Dual of Thevenin's Theorem'? | 1 |
| | | (a) Norton's Theorem | |
| | | (b) Superposition Theorem | |
| | | (c) Millman's Theorem | |
| | | (d) Maximum Power Transfer Theorem | |
| | iv. | In a DC Circuit, Inductive reactance would be_____ | 1 |
| | | (a) Equal as in AC Circuits (b) High | |
| | | (c) Extremely High (d) Zero | |
| | v. | Power factor is _____ | 1 |
| | | (a) $\sin \phi$ (b) $\cos \phi$ (c) $\tan \phi$ (d) None of these | |
| | vi. | The unit of electrical energy is / are | 1 |
| | | (a) Joules (b) Watt - sec | |
| | | (c) Kilowatt - hour (d) All of these | |
| | vii. | Constant loss of transformer is: | 1 |
| | | (a) Iron loss (b) Copper Loss | |
| | | (c) Heat loss (d) None of these | |
| | viii. | What does a capacitor store? | 1 |
| | | (a) Current (b) Voltage (c) Power (d) Charge | |

P.T.O.

[2]


- ix. Shunt Capacitor is used in _____ 1
 (a) Long transmission line (b) Short transmission line
 (c) Medium transmission line (d) All of these
- x. Reactive coil used in the transmission line to protect the _____ 1
 (a) Current (b) Voltage (c) Power (d) Charge

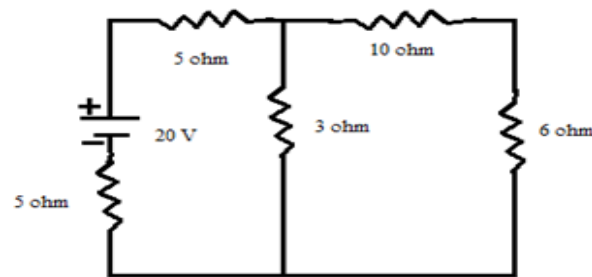- Q.2 i. What are types of sources? 2
 ii. Explain ohm's Law? 3
 iii. Calculate equivalent resistance in the given circuit? Also calculate current in 3 ohm resistance. 5



- OR iv. Explain Kirchhoff's Law with suitable example. 5

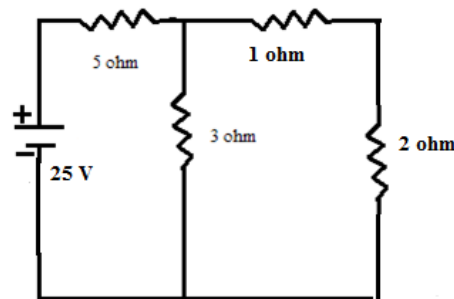- Q.3 i. Explain the maximum power transfer theorem. 2
 ii. Calculate the load current by Thevenin's network when R_L is 2 ohms? 8




- OR iii. Explain the procedure of superposition theorem with a suitable example. 8

- Q.4 i. Explain form factor and peak factor? 3

[3]

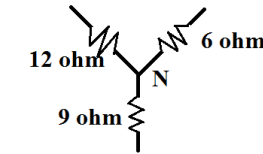- ii. Convert it into Delta Connection? 7



- OR iii. Explain RLC series circuits with Phasor diagram? 7

- Q.5 i. Explain Faraday's law? 4

- ii. Derive the EMF equation of transformer. 6

- OR iii. Explain transformer with its applications and working principle. 6

- Q.6 Attempt any two: 5

- i. What is distribution system? Enlist various layout of distribution system. 5

- ii. What is earthing? Explain its types? Why it is used? 5

- iii. Explain the safety devices used in the transmission line. 5

Marking Scheme
EN3ES11 Principles of Electrical Engineering

Q.1	i.	An Electric Current is_____	1
		(a) Flow of Electrons	
	ii.	Which one is the correct expression for ohm's Law?	1
		(a) $V = IR$	
	iii.	Which among the following is also regarded as 'Dual of Thevenin's Theorem'?	1
		(a) Norton's Theorem	
	iv.	In a DC Circuit, Inductive reactance would be_____	1
		(d) Zero	
	v.	Power factor is _____	1
		(b) $\cos \phi$	
	vi.	The unit of electrical energy is / are	1
		(d) All of these	
	vii.	Constant loss of transformer is:	1
		(a) Iron loss	
	viii.	What does a capacitor store?	1
		(d) Charge	
	ix.	Shunt Capacitor is used in	1
		(d) All of these	
	x.	Reactive coil used in the transmission line to protect the _____	1
		(a) Current	

Q.2	i.	Types of sources	2
	ii.	Explanation of ohm's Law	3
	iii.	Calculation of equivalent resistance	5
OR		Calculate current in 3 ohm resistance	2
	iv.	Explain Kirchhoff's Law	5
		Current	2.5
		Voltage	2.5

Q.3	i.	Maximum power transfer theorem	2
	ii.	Calculate the load current by Thevenin's network	8
		R_{th} calculation	3
		V_{th} calculation	3
		Current	2

OR	iii.	Procedure of superposition theorem	4
		Example	4
Q.4	i.	Form factor and peak factor	3
	ii.	Star to Delta	7
OR	iii.	RLC series circuits	2
		Explanation	3
		Phasor diagram	2
Q.5	i.	Faraday's law	4
	ii.	Derivation of EMF equation of transformer.	6
OR	iii.	Transformer explanation	3
		Principle.	3
Q.6		Attempt any two:	
	i.	Distribution system	2
		Layout of distribution system	3
	ii.	Earthing	1
		Its types	2
		Uses	2
	iii.	Safety devices used in the transmission line.	5
