

Enrollment No.....



Faculty of Engineering  
End Sem (Even) Examination May-2022  
EC3CO07 / EE3CO21 / EX3CO21 Digital Electronics  
Programme: B.Tech. Branch/Specialisation: EC/EE/EX

**Duration: 3 Hrs.****Maximum Marks: 60**


Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.

- Q.1 i. The binary equivalent of  $(0.6875)_{10}$  is \_\_\_\_\_. 1  
 (a)  $(0.1011)_2$  (b)  $(0.1101)_2$  (c)  $(0.1110)_2$  (d)  $(0.0111)_2$
- ii. For the given binary numbers  $X=1010100$  and  $Y=1000011$ , the result of  $X-Y$  and  $Y-X$  respectively is- 1  
 (a) 0110001 and 1001110 (b) 1010001 and 0101110  
 (c) 1101110 and 0010001 (d) 0010001 and 1101110
- iii. The simplified minimum literal representations for the Boolean expressions  $x+x'y$  and  $x(x'+y)$  respectively is- 1  
 (a)  $x'y$  and  $x+y'$  (b)  $x+y'$  and  $x'+y$   
 (c)  $x+y$  and  $xy$  (d)  $xy$  and  $x+y$
- iv. For the given Boolean function  $F=A'C+A'B+AB'C+BC$ , the minimal sum of products expression is- 1  
 (a)  $F= A'C+A'B$  (b)  $F= C+A'B$   
 (c)  $F=AB'C+BC$  (d)  $F=A'C+A'B+AB'C$
- v. A basic S-R flip-flop can be constructed by cross-coupling of which basic logic gates. 1  
 (a) AND or OR gates (b) XOR or XNOR gates  
 (c) NOR or NAND gates (d) AND or NOR gates
- vi. What is the maximum possible range of bit-count specifically in n-bit binary counter consisting of 'n' number of flip-flops? 1  
 (a) 0 to  $2^n$  (b) 0 to  $2^n + 1$  (c) 0 to  $2^n - 1$  (d) 0 to  $2^{n+1/2}$
- vii. The 32 x 8 memory would contain \_\_\_\_ words, each \_\_\_\_ bits long, for a total capacity of \_\_\_\_ bits. 1  
 (a) 32, 8, 256 (b) 8, 32, 256  
 (c) 32, 32, 256 (d) 8, 8, 256

P.T.O.

[2]

 - viii. PLA contains \_\_\_\_\_. **1**  
 (a) AND and OR arrays (b) NAND and OR arrays  
 (c) NOT and AND arrays (d) NOR and OR arrays
- ix. TTL devices consume substantially \_\_\_\_\_ power than equivalent CMOS devices at rest. **1**  
 (a) Less (b) More (c) Equal (d) Very High
- x. CMOS behaves as a/an \_\_\_\_\_. **1**  
 (a) Adder (b) Subtractor (c) Inverter (d) Comparator
- Q.2 i. Convert decimal 153 to octal using division method. **2**  
 ii. What is a Boolean function? How it can be represented? Explain by taking an example. **3**  
 iii. Find the complement of the functions  $F_1 = x'yz' + x'y'z$  and  $F_2 = x(y'z' + yz)$  **5**
- OR iv. Express the Boolean function  $F = A + B'C$  in a sum of minterms. **5**
- Q.3 i. What is the Boolean expression for the AND-OR logic diagram? **2**



- ii. Design a combinational circuit that converts BCD to excess-3 code converter by implementing the truth table and logic circuit. **8**
- OR iii. Implement the following function using a Multiplexer: **8**  
 $F(A,B,C,D) = \sum(0,1,3,4,8,9,15)$
- Q.4 i. Enumerate the differences between combinational circuit and sequential circuit with suitable examples. **3**  
 ii. What is a Master-slave flip flop? Draw the logic diagram of a master-slave D flip flop. Use NAND gates. **7**
- OR iii. Design and implement a mod-6 asynchronous counter using T-flip flops **7**

[3]

- Q.5 i. A certain memory has a capacity of 8K x 16. **4**  
 (a) How many data input and data output lines does it have?  
 (b) How many address lines does it have?  
 (c) What is its capacity in bytes?
- ii. Explain ROM with a block diagram. How a ROM is organized? **6**  
 What are the various types of ROMs? Explain in detail.
- OR iii. Write a short note on Programmable Logic Devices with explanation of PLA and PAL. **6**
- Q.6 Attempt any two: **5**  
 i. Give a comparative analysis of logic families TTL, ECL, MOS, CMOS and IIL on the basis of commonly used specific parameters. **5**  
 ii. What are the different techniques of interfacing TTL and CMOS? Explain in detail. **5**  
 iii. With the help of a neat circuit diagram, explain the working of **5**  
 (a) A MOS inverter  
 (b) A two-input MOS NAND gate  
 (c) A two-input MOS NOR gate.

\*\*\*\*\*

## Marking Scheme

### EC3CO07 / EE3CO21 / EX3CO21 Digital Electronics

Q.1	i.	The binary equivalent of $(0.6875)_{10}$ is_____.		1
		(a) $(0.1011)_2$		
	ii.	For the given binary numbers $X=1010100$ and $Y=1000011$ , the result of $X-Y$ and $Y-X$ respectively is-		1
		(d) 0010001 and 1101110		
	iii.	The simplified minimum literal representations for the Boolean expressions $x+x'y$ and $x(x'+y)$ respectively is-		1
		(c) $x+y$ and $xy$		
	iv.	For the given Boolean function $F=A'C+A'B+AB'C+BC$ , the minimal sum of products expression is-		1
		(b) $F= C+A'B$		
	v.	A basic S-R flip-flop can be constructed by cross-coupling of which basic logic gates.		1
		(c) NOR or NAND gates		
Q.2	vi.	What is the maximum possible range of bit-count specifically in n-bit binary counter consisting of 'n' number of flip-flops?		1
		(c) 0 to $2^n - 1$		
	vii.	The 32 x 8 memory would contain _____words, each _____bits long, for a total capacity of _____bits.		1
		(a) 32, 8, 256		
	viii.	PLA contains _____.		1
		(a) AND and OR arrays		
	ix.	TTL devices consume substantially _____ power than equivalent CMOS devices at rest.		1
		(b) More		
	x.	CMOS behaves as a/an _____.		1
		(c) Inverter		
Q.3	i.	Boolean expression for the AND-OR logic diagram		2
	ii.	Design a combinational circuit	2 marks	8
		Implementing the truth table and logic circuit	3 marks	
		Explanation	3 marks	
OR	iii.	Implement function using a Multiplexer:		8
		1 mark for each	(1 mark * 8)	
Q.4	i.	Differences b/w combinational circuit and sequential circuit with examples.		3
		1 mark for each difference	(1 mark * 3)	
	ii.	Definition of Master-slave flip flop	3 marks	7
		Logic diagram of a master-slave D flip flop	4 marks	
OR	iii.	Diagram	3 marks	7
		Implement a mod-6 asynchronous counter using T-flip flops	4 marks	
Q.5	i.	(a) Data input and data output lines	2 marks	4
		(b) Address lines	1 mark	
		(c) Its capacity in bytes	1 mark	
	ii.	Explanation of ROM	2 marks	6
		Block Diagram	2 marks	
		Types of ROMs	2 marks	
OR	iii.	Programmable Logic Devices with explanation of PLA	3 marks	6
		PAL	3 marks	
Q.6		Attempt any two:		
	i.	Comparative analysis of logic families TTL, ECL, MOS, CMOS and IIL on the basis of commonly used specific parameters		5
		1 mark for each parameter	(1 mark * 5)	
	ii.	Techniques of interfacing TTL	2.5 marks	5
		CMOS	2.5 marks	
	iii.	With the help of a neat circuit diagram, explain the working of		5
		(a) A MOS inverter	1 mark	
		(b) A two-input MOS NAND gate	2 marks	
		(c) A two-input MOS NOR gate	2 marks	

\*\*\*\*\*