

Total No. of Questions: 6

Total No. of Printed Pages: 2

Enrollment No.....



Faculty of Engineering / Science
End Sem Examination Dec-2023
CS3CO33 / EC3CO07 / IT3CO26 / BC3CO38
Digital Electronics

Programme: B.Tech. / B.Sc. Branch/Specialisation: CSE All / EC
/ IT / Computer Science

Duration: 3 Hrs.

Maximum Marks: 60

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d. Assume suitable data if necessary. Notations and symbols have their usual meaning.

- Q.1 i. $A+A=A$ defined by- 1
(a) Null law (b) Idempotent law (c) Identity law (d) None of these
- ii. Canonical form is a unique way of representing- 1
(a) SOP (b) POS
(c) Minterm (d) Boolean Expressions
- iii. In two input XNOR, one input is A & another is always ground then output is: 1
(a) 0 (b) 1 (c) A (d) A'
- iv. Which gate is used as comparator? 1
(a) NAND (b) NOR (c) XNOR (d) XOR
- v. The basic latch consists of _____. 1
(a) Two inverters (b) Two comparators
(c) Two amplifiers (d) Two adders
- vi. What is an ambiguous condition in a NAND based S'-R' latch? 1
(a) S'=0, R'=1 (b) S'=1, R'=0
(c) S'=1, R'=1 (d) S'=0, R'=0
- vii. ROM internal structure consist of- 1
(a) NAND and XOR arrays (b) NOR and NAND arrays
(c) Decoder and OR (d) OR and AND arrays
- viii. The full form of PLA is _____. 1
(a) Programmable Large Array (b) Programmable Logic Array
(c) Program Logic array (d) Printed Logical array
- ix. Which type of ROM has to be programmed by the manufacturer? 1
(a) EEPROM (b) EPROM (c) PROM (d) Mask Rom

[2]

- x. Which ROM can be erased by an electrical signal? 1
(a) ROM (b) Mask ROM (c) EPROM (d) EEPROM
- Q.2 i. Determine the value of base x if $(211)_x = (152)_8$. 2
ii. Express the Boolean function $F=XY+X'Z$ in product of maxterm. 3
iii. Express the following function as the minimal sum of products using a K-map. 5
 $F(a,b,c,d) = \sum(0,2,4,5,6,11,13,15) + \sum d(8,10,14)$
- OR iv. Reduce the following using tabulation method. 5
 $F(A,B,C,D) = \sum(3,4,5,7,9,13,14,15)$
- Q.3 i. Implement the Boolean functions using basic logic gates- 2
(a) $ABC' + (A' + B')C$ (b) ABC
ii. Define encoder & decoder. 3
iii. Explain a full subtractor with logic diagram, truth table & Boolean equation. 5
- OR iv. Implement the Boolean function using 8:1 mux. 5
 $F(A, B, C, D) = A'BD' + ACD + B'CD + A'C'D$
- Q.4 i. Convert SR FF to JK FF using suitable diagram. 3
ii. Define shift registers. Describe any two shift register with example. 7
- OR iii. Design a circuit for 3-bit synchronous up counter using T flip-flop. 7
- Q.5 i. Write types of memories. Which memory is called volatile? Why? 4
ii. Compare the PROM, EPROM and EEPROM. 6
- OR iii. Explain dynamic RAM. 6
- Q.6 Attempt any two: 5
i. Explain the two inputs TTL NAND gate using neat circuit diagram. 5
ii. Write a short note on DTL & RTL. 5
iii. Write a short note on CMOS family. 5

P.T.O.