

[4]

OR iii. What is peak detector? Draw its circuit diagram and explain its working with input output wave forms. 6

Q.6 Attempt any two:

- What is switching regulator? List major component of switching regulator and explain there working. 5
- Write short note on SMPS. 5
- What is fixed and adjustable voltage regulator list the advantage of adjustable voltage regulator over fixed voltage regulator. 5

Total No. of Questions: 6

Total No. of Printed Pages:4

Enrollment No.....



Faculty of Engineering
End Sem (Even) Examination May-2022
EC3CO17 Linear Integrated Circuit

Programme: B.Tech.

Branch/Specialisation: EC

Duration: 3 Hrs.


Maximum Marks: 60

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.

Q.1 i. Which of the following electrical characteristics is not exhibited by an ideal op-amp? 1

- Infinite voltage gain
- Infinite bandwidth
- Infinite output resistance
- Infinite slew rate

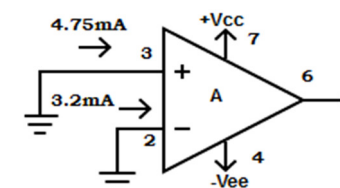ii. Calculate the input offset current from the circuit shown below: 1



- +1.55mA
- $\pm 1.55\text{mA}$
- 1.55mA
- None of these

iii. Define the input resistance with feedback for voltage series feedback amplifier. 1

- $R_{IF} = R(1-AB)$
- $R_{IF} = R(AB-1)$
- $R_{IF} = R(1+AB)$
- None of these

iv. Find out the gain value by which each input of the averaging amplifier is amplified? (Assume there are four inputs) 1

- 0.5
- 0.25
- 1
- 2

v. Match the gain of the filter with the frequencies in the low pass filter. 1


Frequency		Gain of the filter	
A	$f < f_H$	A	$V_O/V_{in} \cong A_F/\sqrt{2}$
B	$f = f_H$	B	$V_O/V_{in} \leq A_F$
C	$f > f_H$	C	$V_O/V_{in} \cong A_F$

- AA, BB, CC
- AB, BC, CA
- AC, BB, CA
- AC, BA, CB

P.T.O.

[2]

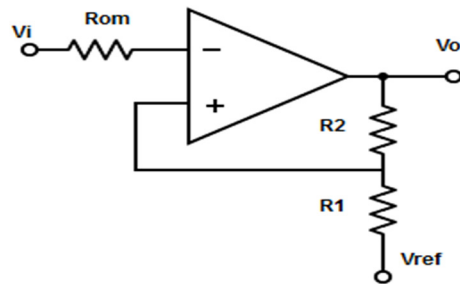- vi. Find the roll-off rate for 8th order Low pass filter- 1
 (a) -160 dB/decade (b) -320 dB/decade
 (c) -480 dB/decade (d) -200 dB/decade
- vii. Determine the time period of a monostable 555 multivibrator. 1
 (a) $T = 0.33RC$ (b) $T = 1.1RC$
 (c) $T = 3RC$ (d) $T = RC$
- viii. Calculate the hysteresis voltage for the schmitt trigger from the given specification: $R_2 = 56 \text{ k}\Omega$, $R_1 = 100 \Omega$, $V_{ref} = 0V$ & $V_{sat} = \pm 14V$. 1



- (a) 0 mV (b) 25 mV
 (c) 50 mV (d) -25 mV
- ix. The 7812 regulator IC provides- 1
 (a) 5 V (b) -5 V (c) 12 V (d) -12 V
- x. Which is not considered as a linear voltage regulator? 1
 (a) Fixed output voltage regulator
 (b) Adjustable output voltage regulator
 (c) Switching regulator
 (d) Special regulator


- Q.2 i. What is Op-Amp? 2
 ii. Design an inverting amplifier with gain of -5 and an input resistance of $10 \text{ k}\Omega$. 3
 iii. Define following electrical parameters of Op-Amp: Input offset voltage, CMRR, Output Voltage Swing, slew rate and SVRR. 5
- OR iv. List and explain the function of all the basic building block of an Op-Amp. 5

- Q.3 i. What is feedback? List two types of feedback. Which type is used in linear application? 2


[3]

- ii. Draw circuit diagram of an integrator, explain its working, drive the expression of output and draw the output waveform for square wave input. 3
- iii. What is instrumentation amplifier? Draw its circuit diagram and drive the expression of output also write its applications. 5
- OR iv. Draw and explain the circuit diagram of phase shift oscillator and design it for output frequency of 200 Hz. 5

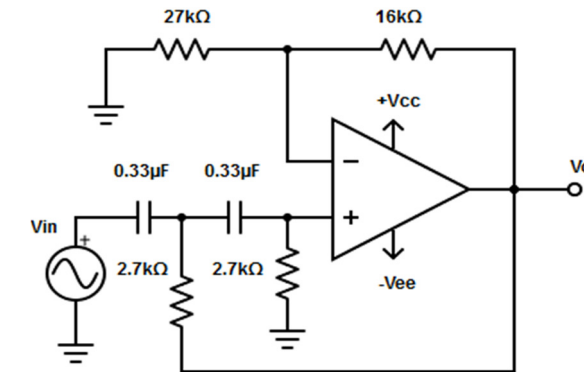- Q.4 i. Define Filter. How are filter classified? 2
 ii. What are the advantages of active filters over passive filters? 3
 iii. Design a first order low pass butterworth filter so that it has a cut off frequency of 1.6 kHz and a pass band gain of 2. 5
- OR iv. Consider the following filter circuit and calculate the low cut-off frequency value 5



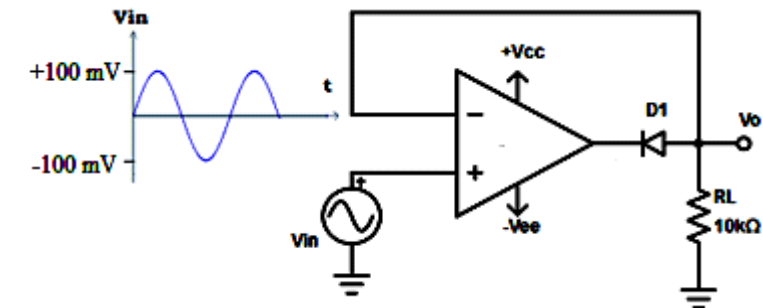- Q.5 i. Draw and explain the functional diagram of a 555 timer. 4
 ii. Identify the circuit given below, explain its working and determine the output waveform for the given sinusoidal input. 6



P.T.O.

Marking Scheme

EC3CO17 Linear Integrated Circuit

Marking Scheme										
EC3CO17 Linear Integrated Circuit										
Q.1	i.	Which of the following electrical characteristics is not exhibited by an ideal op-amp?	1	OR	iii.	Working	0.5 Mark	5		
		(c) Infinite output resistance				Output expression	1 Mark			
	ii.	Calculate the input offset current from the circuit shown below:	1		iv.	Output Waveform	1 Mark			
		(a) +1.55mA				Definition	1 Mark			
	iii.	Define the input resistance with feedback for voltage series feedback amplifier.	1		v.	Circuit diagram	1 Mark			
		(c) $R_{IF} = R(1+AB)$				Expression	2 Mark			
	iv.	Find out the gain value by which each input of the averaging amplifier is amplified? (Assume there are four inputs)	1		vi.	Application	1 Mark			
		(b) 0.25				Circuit diagram	1 Mark			
	v.	Match the gain of the filter with the frequencies in the low pass filter.	1		vii.	Explanation	2 Marks			
		(d) AC, BA, CB				Design	2 Marks			
Q.2	i.	Definition	2 Marks	OR	Q.4	i.	Definition	1 Mark	2	
		Circuit Diagram	1 Marks			ii.	Classification	1 Mark		
	ii.	Calculation of feedback and input resistance	2 Marks		iii.		Each with explanation	1 Mark*3		3
		Each definition	(1 Mark*5)			iv.	Circuit diagram	1 Mark		
	iii.	Block diagram	2 Marks		v.		Parameter for Cut off Frequency	2 Marks		
		Explanation of blocks	3 Marks			vi.	Parameter for Gain	2 Marks		
	iv.	OR	Q.5		i.		PIN Diagram	2 Marks		4
						ii.		Identification of Circuit		
	v.	iii.	Working		3 Mark		6			
					vi.	Out Put Wave form		2 Mark		
vii.	Definition	1 Mark								
		viii.	Circuit Diagram	2 Marks						
ix.	Working			2 Marks						
		x.	Output Wave Form	1 Mark						
				Q.6	Attempt any two:					
Q.3	i.	Definition	1 Marks		OR	i.	Definition	1 Mark	5	
		List type of feedback	0.5 Mark	ii.			List of major component	2 Marks		
	ii.	Which is used for linear application	0.5 Mark			iii.	Working	2 Marks		
		Circuit diagram	0.5 Mark	iv.			Diagram	2 Marks		5
	iii.	OR	Q.7			i.	Explanation	3 Marks		
				ii.			Definition	3 Marks		5
	iii.	Advantage	2 Marks							