

Enrollment No.....



Faculty of Engineering / Science

End Sem Examination May-2023

EN3ES17 / BC3ES01 Basic Electrical Engineering

Programme: B.Tech. / B.Sc.

Branch/Specialisation: All

Duration: 3 Hrs.**Maximum Marks: 60**

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d. Assume suitable data if necessary. Notations and symbols have their usual meaning.


- Q.1 i. According to Thevenin's theorem, any bilateral network can be represented by a network with- 1
- (a) An independent current source in parallel to the equivalent resistance
 - (b) An independent voltage source in series to the equivalent resistance
 - (c) An independent voltage source in parallel to the equivalent resistance
 - (d) None of these
- ii. According to Kirchhoff's voltage law- 1
- (a) The algebraic sum of all the e.m.fs in the circuit is zero
 - (b) Algebraic sum of all the voltage drops in the circuit is zero
 - (c) Algebraic sum of all the e.m.fs plus algebraic sum of voltage drops is equal to zero
 - (d) All of these
- iii. The condition of resonance in series R-L-C circuit is- 1
- (a) Resistance (R) = Inductive reactance (X_L)
 - (b) Resistance (R) = Capacitive reactance (X_C)
 - (c) Inductive reactance (X_L) = Capacitive reactance (X_C)
 - (d) None of these
- iv. The angle between voltage and current in a purely resistive A.C circuit is- 1
- (a) 0°
 - (b) 90° (lag)
 - (c) 90° (lead)
 - (d) 180°

P.T.O.

[2]

- v. The function of pole shoe in DC motor is to- **1**
 (a) Produce the necessary magnetic flux
 (b) Spread flux in the air gap
 (c) Support field coils
 (d) Both (b) & (c)
- vi. If the voltage rating of transformer is 230V/110V then the transformer **1**
 is a-
 (a) Step up transformer (b) Step down transformer
 (c) Both (a) and (b) (d) None of these
- vii. The electric energy meter measures energy in the unit- **1**
 (a) KVAH (b) KVARH (c) KWH (d) None of these
- viii. Full form of UPS is- **1**
 (a) Undersized Power Supply (b) Uninterrupted Power Supply
 (c) Uneven Power Supply (d) Unwanted Power Supply
- ix. Which of the following are the components of a thermal power plant? **1**
 (a) Boiler, Turbine, Condenser, Pump
 (b) Boiler, Turbine, Pump, Expansion valve
 (c) Evaporator, Condenser, Boiler, Turbine
 (d) Evaporator, Condenser, Boiler, Expansion valve
- x. Which of the following is an advantage of heating by electricity? **1**
 (a) Quicker operation (b) Higher efficiency
 (c) Absence of flue gases (d) All of these

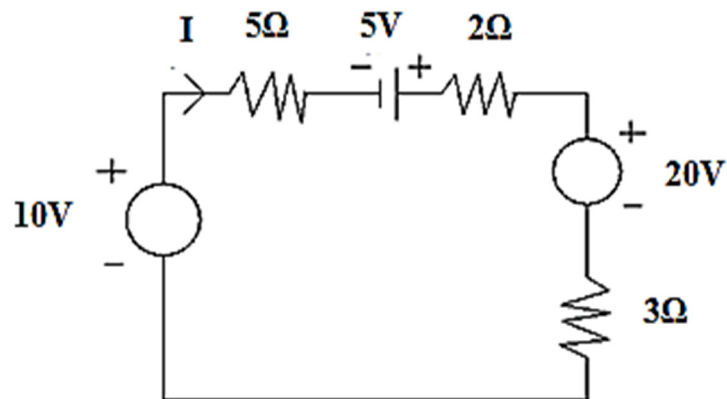
Q.2 i. Solve and find the value of I using KVL. **2**



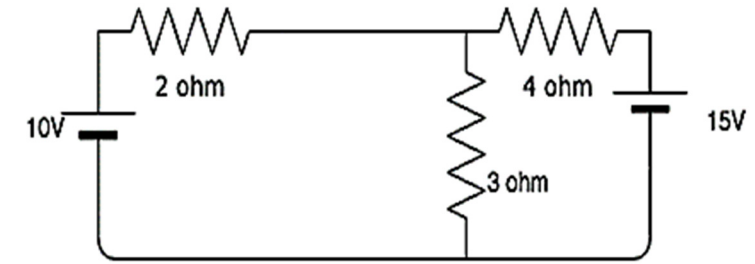- ii. If R_a , R_b and R_c are respectively the resistances of three sides of delta connection then derive the expression of resistances for equivalent star connection. **3**
- iii. State and explain Thevenin's theorem with example. **5**

[3]


- OR iv. Find the current through 2 ohm and 4 ohm resistor using mesh analysis **5**
 method.



- Q.3 i. Define the following terms: **2**
 (a) RMS value (b) Average value of alternating current
- ii. A resistance of 20Ω , inductance of $0.2H$ and capacitance of $100\mu F$ are connected in series across $220V$, $50Hz$ supply. Determine the following: (a) Impedance (b) Current (c) Voltage across R, L & C (d) Power factor and (e) Active and Apparant power **8**
- OR iii. Derive the relation between line and phase quantity in delta connection **8**
 of three phase ac system with circuit and phasor diagram.
- Q.4 i. Differentiate between core and shell type transformer. **3**
 ii. With neat sketch, describe the working principle of D.C motor. **7**
- OR iii. Write short notes on the following: (a) single phase induction motor **7**
 (b) Application of rotating electrical machines.

- Q.5 i. Describe about different types of electrical hazards and its precautions. **4**
 ii. What is UPS? Explain functioning of online UPS with block diagram. **6**
- OR iii. Differentiate between linear and switch mode power supply. **6**
- Q.6 Attempt any two: **5**
 i. Explain thermal power plants with appropriate diagram. **5**
 ii. Explain the principle of induction heating and write down its applications. **5**
 iii. Represent each component of power system in single line diagram **5**
 from generation to distribution.

Scheme of Marking

 Knowledge is Power	Faculty of Engineering End Sem Examination May-2023 EN3ES17 Basic Electrical Engineering	
	Programme: B.Tech.	Branch/Specialisation:

Note: The Paper Setter should provide the answer wise splitting of the marks in the scheme below.

Q.1	i)	(b) An independent voltage source in series to the equivalent resistance	1
	ii)	(c) Algebraic sum of all the e.m.fs plus algebraic sum of voltage drops is equal to zero	1
	iii)	(c) Inductive reactance (X_L) = Capacitive reactance (X_C)	1
	iv)	(a) 0	1
	v)	(d) Both (b) & (c)	1
	vi)	(b) Step down transformer	1
	vii)	(c) KWH	1
	viii)	(b) Uninterrupted Power Supply	1
	ix)	(a) Boiler, Turbine, Condenser, Pump	1
	x)	(d) All of the above	1
Q.2	i.	Applying KVL law – 01 Determination I - 01	2
	ii.	For each resistance expression for star one mark- 1+1+1	3
	iii.	Statement - 01 Explanation - 02 Example - 02	5
OR	iv.	Current through 2 ohm – 2.5 Current through 2 ohm – 2.5	5
Q.3	i.	RMS value - 01 Average value - 01	02
	ii.	Impedance - 01 Current- 01 Voltage across R,L,C- 03 Power factor - 01	8

OR	iii.	Active and Apparant power - 02 Circuit diagram - 02 Phasor diagram - 03 Relationship - 03	08
	Q.4	i. Three difference - 03 ii. Diagram - 03 Working principle explanation - 04	03 07
	OR	iii. Single phase induction motor - 04 Application of rotating machines - 03	07
Q.5	i.	Electrical hazards - 02 Precautions - 02	04
	ii.	Definition of UPS - 01 Block diagram of UPS - 3 Working - 02	06
OR	iii.	Three difference - 06 (02 each)	06
Q.6	i.	Diagram - 03 Explanation - 02	05
	ii.	Working principle- 03 Application - 02	05
	iii.	Single line diagram - 03 Component description - 02	05
