

Enrollment No.....



Faculty of Engineering / Science

End Sem Examination Dec-2023

EN3ES17 / BC3ES01 Basic Electrical Engineering

Programme: B.Tech. / B.Sc.

Branch/Specialisation: All

Duration: 3 Hrs.**Maximum Marks: 60**


Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d. Assume suitable data if necessary. Notations and symbols have their usual meaning.

- Q.1 i. If there are 5 nodes then the number of nodal equations are _____. **1**
 (a) 5 (b) 0 (c) 1 (d) 4
- ii. If there are 3 Resistors R_1 , R_2 and R_3 in series and V is total voltage and I is total current then Voltage across R_2 is- **1**
 (a) $V R_3 / (R_1 + R_2 + R_3)$ (b) $V R_2 / (R_1 + R_2 + R_3)$
 (c) $V R_1 / (R_1 + R_2 + R_3)$ (d) V
- iii. Peak value divided by the rms value gives us- **1**
 (a) Peak factor (b) Form factor
 (c) Power factor (d) None of these
- iv. If we apply a sinusoidal voltage to a circuit, the product of voltage and current is- **1**
 (a) True power (b) Apparent power
 (c) Average power (d) Reactive power
- v. Transformer ratings are given in _____. **1**
 (a) kVAR (b) HP (c) kVA (d) kW
- vi. What are the materials used for brushes in dc machines? **1**
 (a) Iron (b) Carbon (c) Aluminum (d) Steel
- vii. What is the principal on which MCB works? **1**
 (a) Magnetic effect of electric current
 (b) Lenz law
 (c) Faradays law of electric current
 (d) Flemings Right hand rule
- viii. SMPS is used for- **1**
 (a) Obtaining controlled ac power supply
 (b) Obtaining controlled dc power supply
 (c) Storage of dc power
 (d) Switch from one source to another


[2]

- ix. Power generation can be done by- 1
 (a) Thermal power plant (b) Nuclear power plant
 (c) Hydropower plant (d) All of these
- x. Welding transformer is _____. 1
 (a) Step-up transformer (b) Step-down transformer
 (c) Auto transformer (d) One-one transformer

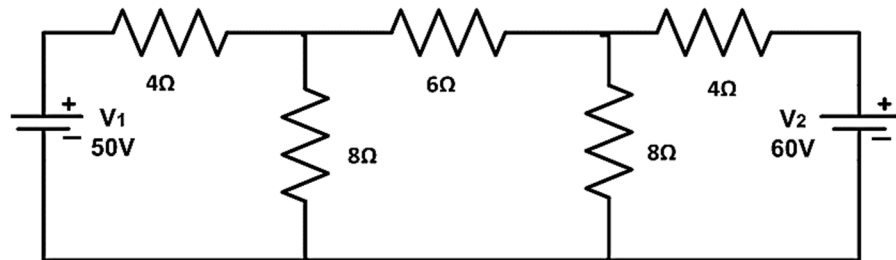- Q.2 i. Define linear and non-linear elements with examples. 2
 ii. With respect to DC circuit, state and explain Kirchhoff's law. 2
 iii. Find the value of current across resistor 6Ω resistor using Thevenin's Theorem. 6



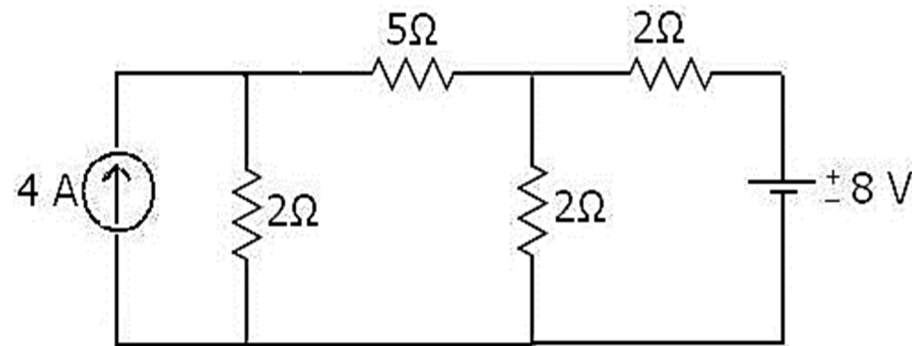- OR iv. Find the current in 5Ω resistance for the given network by using Nodal Analysis? 6




- Q.3 i. Write relation between line and phase quantities in star and delta connection in three phase system. 2
 ii. Find the impedance of a series R-L-C circuit, when $R=6\Omega$, $X_L=20\Omega$, and $X_C=10\Omega$. 2
 iii. A 4Ω resistor is series connected to a 10mH inductor across a 100 V, 50 Hz voltage source. Find input current, impedance, voltage drop across R and L, power factor of the circuit and the real power consumed in the circuit. 6
- OR iv. Draw & explain the phasor diagram of RLC series circuit and give the condition for resonance in this circuit. 6

[3]

- Q.4 i. Explain the working principle of single-phase transformer. 2
 ii. Write the applications of single-phase induction motor. 2
 iii. With a neat diagram, explain the working principle & constructional details of DC motor. 6
- OR iv. Explain the working principle & construction of three phase induction motor. 6
- Q.5 i. What is the necessity of earthing in domestic buildings? 2
 ii. Describe the following in few words: 2
 (a) Fuse (b) MCB
 iii. What is a electric power supply system? Explain and draw a block diagram of a liner power supply. 6
- OR iv. Describe and illustrate an SMPS block diagram. 6
- Q.6 Attempt any two:
 i. Draw a neat schematic diagram of a hydro-electric power plant and explain the functions of various components. 5
 ii. Draw a neat schematic diagram of a thermal power plants and explain its operation. 5
 iii. Explain the principle of induction heating and write down its applications. 5


Scheme of Marking

	Faculty of Engineering	
	End Sem Examination Dec-2023	
	Basic Electrical Engineering (T) - EN3ES17 (T)	
Programme: B.Tech.	Branch/Specialisation: All	


Note: The Paper Setter should provide the answer wise splitting of the marks in the scheme below.

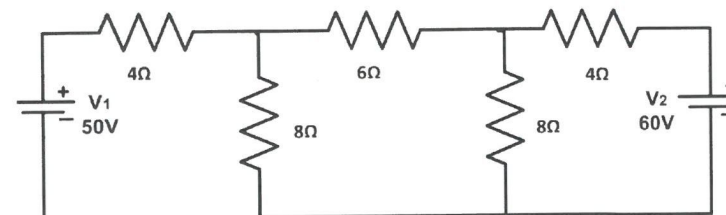- Q.1 i) If there are 5 nodes then the number of nodal equations are 1 1
 d) 4
- ii) If there are 3 Resistors R_1 , R_2 and R_3 in series and V is total voltage and I is total current then Voltage across R_2 is 1 1
 b) $V R_2 / R_1 + R_2 + R_3$
- iii) Peak value divided by the rms value gives us? 1
 a) Peak factor
- iv) If we apply a sinusoidal voltage to a circuit, the product of voltage and current is? 1
 b) apparent power
- v) Transformer ratings are given in 1 1
 c) kVA
- vi) What are the materials used for brushes in dc machines? 1
 b) Carbon
- vii) What is the principal on which MCB works? 1
 a) Magnetic effect of electric current
- viii) SMPS is used for 1
 b) obtaining controlled dc power supply
- ix) Which of the following is a type of power plant? 1
 d) All of the mentioned
- x) Welding transformer is 1 1
 b) step-down transformer
- Q.2 i. Define linear – 01 2
 non-linear elements. – 01
- ii. With respect to DC circuit, state -01 2
 explain Kirchhoff's law. -01
- iii. Find the value of current across resistor 6Ω resistor using Thevenin's 6

Theorem. Ans: $V_a=33.3$, $V_b=40$,
 $V_{ab}=V_{th}=-6.67V$, -02
 $R_{th}=5.33$, -02
 $I=-0.589A$ -02



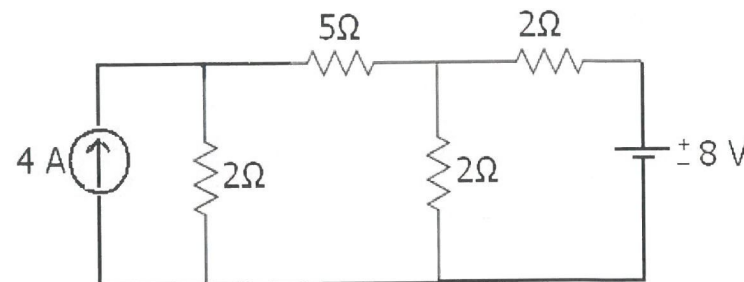- OR iv. Find the current in 5Ω resistance for the given network by using Nodal Analysis? Ans: $I_{5\Omega}=0.5A$ 6
 First Eq -----02
 Second Eq -----02
 $I=0.5A$ -----02



- Q.3 i. Write relation between line and phase quantities in star -01 2
 and delta connection in three phase system. – 01
- ii. Find the impedance of a series R-L-C circuit, when $R=6\Omega$, $X_L=20\Omega$, $X_C=10\Omega$. Ans: $Z=11.66\Omega$ - 02 2
- iii. A 4Ω resistor is connected to a $10mH$ inductor across a $100V$, $50Hz$ voltage source. Find input current, impedance, voltage drop across R and L , power factor of the circuit and the real power consumed in the circuit. 6
 $I=19.66A$, $Z=5.08\Omega$, $V_R=78.65V$, $V_L=61.75V$, $p.f.=0.787(\text{Lag})$,
 $P=1546W$ -01 for each
- OR iv. Draw & explain the phasor diagram of RLC series - 03 6
 circuits and give the condition for resonance in this circuit. – 03
- Q.4 i. Define transformer. - 02 2

principle - 01
explanation - 01

[2]


[3]

- ii. Explain the working principle of single-phase transformer. – 01 *Any two applications (1 mark each)* 2
- iii. With a neat diagram, explain the working principle & constructional details of DC motor. – 02 6
- OR iv. Explain the working principle & construction of three phase induction motor. – 03 6
- Q.5 i. What is the necessity of earthing in domestic buildings? – 02 2
- ii. Write a short note on (i) Fuse and (ii) Electric shock. – 01 2
- iii. What is an electric power supply system? Explain and draw a block diagram of a liner power supply. – 02 6
- OR iv. Describe and illustrate an SMPS block diagram. – 03 6
- Q.6 Attempt any two:
- i. Draw a neat schematic diagram of a hydro-electric power plant and explain the functions of various components. – 2.5 5
- ii. Draw a neat schematic diagram of a thermal power plants and explain its operation. – 2.5 5
- iii. Explain the principle of induction heating and write down its applications. – 3 – 2 5


Solution

①

Q. 2 (iii)

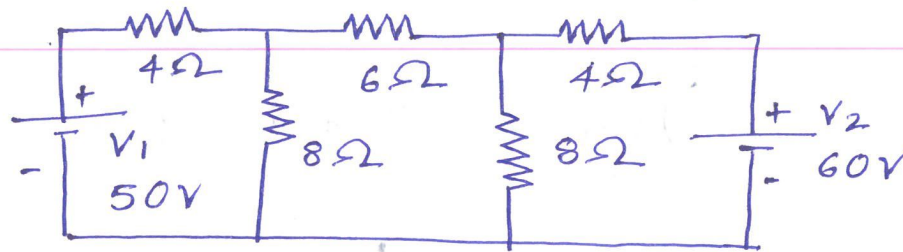


Step-1 calculation of R_{th}

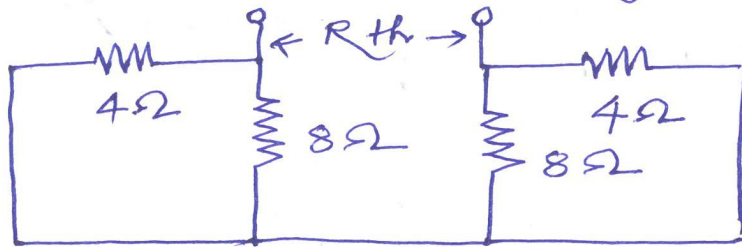

$$R_{th} = 4 \parallel 8 + 4 \parallel 8 = \frac{4 \times 8}{4 + 8} + \frac{4 \times 8}{4 + 8} = 2.667 + 2.667 = \boxed{5.33 \Omega} \quad \text{--- } \underline{2}$$

Step-2 calculation of V_{th}

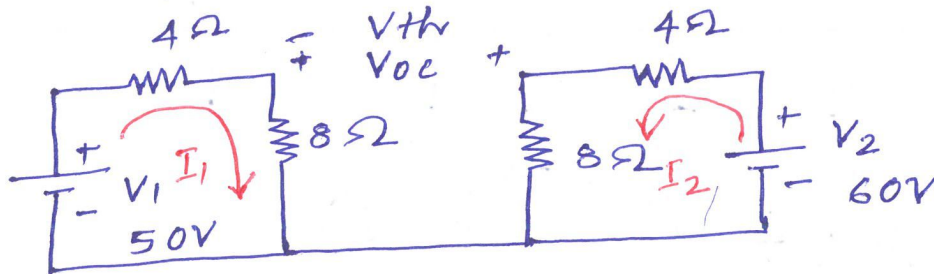


Applying KVL to Loop-1

$$-50 + 4I_1 - 8I_1 = 0 \Rightarrow 12I_1 = 50 \Rightarrow I_1 = 50$$

step-3 calculation of current through 6Ω


$$R_{th} = 5.33\Omega$$

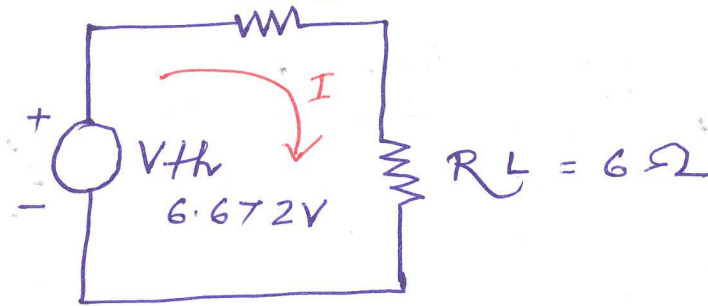

2

$$I = \frac{V_{th}}{R_{th} + R_L} = \frac{6.672}{5.33 + 6} = \boxed{0.589 \text{ A}} \dots \dots 2$$

Nodal Analysis method ^{OR}

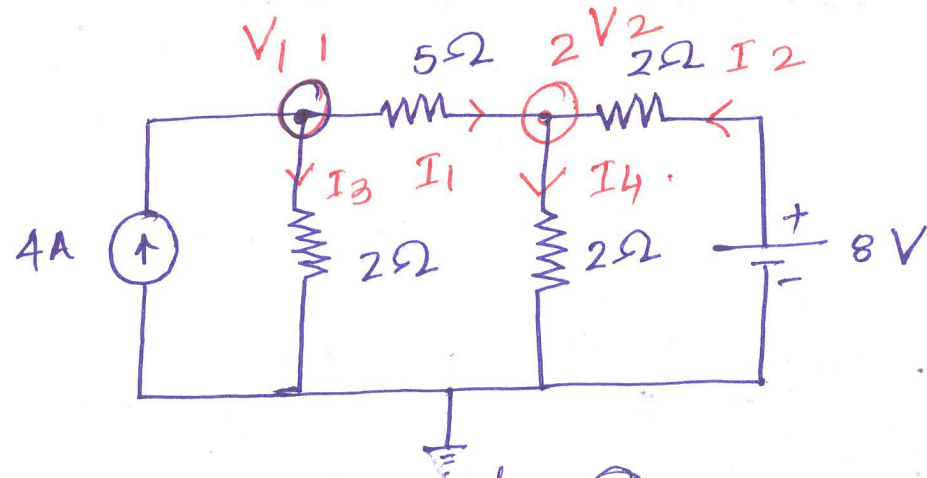

Applying KCL at node ①

$$4 = I_1 + I_2 \Rightarrow 4 = \frac{V_1 - V_2}{5} + \frac{8 - V_2}{2}$$

$$\Rightarrow \frac{V_2}{2} = \frac{2V_1 - 2V_2 + 80 - 5V_2}{10} \quad (3)$$

$$\Rightarrow 10V_2 = 4V_1 - 4V_2 + 80 - 10V_2$$

$$\Rightarrow 20V_2 + 4V_2 - 4V_1 - 80 = 0 \Rightarrow \boxed{24V_2 - 4V_1 - 80 = 0} \quad (1)$$

At node - 1

$$4 = I_1 + I_3 = \frac{V_1 - V_2}{5} + \frac{V_1}{2}$$

$$\Rightarrow 40 = 2V_1 - 2V_2 + 5V_1$$

$$\Rightarrow \boxed{2V_2 - 7V_1 + 40 = 0} \quad (2)$$

from (1) & (2)

$$24V_2 - 4V_1 - 80 = 0$$

$$12 \times 2V_2 - 7V_1 + 40 = 0$$

$$\underline{24V_2 - 4V_1 - 80 = 0}$$

$$- 24V_2 - 84V_1 + 480 = 0$$

$$\underline{+}$$


$$80V_1 - 560 = 0$$

$$\Rightarrow V_1 = \frac{560}{80} = \boxed{7V}$$

$$2V_2 - 49 + 40 = 0 \Rightarrow 2V_2 = 9 \Rightarrow V_2 = \boxed{4.5V}$$

Now current through 5Ω .

(iii)

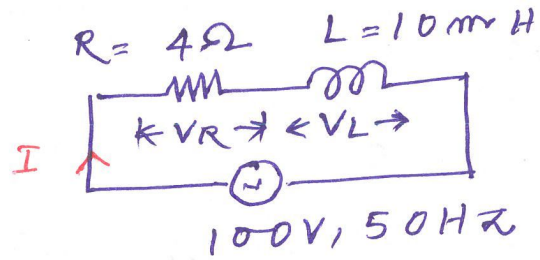

4

L $R = 4\Omega$, $L = 10\text{ mH} = 10 \times 10^{-3}\text{ H} = 0.01\text{ H}$

$$X_L = 2\pi f L = 2\pi \times 50 \times 0.01 = 3.141\Omega$$

$$\therefore Z = \sqrt{R^2 + X_L^2} = \sqrt{4^2 + (3.141)^2} = \sqrt{25.8658} \\ = \boxed{5.08\Omega} \quad \checkmark$$

$$I = \frac{V}{Z} = \frac{100}{5.08} = \boxed{19.685\text{ A}} \quad \checkmark$$

$$V_R = IR = 19.685 \times 4 = \boxed{78.74\text{ V}}$$

$$V_L = I X_L = 19.685 \times 3.141 = \boxed{61.83\text{ V}}$$

$$p.f = \cos \phi = \frac{R}{Z} = \frac{4}{5.08} = \boxed{0.787 \text{ (lagging)}}$$

$$\text{real power} = VI \cos \phi \\ = 100 \times 19.685 \times 0.787 \\ = \boxed{1549.2\text{ W}}$$