

Enrollment No.....



**Faculty of Engineering**  
**End Sem (Odd) Examination Dec-2022**  
**ME3EM02 Electronics Devices & Circuits**

Programme: B.Tech.

Branch/Specialisation: ME

**Duration: 3 Hrs.****Maximum Marks: 60**


Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.

- Q.1 i. The electrons in the conduction band are known as \_\_\_\_\_. 1  
 (a) Bound electrons (b) Valence electrons  
 (c) Free electrons (d) None of these
- ii. When a pentavalent impurity is added to a pure semiconductor, it becomes \_\_\_\_\_. 1  
 (a) An insulator (b) An intrinsic semiconductor  
 (c) p-type semiconductor (d) n-type semiconductor
- iii. The leakage current in a crystal diode is due to \_\_\_\_\_. 1  
 (a) Minority carriers (b) Majority carriers  
 (c) Junction capacitance (d) None of these
- iv. A Zener diode is always \_\_\_\_\_ connected. 1  
 (a) Reverse (b) Forward  
 (c) Either reverse or forward (d) None of these
- v. The ripple factor of a half-wave rectifier is \_\_\_\_\_. 1  
 (a) 2 (b) 1.21 (c) 2.5 (d) 0.48
- vi. The input impedance of a transistor is \_\_\_\_\_. 1  
 (a) High (b) Low (c) Very high (d) Almost zero
- vii. The disadvantage of voltage divider bias is that it has \_\_\_\_\_. 1  
 (a) High stability factor (b) Low base current  
 (c) Many resistors (d) None of these
- viii. The gate of a JFET is \_\_\_\_\_ biased. 1  
 (a) Reverse (b) Forward  
 (c) Reverse as well as forward (d) None of these
- ix. Positive feedback is also known as- 1  
 (a) Regenerative feedback (b) Degenerative feedback  
 (c) Loop feedback (d) Return feedback

P.T.O.

[2]

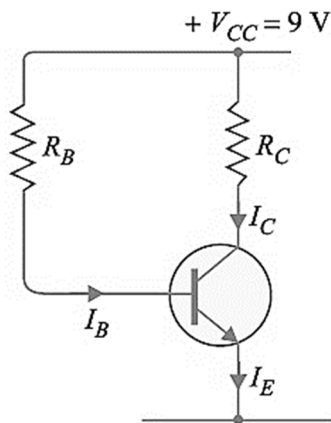- x. With negative feedback, the linearity of operation of the amplifier circuit- **1**  
 (a) Deteriorates (b) Improves  
 (c) Remain same (d) None of these
- Q.2 i. Explain the semiconductor material and its types. **3**  
 ii. Explain the hall effect and derive the expression for hall voltage. **7**
- OR iii. With the help of necessary equations, explain the term drift current and diffusion current. **7**
- Q.3 i. What is doping? What are the majority and minority charge carriers in semiconductor? **3**  
 ii. Describe the action of PN junction diode under forward bias and reverse bias. **7**
- OR iii. Define and explain the working of tunnel diode. **7**
- Q.4 i. What is a clipper? Also describe the following: **3**  
 (a) Positive clipper (b) Biased clipper  
 ii. Define and explain the working principle of a PNP transistor. **7**
- OR iii. With a neat sketch, explain the working of the following: **7**  
 (a) Centre-tap full-wave rectifier (b) Full-wave bridge rectifier.
- Q.5 i. Define the transistor biasing. **3**  
 ii. The figure shown below shows biasing by base resistor method. If it is required to set the operating point at 1mA, 6 V, find the values of  $R_C$  and  $R_B$ . Given  $\beta = 150$ ,  $V_{BE} = 0.3$  V. **7**



[3]

- OR iii. Write the comparison between JFET and MOSFET. **7**
- Q.6 Attempt any two:
- i. Define feedback amplifier. Explain the working principle of feedback amplifier. **5**  
 ii. Draw and explain the circuit diagram of Hartley Oscillator. **5**  
 iii. Draw and explain the working of Colpitts Oscillator. **5**

\*\*\*\*\*



## Scheme of Marking

Faculty of Engineering

End Sem (Odd) Examination Dec-2020

Electronics Device and Circuit (T) - ME3EM02

Programme: B.Tech.

Branch/Specialisation: ME

- Q.1
- The electrons in the conduction band are known as..... 1  
(c) free electrons
  - When a pentavalent impurity is added to a pure semiconductor, it becomes..... 1  
(d) n-type semiconductor
  - The leakage current in a crystal diode is due to..... 1  
(a) minority carriers
  - A zener diode is always ..... connected. 1  
(a) reverse
  - The ripple factor of a half-wave rectifier is..... 1  
(d)  $0.48$   $\frac{1}{\sqrt{2}}$
  - The input impedance of a transistor is..... 1  
(b) low
  - The disadvantage of voltage divider bias is that it has..... 1  
(c) many resistors
  - The gate of a JFET is ..... biased. 1  
(a) reverse
  - Positive feedback is also known as 1  
(a) regenerative feedback
  - With negative feedback, the linearity of operation of the amplifier circuit 1  
(b) improves
- Q.2
- Explain the semiconductor material and its types. 3  
Semiconductor material - 1 Mark  
Forward Biasing - 1 Mark  
Reverse Biasing - 1 Mark
  - Explain the Hall Effect and derive the expression for Hall Voltage. 7  
Hall Effect - 2 Marks  
Expression for Hall Voltage - 5 Marks

- OR
- With the help of necessary equations; Explain the term Drift Current and Diffusion Current. 7  
Drift Current and equation - 3.5 Marks  
Diffusion Current and equation - 3.5 Marks
- Q.3
- What is doping? What are the majority and minority charge carriers in semiconductor? 3  
Doping - 1 Mark  
Majority Charge Carrier - 1 Mark  
Minority Charge Carrier - 1 Mark
  - Describe the action of PN junction diode under forward bias and reverse bias. 7  
Forward Biasing - 3 Marks  
Reverse Biasing - 4 Marks
- OR
- Define and explain the working of Tunnel Diode. 7  
Definition - 2 Marks  
Working - 5 Marks
- Q.4
- What is a clipper? Describe (i) positive clipper (ii) biased clipper 3  
Clipper - 1 Mark  
Positive Clipper - 1 Mark  
Biased Clipper - 1 Mark
  - Define and explain the working principle of a PNP transistor. 7  
PNP Transistor - 2 Marks  
Working Principle - 5 Marks
- OR
- With a neat sketch, explain the working of (a) Centre-tap full-wave rectifier (b) Full-wave bridge rectifier. 7  
Diagram of Centre-Tap - 1 Mark  
Working of Centre-Tap - 3 Marks  
Diagram of Full Wave bridge - 1 Mark  
Working of Full Wave bridge - 2 Marks
- Q.5
- Define the transistor biasing. 3  
Transistor Biasing - 3 Marks
  - The figure shown below shows biasing by base resistor method. If it is required to set the operating point at  $1\text{mA}$ ,  $6\text{V}$ , find the values of  $R_C$  and  $R_B$ . Given  $\beta = 150$ ,  $V_{BE} = 0.3\text{V}$ . 7  
Solution:  
 $R_C = 3\text{ k}\Omega$ , - 3 Marks  
 $R_B = 1.3\text{ M}\Omega$  - 4 Marks
- OR
- Write the comparison between JFET and MOSFET. 7

- Q.6 Attempt any two:
- |      |   |           |
|------|---|-----------|
| i.   | Define feedback amplifier. Explain the working principle of feedback amplifier. | 5         |
|      | Feedback Amplifier  | - 2 Marks |
|      | Working   | - 3 Marks |
| ii.  | Draw and explain the diagram of Hartley Oscillator.                             | 5         |
|      | Diagram   | - 2 Marks |
|      | Explanation   | - 3 Marks |
| iii. | Draw and explain the diagram of Colpitts Oscillator.                            | 5         |
|      | Diagram   | - 2 Marks |
|      | Explanation   | - 3 Marks |

\*\*\*\*\*