

Enrollment No.....



Faculty of Engineering
End Sem Examination May-2023
EC3CO12 VLSI Design

Programme: B.Tech.

Branch/Specialisation: EC

Duration: 3 Hrs.**Maximum Marks: 60**

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d. Assume suitable data if necessary. Notations and symbols have their usual meaning.

- Q.1 i. In MOSFET devices the N-channel type is better than the P – Channel type in the following respect- **1**
 (a) It has better immunity (b) It is Faster
 (c) It is TTL compatible (d) It has better drive capability
- ii. How many TG are required to implement 4 x 1 mux? **1**
 (a) 3 (b) 4 (c) 5 (d) 6
- iii. In the CMOS inverter circuit if the transconductance parameters of NMOS and PMOS transistor are $K_n = K_p = \mu_n C_{ox} W_n / L_n = \mu_p C_{ox} W_p / L_p = 40 \mu A / V^2$ and threshold voltages are $V_T = 1V$, $V_{GS} = 2.5V$, $V_{DD} = 5V$ then the current I_D is- **1**
 (a) 0 A (b) 25 μA (c) 45 μA (d) 90 μA
- iv. In CMOS circuits, which type of power dissipation occurs due to switching of transient current and charging & discharging of load capacitance? **1**
 (a) Static dissipation (b) Dynamic dissipation
 (c) Both (a) and (b) (d) Open Circuit dissipation
- v. Two states are said to be equivalent states if they have exactly same- **1**
 (a) Inputs (b) Next state (c) Output (d) Both (b) and (c)
- vi. In a sequence detector, if the required bit is at its input while checking the sequence bit by bit, the detector moves to- **1**
 (a) Previous state (b) Next state
 (c) present state (d) Null state
- vii. If there are 7 states in any sequential circuit, then its merger table will contain _____ squares(cells). **1**
 (a) 10 (b) 11 (c) 21 (d) 20

P.T.O.

[2]

- viii. When a circuit goes through a unique sequence of unstable states then it is called as- **1**
 (a) Hazards (b) Glitch (c) Cycle (d) Race
- ix. In modern ICS _____ is used as gate material. **1**
 (a) Polysilicon (b) Si (c) Cu (d) Al
- x. Which gives scalable design rules? **1**
 (a) Micron rules (b) Layer rules
 (c) Thickness rules (d) Lambda rules

- Q.2 i. What is body effect? **2**
 ii. Explain the term pass transistor with example. **3**
 iii. Explain the operation of negative edge-triggered register using complementary switch. **5**

- OR iv. Describe the equation for source to drain current in the three regions of operation of a PMOS transistor and draw the VI characteristics. **5**

- Q.3 i. Define rise time, fall time and propagation delay. **3**
 ii. What is PDP? Derive expression for dynamic power dissipation. **7**

- OR iii. Draw and explain the DC characteristics of a CMOS inverter with necessary conditions for the different regions of operation. **7**

- Q.4 i. Discuss mealy to moore machine conversion with example. **4**
 ii. Design a sequence detector which detects sequence "0110" for input X and produce output Z as '1'. Realize the hardware (overlapping allowed). **6**

- OR iii. Determine the minimal state table equivalent to the following using merger graph method: **6**

Present State	Next state, output	
	X = 0	X = 1
A	B,0	C,1
B	A,1	E,0
C	D,0	A,1
D	C,1	E,0
E	A,1	F,0
F	E,0	F,1

- Q.5 i. What is fundamental mode & pulse mode operation? **2**
 ii. What do you mean by race? Explain types of races with proper example. **3**

[3]


- iii. Find race free state assignment for following flow table: **5**

a	c	d	a
a	d	b	b
d	c	b	a
d	d	d	b

- OR iv. What is hazard? Find the circuit that has no static hazards and implement the Boolean function $F(A,B,C,D)=\sum m(1,5,6,7)$. **5**


- Q.6 Attempt any two: **5**
 i. Explain the different steps involved in n-well CMOS fabrication process with neat diagrams. **5**
 ii. Describe architecture of FPGA. **5**
 iii. What are layout design rules? Design the layout of CMOS inverter with suitable design rules. **5**

Scheme of Marking

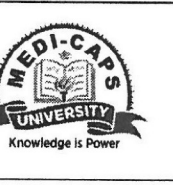	<p>Faculty of Engineering End Sem Examination May-2023 EC3CO12 VLSI Design</p>
Programme: B.Tech.	Branch/Specialisation:


The Paper Setter should provide the answer wise splitting of the marks in the scheme below.

1	i)	(b) It is Faster	1
	ii)	(d) 6	1
	iii)	(c) 45 μ A	1
	iv)	(b) Dynamic dissipation	1
	v)	d. both b and c	1
	vi)	b. Next state	1
	vii)	(c) 21	1
	viii)	(c) cycle	1
	ix)	(a) Polysilicon	1
	x)	(d) lambda rules	1
2	i.	definition	2
	ii.	definition	1.5,1.5
	iii.	diagram & working	2.5,2.5
	iv.	diagram & working	2.5,2.5
3	i.	Each definition	3
	ii.	Definition & derivation	3,4
	iii.	Characteristics & diagram with equations	3,2,2
4	i.	Conversion with example	2,2
	ii.	Solution with hardware	3,3

 


OR	iii.	PS		NS		Z		3,3
				X=0	X=1	X=0	X=1	
		A	B	A		0	1	
		B	A	E		1	0	
		E	A	F		1	0	
		F	E	F		0	1	
		$A \equiv C \ B \equiv D$						
Q.5	i.	definition						
	ii.	Race with example						
	iii.	solution						
OR	iv.	Definition & solution						
Q.6	i.	Steps & diagram						
	ii.	Architecture diagram & explanation						
	iii.	Definition & design						

Q.5(iiv) $f = \sum m(1,5,6,7)$ *****

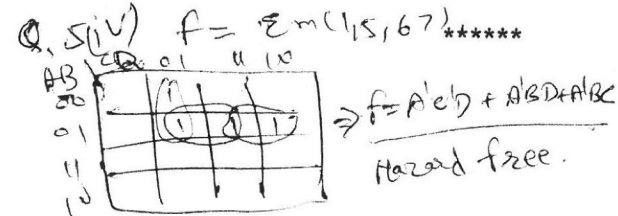

$f = A'c'd + A'Bd + A'Bc$
Hazard free.

Q.5(ii) $\sum m(0,1,2,3,4,5,6,7)$

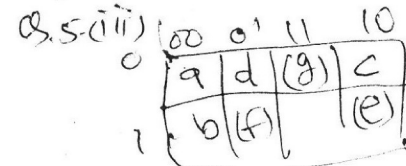

$f = 1$

(i) $a \leftrightarrow c$ via (g)
(ii) $d \leftrightarrow b$ via (f)
(iii) $c \leftrightarrow b$ via (e)