

[4]

- iii. Describe the construction, operation and V-I characteristics of a P-N diode. What do you mean by cut-in voltage? **5**
- OR iv. Draw and explain output characteristic of transistor in CE configuration. **5**
- Q.6 i. Explain De-Morgan's Theorem. **2**
- ii. What are universal gates and why they are called so? **3**
- iii. Draw and explain half adder and full adder for binary addition. **5**
- OR iv. Convert the following numbers into the respective index given: **5**
- (a)  $(1011.101101)_2 = ( )_{10}$  (b)  $(374.37)_{10} = ( )_{16}$
- (c)  $(3AB)_{16} = ( )_2$  (d)  $(36.125)_8 = ( )_{10}$
- (e)  $(324.987)_{10} = ( )_8$

\*\*\*\*\*

Total No. of Questions: 6

Total No. of Printed Pages:4

Enrollment No.....



Faculty of Engineering  
End Sem (Odd) Examination Dec-2018  
EN3ES04 Basic Electrical and Electronics Engineering  
Programme: B.Tech. Branch/Specialisation: All

Duration: 3 Hrs.

Maximum Marks: 60

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.


- Q.1 i. A voltage source of 100V with internal resistance  $5\Omega$  may be represented by a current source of **1**
- (a) A current source of 20A with a resistance of  $5\Omega$  in parallel  
(b) A current source of 40A with a resistance of  $2.5\Omega$  in parallel  
(c) A current source of 500A with a resistance of  $5\Omega$  in parallel  
(d) A current source of 20A with a resistance of  $5\Omega$  in series
- ii. The efficiency at maximum power transfer is **1**
- (a) 100% (b) 80% (c) 50% (d) 40%
- iii. A current wave represented by  $i = I_{\max} \sin \theta$ , has its 50% of maximum value at, **1**
- (a)  $\theta = 45^\circ$  (b)  $\theta = 30^\circ$  (c)  $\theta = -210^\circ$  (d)  $\theta = 30^\circ$  and  $\theta = 150^\circ$
- iv. The unit of flux density is, **1**
- (a) tesla (b)  $A/m^2$  (c)  $Wb/mm^2$  (d)  $Wb/cm^2$
- v. Copper losses at full load operation are 1600W. If the load on the transformer is reduced to 75% of full load, the copper loss will be, **1**
- (a) 1600W (b) 1200W (c) 900W (d) 800W
- vi. The nature of operating p.f. of 3-phase induction motor is, **1**
- (a) Always lagging (b) Leading  
(c) May be leading or lagging (d) Unity
- vii. A zener diode is always ..... connected. **1**
- (a) Reverse (b) Forward  
(c) Either reverse or forward (d) None of these

P.T.O.


[2]

- viii. The voltage gain of a transistor connected in common collector arrangement is ..... **1**  
 (a) Equal to 1 (b) More than 10  
 (c) More than 100 (d) Less than 1
- ix. The 2's complement of  $1000_2$  is **1**  
 (a) 0111 (b) 0101 (c) 1000 (d) 0001
- x. The number  $100101_2$  is equivalent to octal **1**  
 (a) 54 (b) 45 (c) 37 (d) 25

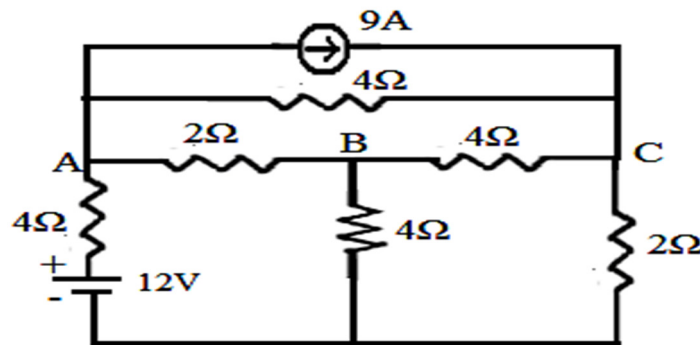- Q.2 i. Explain Kirchhoff's current and voltage law. **2**  
 ii. State and explain maximum power transfer theorem. **3**  
 iii. Use Nodal analysis to determine the voltage across BC and the current in the 12V source. **5**



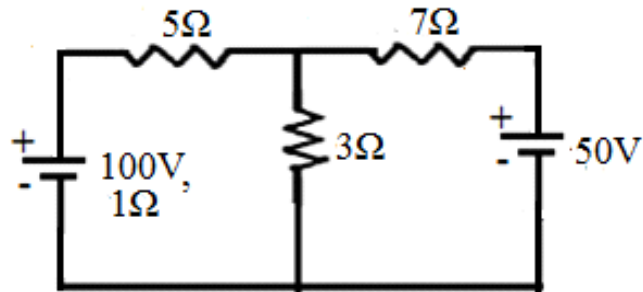- OR iv. State and explain superposition theorem. Use superposition theorem to determine currents in all the branches in given network. **5**



- Q.3 i. What are similarities in magnetic and electric circuits? **2**

[3]

- ii. Drive the condition for resonance in a series circuit. Explain Q factor of series resonant circuit. **3**
- iii. A coil of resistance  $10\Omega$  and inductance  $0.1H$  is connected in series with a capacitor of  $150mF$  across a  $230V, 50Hz$  supply. Determine : **5**  
 (a) Impedance (b) Current drawn from supply  
 (c) Voltage drop across coil (d) Power factor of circuit  
 (e) Power factor of the coil.

- OR iv. A  $60Hz$  sinusoidal voltage  $v=100\sin\omega t$  is supplied to a series R-L circuit. Assuming  $R=10\Omega, L=0.001H$ . Find the steady state current and relative phase angle. Also compute the effective magnitude and phase of voltage drop across each circuit elements. **5**


- Q.4 i. Explain the principle of operation of a DC motor. **2**  
 ii. Show that  $\frac{V_2}{V_1} = \frac{E_2}{E_1} = \frac{N_2}{N_1} = \frac{I_1}{I_2} = K$  in a single phase transformer. **3**  
 iii. Draw and explain the phasor diagram of transformer when it is operating lagging power factor. **5**
- OR iv. A  $10kVA, 200/400V, 50Hz$ . Single phase transformer gave the following test results: **5**  
 Open circuit test- $200V, 1.25A, 120W$ , on low voltage side  
 Short circuit test-  $20V, 25A, 200W$ , on high voltage side.  
 Calculate:  
 (a) OCT circuit parameters  
 (b) SCT circuit parameters  
 (c) Full load efficiency at unity p.f.  
 (d) Half load efficiency at  $0.8$  lagging p.f.  
 (e) Iron loss and copper loss

- Q.5 i. Justify that full wave rectifier is more efficient than half wave rectifier. **2**  
 ii. Explain how a Zener diode maintains constant voltage across the load. **3**


P.T.O.

Marking Scheme  
EN3ES04 Basic Electrical and Electronics Engineering

- Q.1
- |       |                                                                                                                                        |   |
|-------|----------------------------------------------------------------------------------------------------------------------------------------|---|
| i.    | A voltage source of 100V with internal resistance $5\Omega$ may be represented by a current source of                                  | 1 |
|       | (a) A current source of 20A with a resistance of $5\Omega$ in series                                                                   |   |
| ii.   | The efficiency at maximum power transfer is                                                                                            | 1 |
|       | (c) 50%                                                                                                                                |   |
| iii.  | A current wave represented by $i = I_{\max} \sin \theta$ , has its 50% of maximum value at,                                            | 1 |
|       | (d) $\theta = 30^\circ$ and $\theta = 150^\circ$                                                                                       |   |
| iv.   | The unit of flux density is,                                                                                                           | 1 |
|       | (a) tesla                                                                                                                              |   |
| v.    | Copper losses at full load operation are 600W. If the load on the transformer is reduced to 75% of full load, the copper loss will be, | 1 |
|       | (c) 900W                                                                                                                               |   |
| vi.   | The nature of operating p.f. of 3-phase induction motor is,                                                                            | 1 |
|       | (a) always lagging                                                                                                                     |   |
| vii.  | A zener diode is always ..... connected.                                                                                               | 1 |
|       | (a) reverse                                                                                                                            |   |
| viii. | The voltage gain of a transistor connected in common collector arrangement is .....                                                    | 1 |
|       | (d) less than 1                                                                                                                        |   |
| ix.   | The 2's complement of $1000_2$ is                                                                                                      | 1 |
|       | (c) 1000                                                                                                                               |   |
| x.    | The number $100101_2$ is equivalent to octal                                                                                           | 1 |
|       | (b) 45                                                                                                                                 |   |
- Q.2
- |      |                                                       |         |   |
|------|-------------------------------------------------------|---------|---|
| i.   | Explain Kirchhoff's current                           | 1 mark  | 2 |
|      | Voltage law.                                          | 1 mark  |   |
| ii.  | State                                                 | 1 mark  | 3 |
|      | and explain maximum power transfer theorem.           | 2 marks |   |
| iii. | Use Nodal analysis to determine the voltage across BC |         | 5 |
|      |                                                       | 2 marks |   |
|      | The current in the 12V source.                        | 3 marks |   |

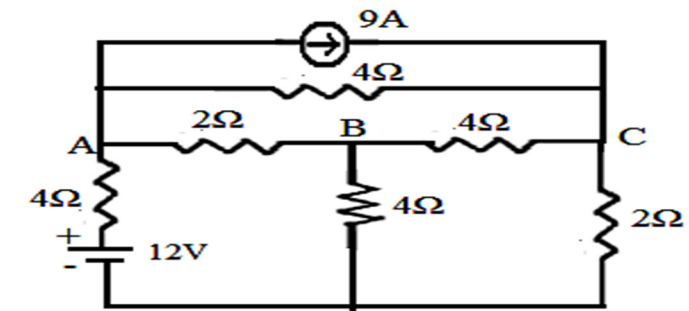

- OR
- |     |                                                                        |         |   |
|-----|------------------------------------------------------------------------|---------|---|
| iv. | State and explain superposition theorem.                               | 2 marks | 5 |
|     | Use superposition theorem to determine branch current in given network |         |   |
|     | 1 mark in each branch current (1 mark *3)                              | 3 marks |   |

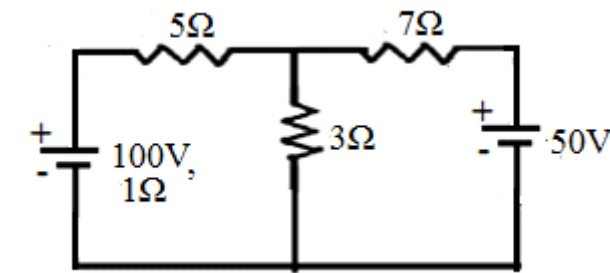

- Q.3
- |      |                                                                                                                                                                                                 |                                                                                                                                                                                                        |         |
|------|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---------|
| i.   | Similarities in magnetic and electric circuits                                                                                                                                                  |                                                                                                                                                                                                        | 2       |
|      | 0.5 mark in each similarities                                                                                                                                                                   | (0.5 mark *4)                                                                                                                                                                                          |         |
| ii.  | Drive the condition for resonance in a series circuit                                                                                                                                           | 2 marks                                                                                                                                                                                                | 3       |
|      | Q factor of series resonant circuit.                                                                                                                                                            | 1 mark                                                                                                                                                                                                 |         |
| iii. | A coil of resistance $10\Omega$ and inductance $0.1\text{H}$ is connected in series with a capacitor of $150\text{mF}$ across a $230\text{V}$ , $50\text{Hz}$ supply. Determine 1 mark for each |                                                                                                                                                                                                        | 5       |
|      | (a) impedance                                                                                                                                                                                   | (1 mark *5)                                                                                                                                                                                            |         |
|      | (b) current drawn from supply                                                                                                                                                                   |                                                                                                                                                                                                        |         |
|      | (c) voltage drop across coil                                                                                                                                                                    |                                                                                                                                                                                                        |         |
|      | (d) power factor of circuit                                                                                                                                                                     |                                                                                                                                                                                                        |         |
|      | (e) power factor of the coil.                                                                                                                                                                   |                                                                                                                                                                                                        |         |
| OR   | iv.                                                                                                                                                                                             | A $60\text{Hz}$ sinusoidal voltage $v = 100 \sin \omega t$ is supplied to a series RL circuit. Assuming $R = 10\Omega$ , $L = 0.001\text{H}$ . Find the steady state current and relative phase angle. | 5       |
|      |                                                                                                                                                                                                 |                                                                                                                                                                                                        | 2 marks |

		Complete the effective magnitude and phase of voltage drop across each circuit elements.	3 marks	
Q.4	i.	Principle of operation of a DC motor	2 marks	2
	ii.	Show that $\frac{V_2}{V_1} = \frac{E_2}{E_1} = \frac{N_2}{N_1} = \frac{I_1}{I_2} = K$ in a single phase transformer.	3 marks	3
	iii.	Daigram Phasor diagram of transformer when it is operating lagging power factor.	3 marks 2 marks	5
OR	iv.	A 10kVA, 200/400V, 50Hz. Single phase transformer gave the following test results: Open circuit test 200V, 1.25A, 120W, on low voltage side Short circuit test 20V, 25A, 200W, on high voltage side. Calculate: 1 mark for each (1 mark *5) (a) OCT circuit parameters (b) SCT circuit parameters (c) Full load efficiency at unity p.f. (d) Half load efficiency at 0.8 lagging p.f. (e) Iron loss and copper loss		5
Q.5	i.	Full wave rectifier is more efficient that half wave rectifier.		2
	ii.	Zener diode maintains constant voltage across the load. Circuit diagram Waveform Explanation	1 mark 1 mark 1 mark	3
	iii.	Construction, Operation and VI characteristics of a PN diode. What do you mean by cutin voltage	2 marks 2 marks 1 mark	5
OR	iv.	Diagram Output characteristic of transistor in CE configuration.	2 marks 3 marks	5
Q.6	i.	DeMorgan's Theorem		2
	ii.	Universal gates Why they are called so?	2 marks 1 mark	3

	iii.	Half adder and diagram Full adder for binary addition.	2 marks 3 marks	5
OR	iv.	Convert the following numbers into the respective index given: 1 mark for each conversion (1 mark * 5) (a) $(1011.101101)_2 = ( )_{10}$ (b) $(374.37)_{10} = ( )_{16}$ (c) $(3AB)_{16} = ( )_2$ (d) $(36.125)_8 = ( )_{10}$ (e) $(324.987)_{10} = ( )_8$		5