

Enrollment No.....



Faculty of Engineering
End Sem Examination May-2023
EE3CO33 / EE3CO03 / EX3CO03
Electrical Measurement & Instrumentation

Programme: B.Tech.

Branch/Specialisation: EE/EX

Duration: 3 Hrs.**Maximum Marks: 60**

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d. Assume suitable data if necessary. Notations and symbols have their usual meaning.

- Q.1 i. An ammeter of 0-25 A range has a guaranteed accuracy of 1% of full-scale reading. The current measured is 5 A. The limiting error is- **1**
(a) 2% (b) 2.5% (c) 4% (d) 5%
- ii. A moving coil instrument has a resistance of 0.6Ω and full-scale deflection at 0.1 A. To convert it into an ammeter of 0-15 A range, the resistance of shunt should be- **1**
(a) 0.6Ω (b) 0.06Ω (c) 0.1Ω (d) 0.004Ω
- iii. In 3 phase power measurement by two wattmeter method, the reading of one wattmeter is zero. The power factor of load is- **1**
(a) 1 (b) 0.5 (c) 0 (d) 0.8
- iv. Induction type single phase energy meter measures energy in- **1**
(a) kW (b) kWh (c) Wh (d) Var
- v. What is the use of current transformer? **1**
(a) Stepping up AC current
(b) Stepping down AC current
(c) Protection and Measurement
(d) Both (b) and (c)
- vi. Kelvin's double bridge is used to measure low resistance because- **1**
(a) It has high sensitivity
(b) There is no thermoelectric emf
(c) Resistance variation due to temperature
(d) Effect of contact and lead resistances eliminated.

P.T.O.

[2]

- vii. Anderson bridge is used to measure- **1**
 (a) L (b) R (c) V (d) I
- viii. The frequency can be measured by- **1**
 (a) Wein's bridge (b) De-Sauty's Bridge
 (c) Schering's bridge (d) Anderson's bridge
- ix. Strain gauge, LVDT and thermocouple are example of- **1**
 (a) Active transducer (b) Passive transducer
 (c) Analog transducer (d) Primary transducer.
- x. Which of the following can be measured with Piezo electric crystal? **1**
 (a) Force (b) Velocity (c) Sound (d) Pressure
- Q.2 i. Explain the methods of measurement. **2**
 ii. A meter reads 127.50 V and the true value of the voltage is 127.37 V. Determine the static error and the static correction for this instrument. **3**
 iii. Explain the principle and construction of Galvanometer. **5**
- OR iv. Explain the method by which the measuring range of voltmeter is extended. **5**
- Q.3 i. Draw the circuit diagram of measurement of power by 3-wattmeter method. **2**
 ii. Explain the two-wattmeter method for measuring 3-phase power. Derive the necessary equation of power and power factor. **8**
- OR iii. Define energy. Draw and explain the well-labelled circuit diagram of measuring energy by single phase energy meter. **8**
- Q.4 i. Explain the CT saturation characteristic. **3**
 ii. Explain the working principle and construction of Megger. How the insulation resistance of 3-phase transformer is measured by Megger? **7**
- OR iii. Explain the Wheatstone Bridge method for measurement of resistance with necessary vector diagram. **7**
- Q.5 i. Define Q-factor. Draw the circuit diagram of De-Sauty's bridge. **4**
 ii. Explain the Maxwell inductance capacitance bridge. **6**
- OR iii. Explain the Anderson's bridge with necessary vector diagram. **6**

[3]

- Q.6 Attempt any two:
- i. What is the function of transducer? Explain the transducer used for measurement of temperature. **5**
- ii. Explain hall effect. Explain the photo voltaic transducer. **5**
- iii. Explain the working principle and construction of LVDT. **5**

SCHEME

End Sem Examination May-23

EE3CO33 / EE3CO03 / EX3CO03

Electrical Measurement & Instrumentation

Programme :- B.Tech.

Branch :- EE/EX

Q.1

- (i) (d) 5%
- (ii) (d) 0.004 Ω
- (iii) (b) 0.5
- (iv) (b) kWh
- (v) (d) ~~Protection & Measurement~~ Both (b) and (c) Rep
- (vi) (d) Effect of contact and lead resistance eliminated
- (vii) (a) L
- (viii) (a) Wein's bridge
- (ix) (c) Analog Transducer
- (x) (d) ~~Free~~ Pressure

Q.2

- (i) At least 2 method in short each 1 marks 2
- (ii) Static error ~~+5~~ 2 marks
Static correction 1 marks 3
- (iii) Principle - 2 marks
construction 3 marks 5

Q.3

- (i) Clear ckt diagram 2 marks 2
- (ii) Ckt diagram - 2 marks

Q.3 (iii)

Define - 1 marks
Diagram - 4 marks
Explanation - 3 marks

6

Q.4 (i)

Characteristics 1.5 marks
Explanation 1.5 marks

3

(ii)

Construction 3 marks
Principle 2 marks
How explanation 1 mark

7

(iii)

Ckt diagram - 3 marks
Vector diagram - 1 mark
Explanation with - 2 marks
derivation

7

Q.5 (i)

define - 2 marks
Descendy bridge: - 2 mark

4

(ii)

Ckt diagram - 3 marks
Explanation with - 3 marks
Derivation

6

(iii)

Ckt diagram - 2 marks
Vector diag - 2 marks
Explanation with - 2 marks
Derivation

6

Q.6

(i)

function of transducer - 2 marks
Explanation - 3 marks

5

(ii)

Hall effect explanation - 2.5 marks
Photo voltaic transducer - 2.5 marks

5

(iii)

Construction - 2.5 marks

5

Principle - 2.5 marks