



Faculty of Engineering

End Semester Examination May 2025

EC3EV01 Design for Testability

Programme	:	B.Tech.	Branch/Specialisation	:	EC
Duration	:	3 hours	Maximum Marks	:	60

Note: All questions are compulsory. Internal choices, if any, are indicated. Assume suitable data if necessary. Notations and symbols have their usual meaning.

Section 1 (Answer all question(s))					Marks	CO	BL
Q1.	If any signal line is permanently connected to Vdd power supply then it causes-				1	1	2
	<input type="radio"/> Bridge fault	<input type="radio"/> Transistor fault					
	<input type="radio"/> Delay fault	<input checked="" type="radio"/> Stuck at fault					
Q2.	Stuck open fault is a type of-				1	1	1
	<input checked="" type="radio"/> Transistor fault	<input type="radio"/> Behavioral fault					
	<input type="radio"/> Logical fault	<input type="radio"/> Power supply fault					
Q3.	D- Algorithm was developed by-				1	2	1
	<input type="radio"/> P. Goel	<input checked="" type="radio"/> Roth					
	<input type="radio"/> Fujiwara	<input type="radio"/> Cheng					
Q4.	Decisions are made only at primary inputs in _____ algorithm.				1	2	2
	<input type="radio"/> Path sensitization	<input type="radio"/> D- algorithm					
	<input checked="" type="radio"/> PODEM	<input type="radio"/> FAN					
Q5.	Time frame expansion method belongs to-				1	2	2
	<input type="radio"/> Delay fault testing	<input checked="" type="radio"/> Structural testing					
	<input type="radio"/> Power testing	<input type="radio"/> Functional testing					
Q6.	Which logic is used in sequential ATPG?				1	2	1
	<input type="radio"/> 2-valued	<input type="radio"/> 4-valued					
	<input type="radio"/> 7-valued	<input checked="" type="radio"/> 9-valued					
Q7.	Which is not an Ad-hoc technique of DFT?				1	3	2
	<input type="radio"/> Avoid asynchronous logic feedbacks	<input type="radio"/> Make flip-flops initializable					
	<input checked="" type="radio"/> Using gates with a large number of fan-in signals	<input type="radio"/> Provide test control for difficult-to-control signals					
Q8.	To make board testing convenient we use-				1	3	1
	<input checked="" type="radio"/> Boundary scan	<input type="radio"/> Ad hoc testing					
	<input type="radio"/> Exhaustive testing	<input type="radio"/> State table verification					
Q9.	BIST stands for-				1	4	1
	<input type="radio"/> Binary input sequential testing	<input type="radio"/> Binary input synchronous testing					
	<input type="radio"/> Built in sequential test	<input checked="" type="radio"/> Built in Self Test					

Q10. Testing in which circuit is partitioned in sub-circuits and then all possible input combinations are applied to each sub-circuit? 1 4 1

- ☐ Exhaustive testing
 ☒ Pseudo exhaustive testing
 ☐ Pseudo random testing
 ☐ Deterministic testing

Section 2 (Answer all question(s))

Marks CO BL

Q11. Define defect and fault for VLSI circuits.

2 1 1

Rubric	Marks
Define defect Define fault	2

Q12. Discuss various stuck at faults in detail.

3 1 2

Rubric	Marks
single stuck at 0 fault, single stuck at 1 fault, Multiple stuck at faults	3

Q13. (a) What do you mean by Bridging faults in ICs? How such faults are modelled? Explain with example.

5 1 2

Rubric	Marks
Definition, types / models, example circuits	5

(OR)

(b) Discuss Transistor faults in detail.

Rubric	Marks
Definition, Stuck open fault, Stuck on fault	5

Section 3 (Answer all question(s))

Marks CO BL

Q14. How Boolean difference is defined? Discuss various properties of it.


4 2 2

Rubric	Marks
Definition, Properties	4

Q15. (a)

Explain various steps of Path sensitization method of ATPG. Derive test vectors for given fault by using same method.


623

 

Rubric	Marks
At least 3 Steps, solution	6

(OR)

 (b) Derive test vectors for given fault using D-algorithm.



Rubric	Marks
fault activation, fault effect propagation, justification and test vecors	6

Section 4 (Answer all question(s))

Q16.

Why ATPG for sequential circuit is more difficult than combinational circuit? Justify your answer.

Marks

CO

BL

322

Rubric	Marks
1 marks for each reason	3

Q17. (a) Design a test experiment for given machine:

7 2 3


Present state	Input	
	$x = 0$	$x = 1$
A	$C, 1$	$D, 0$
B	$D, 0$	$B, 1$
C	$B, 0$	$C, 1$
D	$C, 0$	$A, 0$

Next state, output

Rubric	Marks
Synchronizing/homing sequence, Distinguishing sequence, final test sequence	7

(OR)

 - (b) Show that a test for the fault A s-a-0 in the circuit cannot be obtained using the five-valued logic of the D-calculus. Obtain a test for this fault using the nine-valued logic.



Rubric	Marks
Showing inability of 5 valued logic, solution by 9 valued logic	7

Section 5 (Answer all question(s))

Q18. Discuss controllability and observability with examples.

Marks CO BL
4 3 2

Rubric	Marks
controllability and observability , example	4

Q19. (a) Discuss level sensitive scan design in detail.

6 3 2

Rubric	Marks
Diagrams, Discussion	6

(OR)

- (b) Explain Boundary scan architecture with appropriate diagrams.

Rubric	Marks
Diagrams, Explanation	6

Section 6 (Answer all question(s))

Q20. Write some advantages of BIST.

Marks CO BL
3 4 2

Rubric	Marks
At least 3 advantages	3

Q21. (a) Discuss test pattern generation techniques for BIST. Which one is preferred mostly?

7 4 3

Rubric	Marks
At least 3 techniques: Preference	7

(OR)

(b) Write a note on BIST architecture.

Rubric	Marks
Diagrams, Discussion	7
