

Total No. of Questions: 6

Total No. of Printed Pages:3

Enrollment No.....



Faculty of Science

End Sem (Even) Examination May-2019

BC3CO06 Digital Electronics and Computer Architecture

Programme: B.Sc. (CS)

Branch/Specialisation: Computer

Science

Duration: 3 Hrs.

Maximum Marks: 60

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.

- Q.1 i. Convert $(214)_8$ into decimal: **1**
(a) $(140)_{10}$ (b) $(141)_{10}$ (c) $(142)_{10}$ (d) $(130)_{10}$
- ii. Which of the following is an invalid BCD code? **1**
(a) 0011 (b) 1101 (c) 0101 (d) 1001
- iii. The NOR gate output will be high if the two inputs are. **1**
(a) 00 (b) 01 (c) 10 (d) 11
- iv. A full adder logic circuit will have **1**
(a) Two inputs and one output
(b) Three inputs and three outputs
(c) Two inputs and two outputs
(d) Three inputs and two outputs
- v. The truth table for an S-R flip-flop has how many VALID entries? **1**
(a) 1 (b) 2 (c) 3 (d) 4
- vi. A decimal counter has _____ states. **1**
(a) 5 (b) 10 (c) 15 (d) 20
- vii. Computers invariably use RAM for **1**
(a) High complexity (b) High resolution
(c) High speed main memory (d) High flexibility
- viii. The software used to drive microprocessor-based systems is **1**
called:
(a) Assembly language (b) Firmware
(c) Machine language code (d) BASIC interpreter instructions

P.T.O.

[2]

- | | | | |
|-----|------|---|----------|
| | ix. | The instructions like MOV or ADD are called as _____ | 1 |
| | | (a) OP-Code (b) Operators (c) Commands (d) None of these | |
| | x. | Which bus is unidirectional? | 1 |
| | | (a) Data bus (b) Control bus | |
| | | (c) System bus (d) Address bus | |
| Q.2 | i. | Define ASCII (American Standard Code for Information Interchange) Code. | 2 |
| | ii. | Explain Excess3 Code and Gray Code with example. | 3 |
| | iii. | Convert $(225)_{10}$ in to hexa, binary and octal numbers. | 5 |
| OR | iv. | Solve this $112-222$ using 9s and 2s complements and 10s method. | 5 |
| Q.3 | i. | Write down any two differences between combinational and sequential circuits. | 2 |
| | ii. | Design EX-OR and EX-NOR gates using NAND gate. | 3 |
| | iii. | Solve the following expression | 5 |
| | | (a) $X.Y + X(Y + Z) + Y(Y + Z)$ | |
| | | (b) $(X + Y)(X + \bar{Y})(X + \bar{Z})$ | |
| OR | iv. | Design full subtractor using half subtractor and draw its truth table also derive the expression for difference and borrow. | 5 |
| Q.4 | i. | Design the truth table of D flip flop. | 2 |
| | ii. | What is Race around condition and how it is Eliminated? | 3 |
| | iii. | Design and explain mod-6 asynchronous Counter also draw the output waveform. | 5 |
| OR | iv. | Draw the circuit of Serial-in-serial-out and parallel-in-serial-out shift registers, also explain its working principle. | 5 |
| Q.5 | i. | Explain the Bus structures in a simple processor. | 2 |
| | ii. | Draw the basic structure of computers functional units. | 3 |
| | iii. | Defined the following terms for simple processor: | 5 |
| | | (a) RAM (b) ROM | |
| | | (c) Memory address (d) Interrupt | |
| | | (e) Addressing mode | |
| OR | iv. | Draw and explain Architecture of a simple processor. | 5 |

[3]

- | | | | |
|-----|------|--|----------|
| Q.6 | i. | What is conditional and unconditional statements explain with examples. | 2 |
| | ii. | Write down any six differences between Synchronous & Asynchronous data transfer techniques. | 3 |
| | iii. | The contents of accumulator are 6AH and register C is A7H. Write a program to add the contents of two registers and comment on the result. | 5 |
| OR | iv. | Write an assembly language program using instructions to multiply two unsigned 8 bit binary numbers using add algorithm. Also, explain working of the algorithm with an example. | 5 |

Marking Scheme

BC3CO06 Digital Electronics and Computer Architecture

Q.1	i.	Convert $(214)_8$ into decimal: (a) $(140)_{10}$	1
	ii.	Which of the following is an invalid BCD code? (b) 1101	1
	iii.	The NOR gate output will be high if the two inputs are. (a) 00	1
	iv.	A full adder logic circuit will have (d) Three inputs and two outputs	1
	v.	The truth table for an S-R flip-flop has how many VALID entries? (c) 3	1
	vi.	A decimal counter has _____ states. (b) 10	1
	vii.	Computers invariably use RAM for (c) High speed main memory	1
	viii.	The software used to drive microprocessor-based systems is called: (a) Assembly language	1
	ix.	The instructions like MOV or ADD are called as _____ (a) OP-Code	1
	x.	Which bus is unidirectional? (d) Address bus	1
Q.2	i.	American Standard Code for Information Interchange Code.	2
	ii.	Excess3 Code with example 1.5 marks Gray Code with example 1.5 marks	3
	iii.	Convert $(225)_{10}$ in to hexa, octal numbers. 4 marks Convert $(225)_{10}$ in to binary 1 mark	5
OR	iv.	112-222 using 9s and 10s method 4 marks Solve this 112-222 using 2s complements 1 mark	5
Q.3	i.	Any two differences b/w combinational and sequential circuits. 1 mark for each points (1 mark * 2)	2
	ii.	EX-OR gates using NAND gate. 1.5 marks EX-NOR gates using NAND gate 1.5 marks	3
	iii.	Solve the following expression	5

OR	iv.	(a) $X.Y + X(Y + Z) + Y(Y + Z)$ 2.5 marks (b) $(X + Y)(X + \bar{Y})(X + \bar{Z})$ 2.5 marks	5
		Design full subtractor using half subtractor 2 marks Its truth table 1 marks Derive the expression for difference and borrow. 2 marks	
Q.4	i.	Truth table of D flip flop.	2
	ii.	Race around condition 2 marks How it is Eliminated 1 mark	3
	iii.	Design mod-6 asynchronous Counter 1 mark Explanation mod-6 asynchronous Counter 2 marks Output waveform 2 marks	5
OR	iv.	Circuit of Serial-in-serial-out shift registers and working principle 2.5 marks Circuit of Parallel-in-serial-out shift registers and working principle. 2.5 marks	5
Q.5	i.	Bus structures in a simple processor.	2
	ii.	Basic structure of computers functional units.	3
	iii.	Defined the terms for simple processor: 1 mark for each (1 mark * 5)	5
OR	iv.	Architecture of a simple processor diagram 2 marks Explanation Architecture of a simple processor 3 marks	5
Q.6	i.	Conditional statements with examples 1 mark Unconditional statements with examples 1 mark	2
	ii.	Any six differences between Synchronous & Asynchronous data transfer techniques. 0.5 mark for each difference (0.5 mark * 6)	3
	iii.	Program to add the contents of two registers and comment on the result.	5
OR	iv.	Write an assembly language program and working of the algorithm with an example.	5
