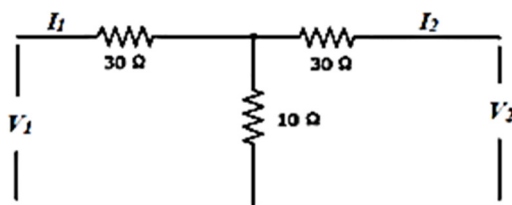


[4]


- iii. With the help of frequency response curves, give the classification of passive filters. 5

Q.5 Attempt any two:


- i. For the symmetrical two port network shown in the given figure, find the Z parameters and ABCD parameters. 5



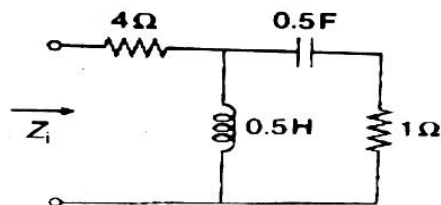- ii. Calculate the driving point impedance $Z(s)$ of the network shown in the given figure. Plot the poles and zeros of the driving point impedance function on the s-plane. 5



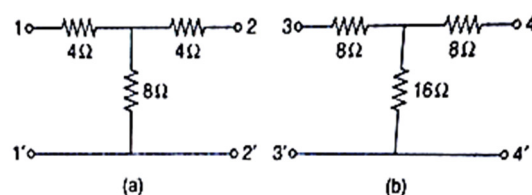- iii. Two networks shown in given figure are connected in series. Determine the Z-parameters of the cascaded network. 5



Q.6 Attempt any two:

- i. What are the properties of a positive real function? Explain the procedure of testing of positive real function. 5
- ii. Explain how one port R-L network can be synthesised using Foster form -I, Cauer form -I method. 5
- iii. Test whether the following polynomial is Hurwitz or not- 5

$$F(s) = \frac{2s^4 + 6s^3 + 11s^2 + 10s + 5}{s^4 + 5s^3 + 8s^2 + 9s + 6}$$

Total No. of Questions: 6

Total No. of Printed Pages: 4

Enrollment No.....



Faculty of Engineering
End Sem Examination Dec-2023
EE3CO49 Electrical Circuit Analysis

Programme: B.Tech.

Branch/Specialisation: EE

Duration: 3 Hrs.

Maximum Marks: 60


Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d. Assume suitable data if necessary. Notations and symbols have their usual meaning.

- Q.1 i. If there are “b” branches and “n” nodes, the number of tie set equations given by- 1
(a) b (b) n-1 (c) b-n+1 (d) b+n+1
- ii. The “sharpness” of the resonance in a resonant circuit is measured quantitatively by- 1
(a) Bandwidth (b) Quality factor
(c) Resonant frequency (d) None of these
- iii. Which of the following theorems enables a number of sources to be combined directly into a single source: 1
(a) Compensation theorem (b) Reciprocity theorem
(c) Superposition theorem (d) Millman’s theorem
- iv. In a linear system, several sources acting simultaneously produce an effect which is the sum of the separate effects caused by individual sources acting at a time. This is- 1
(a) Thevenin theorem (b) Norton’s theorem
(c) Reciprocity theorem (d) Superposition theorem
- v. In the passive bandpass filter, the shunt element is- 1
(a) Capacitive
(b) Inductive
(c) Series combination of L & C
(d) Parallel combination of L & C
- vi. If a capacitor is energized by a symmetrical square wave current source, then the steady state voltage across the capacitor will be – 1
(a) Square wave (b) Triangular wave
(c) Step Function (d) Impulse function


[2]

- vii. When the two 2-port networks are connected in parallel, it is convenient to use- **1**
 (a) Z parameter (b) h parameter
 (c) ABCD parameter (d) Y parameter
- viii. When the two 2-port networks are connected in cascade, it is convenient to use- **1**
 (a) Z parameter (b) h parameter
 (c) ABCD parameter (d) Y parameter
- ix. Foster Form-I is defined only for- **1**
 (a) Admittance function (b) Impedance functions
 (c) Both (a) and (b) (d) None of these
- x. The poles and zeros of a positive real function cannot have- **1**
 (a) Negative real parts (b) Positive real part
 (c) Imaginary part (d) None of these

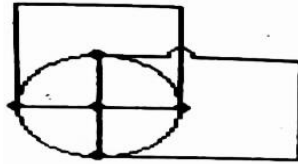- Q.2 i. Count the number of branches and nodes in the following graph: **2**




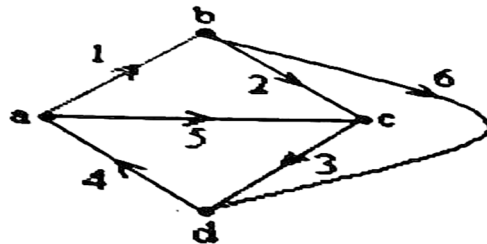- ii. Draw the incidence matrix of the following graph - **3**



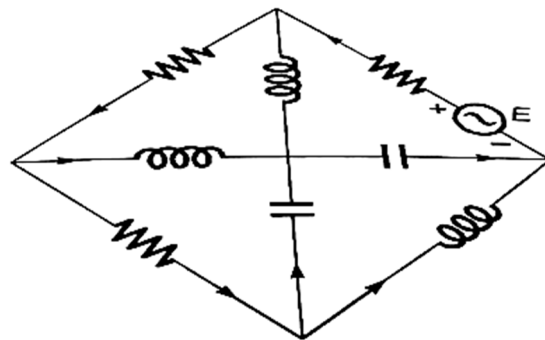- iii. In a parallel RLC circuit tuned to frequency $f_0 = 10^6$ Hz and Bandwidth = 10 KHz. Given that $L = 50 \mu\text{H}$. Find (a) Q Factor **5**
 (b) Capacitance at f_0 and (c) Resistance

- OR iv. Develop tie-set schedule of the network shown below: **5**




[3]


Q.3

Attempt any two:

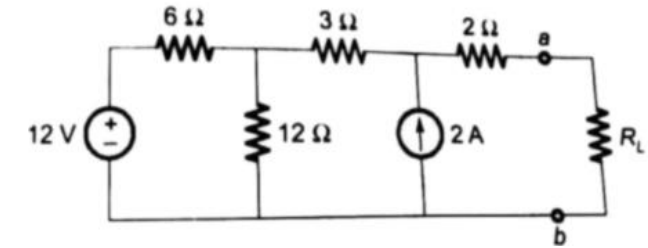
- i. Find the value of R_L for maximum power transfer in the circuit of given figure. Find the maximum power. **5**



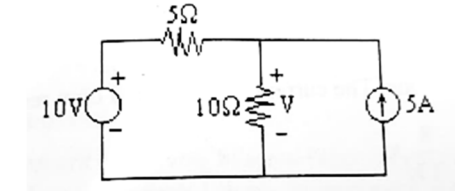- ii. Calculate the voltage V in the given circuit shown below using superposition theorem. **5**



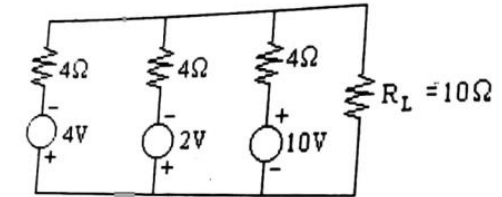
- iii. Using Millman's theorem, find the current through load R_L in the circuit shown in figure given below. Also find the voltage drop across R_L ? **5**



Q.4

Attempt any two:

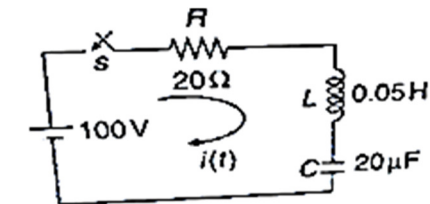- i. The circuit shown in the given figure consists of R, L, and C in series with a 100 V constant source. When the switch is closed at $t=0$, find the transient current. **5**



- ii. For the given circuit, find the complete solution for current $i(t)$ using Laplace transformation when the switch is closed. Assume zero charge across the capacitor before switching. **5**

