

Enrollment No.....



Faculty of Engineering
End Sem Examination May-2024

EC3CO17 Linear Integrated Circuits & Applications

Programme: B.Tech.

Branch/Specialisation: EC


Duration: 3 Hrs.**Maximum Marks: 60**

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d. Assume suitable data if necessary. Notations and symbols have their usual meaning.

- Q.1 i. Which of the following electrical characteristics is not exhibited by an ideal op-amp? **1**

- (a) Infinite voltage gain (b) Infinite bandwidth
(c) Infinite output resistance (d) Infinite slew rate

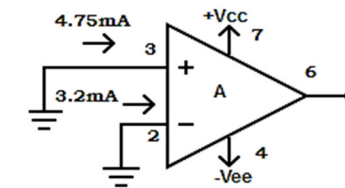- ii. Calculate the input offset current from the circuit shown below: **1**



- (a) +1.55mA (b) $\pm 1.55\text{mA}$
(c) -1.55mA (d) None of these

- iii. Define the input resistance with feedback for voltage series feedback amplifier- **1**

- (a) $R_{IF} = R(1-AB)$ (b) $R_{IF} = R(AB-1)$
(c) $R_{IF} = R(1+AB)$ (d) None of these

- iv. Find out the gain value by which each input of the averaging amplifier is amplified? (Assume there are four inputs) **1**


- (a) 0.5 (b) 0.25 (c) 1 (d) 2

- v. Match the gain of the filter with the frequencies in the low pass filter- **1**

- | Frequency | Gain of the filter |
|--------------------|-----------------------------------|
| 1. $f < f_H$ | i. $V_O/V_{in} \cong AF/\sqrt{2}$ |
| 2. $f = f_H$ | ii. $V_O/V_{in} \leq AF$ |
| 3. $f > f_H$ | iii. $V_O/V_{in} \cong AF$ |
| (a) 1-i,2-ii,3-iii | (b) 1-ii,2-iii,3-i |
| (c) 1-iii,2-ii,3-i | (d) 1-iii,2-i,3-ii |

[2]

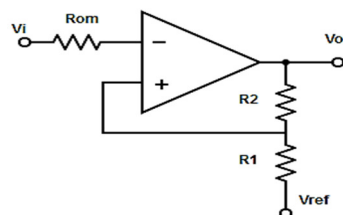- vi. Find the roll-off rate for 8th order low pass filter- 1
 (a) -160dB/decade (b) -320dB/decade
 (c) -480dB/decade (d) -200dB/decade
- vii. Determine the time period of a monostable 555 multivibrator- 1
 (a) $T = 0.33RC$ (b) $T = 1.1RC$
 (c) $T = 3RC$ (d) $T = RC$
- viii. Calculate the hysteresis voltage for the schmitt trigger from the 1
 given specification:
 $R_2 = 56k\Omega$, $R_1 = 100\Omega$, $V_{ref} = 0V$ & $V_{sat} = \pm 14V$.




- (a) 0 mV (b) 25 mV (c) 50 mV (d) -25 mV
- ix. The 7812 regulator IC provides- 1
 (a) 5V (b) -5V (c) 12V (d) -12V
- x. Which is not considered as a linear voltage regulator? 1
 (a) Fixed output voltage regulator
 (b) Adjustable output voltage regulator
 (c) Switching regulator
 (d) Special regulator

- Q.2 i. What is Op-Amp? 2
 ii. Design an inverting amplifier with gain of -5 and an input resistance of 10K Ω . 3
 iii. Define following electrical parameters of Op-Amp: Input offset voltage, CMRR, Output Voltage Swing, slew rate and SVRR. 5
- OR iv. List and explain the function of all the basic building block of an Op-Amp. 5

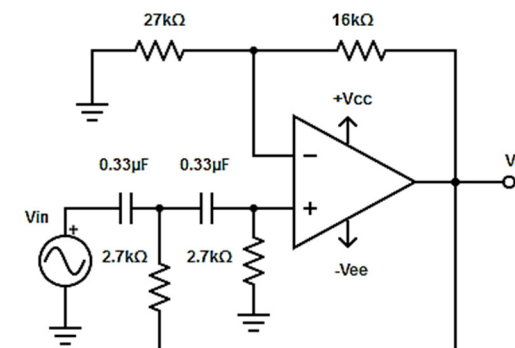
- Q.3 i. What is feedback? List two types of feedback. Which type is used in linear application? 2
 ii. Draw circuit diagram of an integrator, explain its working, derive the expression of output and draw the output waveform for square wave input. 3
 iii. What is instrumentation amplifier? Draw its circuit diagram and derive the expression of output also write its applications. 5

[3]

- OR iv. Draw and explain the circuit diagram of phase shift oscillator, and also design it for output frequency of 200Hz. 5
- Q.4 i. Define Filter. How are filter classified? 2
 ii. What are the advantages of active filters over passive filters? 3
 iii. Design a first order low pass butterworth filter so that it has a cut off frequency of 1.6KHz and a pass band gain of 2. 5
- OR iv. Consider the following filter circuit and calculate the low cut-off frequency value and draw the frequency response of filter. 5



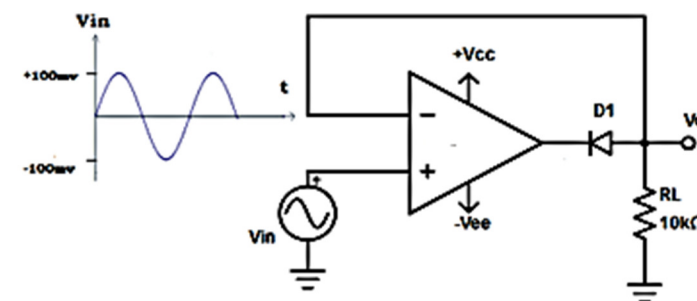- Q.5 i. Draw and explain the functional diagram of a 555 timer. 4
 ii. Identify the circuit given below, explain its working and determine the output waveform for the given sinusoidal input. 6



- OR iii. What is peak detector draw its circuit diagram and explain its working with input output wave forms. 6

- Q.6 Attempt any two: 5
 i. What is switching regulator? List major component of switching regulator and explain their working. 5
 ii. Write short note on SMPS. 5
 iii. What is fixed and adjustable voltage regulator list the advantage of adjustable voltage regulator over fixed voltage regulator. 5

Marking Scheme

Linear Integrated Circuits & Applications (T) - EC3CO17 (T)

Q.1	i)	c. Infinite output resistance		1
	ii)	a. +1.55mA		1
	iii)	c. $R_{IF} = R(1+AB)$		1
	iv)	b. 0.25		1
	v)	d. 1-iii,2-i,3-ii		1
	vi)	a. -160dB/decade		1
	vii)	b. $T = 1.1RC$		1
	viii)	c. 50 mv		1
	ix)	c. 12V		1
	x)	c. Switching regulator		1
Q.2	i.	Definition-	2 Marks	2
	ii.	Circuit Diagram-	1 Marks	3
		Formula Derivation-	1 Marks	
		For R_f Value-	1 Marks	
OR	iii.	Each Parameter Defining-	1*5= 5 Marks	5
	iv.	Block Diagram-	2 Marks	5
		Explanations-	3 Marks	
Q.3	i.	Definition of feedback-	1 Marks	2
		Types of feedback-	0.5 Marks	
		Which feedback used in linear application-	0.5 Marks	
	ii.	Circuit Diagram-	0.5 Marks	3
		Working-	0.5 Marks	
		Expression derivation-	1 Marks	
OR	iii.	Input out waveform-	1 Marks	
		defining instrumentation amplifier-	0.5 Marks	5
		circuit diagram-	2 Marks	
		expression of output-	2 Marks	
Q.4	i.	Defining Filter-	1 Marks	2
		Filter classification	1 Marks	
	ii.	Circuit diagram	2 Marks	5
		Frequency Response	1 Marks	
		Finding the value of components according to the given value of cut off frequency and pass band gain-	2 Marks	

OR	iii.	Cut off frequency derivation- Frequency response-	3 Marks 2 Marks	5
Q.5	i.	Diagram- Explanation -	2 Marks 2 Marks	4
	ii.	Identification of circuit - Working Explanation- output waveform -	1 Marks 3 Marks 2 Marks	6
OR	iii.	What is peak detector- circuit diagram - working- Input output wave forms	1 Marks 2 Marks 2 Marks 1 Marks	6
Q.6				
	i.	What is switching regulator- List major component- Working-	2 Marks 1 Marks 2 Marks	5
	ii.	Circuit diagram- Explanation	2 Marks 3 Marks	5
	iii.	What is fixed and adjustable voltage regulator - advantage -	3 Marks 2 Marks	5
