

Enrollment No.....



Faculty of Engineering

End Sem Examination May-2023

EE3CO42 / EE3CO02 / EX3CO02 Power Electronics

Power Electronics Devices & Circuits

Programme: B.Tech.

Branch/Specialisation: EE/EX

Duration: 3 Hrs.**Maximum Marks: 60**

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d. Assume suitable data if necessary. Notations and symbols have their usual meaning.

- Q.1 i. An SCR is a- 1
 (a) 4-layer, 3-junction devices (b) 4-layer, 4-junction devices
 (c) 4-layer, 2-junction devices (d) 3-layer, single junction device
- ii. The GTO can be turned off- 1
 (a) By positive gate pulse
 (b) By a negative gate pulse
 (c) By negative anode-cathode voltage
 (d) By removing the gate pulse
- iii. In a three-phase half wave 6-pulse mid-point type diode rectifier, each diode conducts for 1
 (a) 120° (b) 60° (c) 90° (d) 180°
- iv. A single-phase full converter with B-2 type of connection has a continuous load current waveform. The thyristor pairs T3, T4 is triggered at $\omega t =$ _____. 1
 (a) 0 (b) α (c) $\pi + \alpha$ (d) $\pi - \alpha$
- v. Inverters converts- 1
 (a) DC power to DC power (b) DC power to AC power
 (c) AC power to AC power (d) AC power to DC power
- vi. The output voltage from a single-phase full wave bridge inverter varies from- 1
 (a) V_s to $-V_s$ (b) V_s to zero
 (c) $V_s/2$ to zero (d) $-V_s/2$ to $V_s/2$
- vii. Which device can be used in a chopper circuit? 1
 (a) BJT (b) MOSFET (c) GTO (d) All of these

P.T.O.

[2]

- viii. What is the duty cycle of a chopper? **1**
 (a) T_{on}/T_{off} (b) T_{on}/T (c) T/T_{on} (d) $T_{off} \times T_{on}$
- ix. AC voltage controllers convert- **1**
 (a) Fixed AC to fixed DC (b) Variable AC to variable DC
 (c) Fixed AC to variable AC (d) Variable AC to fixed AC
- x. Applications of cyclo-converters include- **1**
 (a) Speed control of ac drives (b) Induction heating
 (c) Static VAR compensation (d) All of these
- Q.2 i. Define latching and holding currents as applicable to an SCR. **2**
 ii. Draw & explain V-I characteristics of SCR. **3**
 iii. Describe GTO with the help of symbol and characteristics. Give the merits and demerits of a GTO as compared to SCR. **5**
- OR iv. Draw and explain UJT firing circuit with the help of its waveform. **5**
- Q.3 i. A single-phase half wave-controlled rectifier with R load is fed from a 220V, 50Hz AC supply. When $R=10\Omega$ and $\alpha=45^\circ$, determine average DC output voltage and current. **4**
 ii. Draw & explain full wave B-2 converter in rectifying mode with suitable circuit diagram and relevant waveforms also calculate V_{dc} & V_{rms} value. **6**
- OR iii. Draw & explain circuit diagram and its relevant waveform of symmetrical & asymmetrical half-controlled converter with RL load at $\alpha=30^\circ$. **6**
- Q.4 i. What is pulse width modulation? List the various PWM techniques. **4**
 ii. Discuss the principle of working of a three-phase bridge inverter with appropriate circuit diagram. Draw line and phase voltage waveforms on the assumption that each thyristor conducts for 180° and resistive load is star connected. **6**
- OR iii. Describe the working of a series inverter with appropriate circuit diagram and waveforms. **6**
- Q.5 i. Define chopper. What are the types of choppers? What are the applications of chopper circuit? **4**
 ii. Explain the operating principle of DC chopper with a suitable diagram. Draw the voltage and current waveform of chopper. **6**
- OR iii. A step-down chopper has a load resistance of 20Ω and input DC voltage is 200V. When the chopper switch is ON, the voltage across

[3]

- semiconductor is 2 V. If the switching frequency is 1.5kHz and duty ratio is 40%, determine (a) average DC output voltage (b) rms output voltage (c) efficiency.
- Q.6 i. What is an AC voltage controller? List some of its industrial applications. Enumerate its merits and demerits. **4**
 ii. What is cyclo-converter? What are the types of cyclo-converter? What are the advantage and application of cyclo-converter? **6**
- OR iii. Discuss the operating principle of single phase to single phase step down cycloconverter using bridge converter. Mention the conduction of various thyristor in the waveform. **6**

[1]
Marking Scheme

EE3CO42 Power Electronics

EE3CO02-EX3CO02 Power Electronics Devices & Circuits

Q.1	i)	a) 4-layer, 3-junction device	1
	ii)	b) by a negative gate pulse	1
	iii)	b) 60°	1
	iv)	c) $\pi + \alpha$	1
	v)	b) dc power to ac power	1
	vi)	a) V_s to $-V_s$	1
	vii)	d) All of the mentioned	1
	viii)	b) T_{on}/T	1
	ix)	c) fixed ac to variable ac	1
	x)	d) all of the mentioned	1
Q.2	i.	Define latching and holding currents as applicable to an SCR.	1
	ii.	Draw & explain V-I characteristics of SCR?	1
	iii.	Describe GTO with the help of symbol and characteristics.	2
		Give the merits and demerits of a GTO as compared to SCR.	1
			1
OR	iv.	Draw and explain UJT firing circuit with the help of its waveform?	2
			2
			1
Q.3	i.	A single-phase half wave-controlled rectifier with R load is fed from a 220V, 50Hz AC supply. When $R=10\Omega$ and $\alpha=45^\circ$, determine average DC output voltage and current.	2
		$V_o=84.56V$, $I_o=8.456A$.	2
	ii.	Draw & explain full wave B-2 converter in rectifying mode with suitable circuit diagram and relevant waveforms also	3
		calculate V_{dc} & V_{rms} value?	2
			1
OR	iii.	Draw & explain circuit diagram and its relevant waveform of symmetrical & asymmetrical half-controlled converter with RL load at $\alpha=30^\circ$.	4
			2

[2]

Q.4	i.	What is pulse width modulation? List the various PWM techniques.	2
			2
	ii.	Discuss the principle of working of a three-phase bridge inverter with appropriate circuit diagram. Draw line and phase voltage waveforms on the assumption that each thyristor conducts for 180° and resistive load is star connected.	3
OR	iii.	Describe the working of a series inverter with appropriate circuit, waveform	3
			4,2
Q.5	i.	Define chopper. What are the types of choppers? What are the applications of chopper circuit?	1
			2
			1
	ii.	Explain the operating principle of DC chopper with a suitable diagram. Draw the voltage and current waveform of chopper.	4
			2
OR	iii.	A step-down chopper has a load resistance of 20Ω and input DC voltage is 200V. When the chopper switch is ON, the voltage across semiconductor is 2 V. If the switching frequency is 1.5kHz and duty ratio is 40%, determine (a) average DC output voltage (b) rms output voltage (c) efficiency.	2*3=6
Q.6	i.	What is an AC voltage controller? List some of its industrial applications. Enumerate its merits and demerits.	2
			1
			1
	ii.	What is cycloconverter? What are the types of cycloconverter? What are the advantage and application of cycloconverter?	2*3=6
OR	iii.	Discuss the operating principle of single phase to single phase step down cycloconverter using bridge converter. Mention the conduction of various thyristor in the waveform.	4
			2