

Enrollment No.....



Faculty of Engineering
End Sem Examination Dec 2024
OE00003 Industrial Electronics

Programme: B.Tech.

Branch/Specialisation: All

Duration: 3 Hrs.**Maximum Marks: 60**

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d. Assume suitable data if necessary. Notations and symbols have their usual meaning.

		Marks	BL	PO	CO	PSO
Q.1	i. Silicon controlled rectifier can be turned on.....	1	1	1	1	
	(a) By applying a gate pulse and turned off only when current becomes zero					
	(b) Turned off by applying gate pulse					
	(c) By applying a gate pulse and turned off by removing the gate pulse					
	(d) By making current negative and turned off by making current zero					
	ii. The power MOSFET device is a.....	1	1	1	1	
	(a) Current controlled unipolar device					
	(b) Voltage controlled unipolar device					
	(c) Current controlled bipolar device					
	(d) Voltage controlled bipolar device					
	iii. The most suited gate pulses given to the AC regulator with R-L load can be in the form of.....	1	1	1	2	
	(a) Continuous signal					
	(b) Large isolating pulse transformer					
	(c) A train of pulses					
	(d) None of these					
	iv. Latching current is important for.....	1	1	1	2	
	(a) SCR turn on					
	(b) SCR turn off					
	(c) Both (a) and (b)					
	(d) None of these					
	v. A chopper may be thought as a-	1	1	1	3	

[2]

	(a) Inverter with dc input				
	(b) DC equivalent of an ac transformer				
	(c) Diode rectifier				
	(d) DC equivalent of induction motor				
vi.	Which device can be used in chopper circuit?	1	1	1	3
	(a) BJT				
	(b) MOSFET				
	(c) GTO				
	(d) All of these				
vii.	The ac output voltage waveform of VSI and AC output current waveform of CSI respectively is composed of-	1	1	1	4
	(a) High dv/dt, low di/dt				
	(b) Low dv/dt, low di/dt				
	(c) Low dv/dt, high di/dt				
	(d) High dv/dt, high di/dt				
viii.	Single phase VSI are mainly used in-	1	1	1	4
	(a) Power supplies				
	(b) UPS				
	(c) Multilevel configuration				
	(d) All of these				
ix.	A cycloconverter is a-	1	1	1	5
	(a) One stage power converter				
	(b) One stage voltage converter				
	(c) One stage frequency converter				
	(d) None of these				
x.	AC voltage controllers convert-	1	1	1	5
	(a) Fixed ac to fixed dc				
	(b) Variable ac to variable dc				
	(c) Fixed ac to variable ac				
	(d) Variable ac to fixed ac				
Q.2	i. Write different applications of DIAC.	2	1	1	1
	ii. What is power diode? Enlist different use of power diode.	3	1	1	1
	iii. Draw and explain V-I characteristic of SCR.	5	2	1	1
OR	iv. Explain two transistor analogy of thyristor.	5	2	1	1
Q.3	i. Explain the characteristic of UJT.	3	1	1	2

[3]

	ii. Draw the waveform of phase-controlled rectifier (half wave) with RLE load and explain it's working.	7	2	1	2
OR	iii. How SCR turn off? Discuss any one commutation technique to turn off SCR.	7	2	1	2
Q.4	i. Write the basic principle of chopper.	3	1	1	3
	ii. Describe the working of buck converter and boost converter.	7	2	2	3
OR	iii. Discuss the working of class B chopper with neat diagram.	7	2	2	3
Q.5	i. Compare current source inverter and voltage source inverter.	4	1	2	4
	ii. Explain working of PWM inverter with neat diagram.	6	2	2	4
OR	iii. Draw and explain full bridge inverter.	6	2	2	4
Q.6	Attempt any two:				
	i. Write any three industrial applications of cycloconverter.	3	1	1	5
	ii. Describe the working of cycloconverter with neat diagram.	7	2	2	5
OR	iii. What is ac voltage controller? Discuss its industrial application.	7	1	2	5

Marking Scheme
OE00003 (T) Industrial Electronics (T)

Q.1	i)	(a) by applying a gate pulse and turned off only when current becomes zero	1
	ii)	(b) voltage controlled unipolar device	1
	iii)	(c) a train of pulses	1
	iv)	(a) SCR turn on	1
	v)	(b) dc equivalent of an ac transformer	1
	vi)	(d) All the mentioned	1
	vii)	(d) high dv/dt, high di/dt	1
	viii)	(d) all of these	1
	ix)	(c) one stage frequency converter	1
	x)	c) fixed ac to variable ac	1

Q.2	i.	Two applications	2
	ii.	power diode -1-mark, power diode uses- 2 marks	3
	iii.	Draw-2 marks, explain- 3 marks	5
OR	iv.	Explain with diagram- 5 marks	5

Q.3	i.	characteristic- 3 marks	3
	ii.	Draw-3 marks, working -4 marks	7
OR	iii.	SCR turn off- 3 marks, one commutation technique- 4 marks	7

Q.4	i.	Principle- 3 marks	3
-----	----	--------------------	---

	ii.	3.5 marks each	7
OR	iii.	Diagram- 3marks, working- 4 marks	7
Q.5	i.	Compare four point- 4 marks	4
	ii.	Diagram- 2marks, working- 4 marks	6
OR	iii.	Draw- 2 marks, explain-4 marks	6
Q.6			
	i.	Each 1 mark	3
	ii.	Diagram- 3marks, working- 4 marks	7
	iii.	ac voltage controller-5 marks, application- 2 marks	7
