

[4]

- iii. Draw and explain the circuit diagram of a half wave rectifier. Explain its working and disadvantages as compare to full wave rectifier. **5**
- OR iv. Draw the typical output characteristics of a p-n-p transistor in CB configuration. Label all variable and indicate active, cut-off and saturation region. **5**
- Q.6 i. State and explain De-Morgan's theorem. **2**
- ii. Convert the following numbers into the respective index given: **3**
- (a) $(1101011010.101)_2 = (\quad)_{16}$
- (b) $(35.726)_{10} = (\quad)_{16}$
- (c) $(206)_8 = (\quad)_{10}$
- iii. Draw and explain full adder with its truth table. Derive the logic expression for sum and carry. **5**
- OR iv. Explain universal gates and implementation of AND gates using universal gates. **5**

Total No. of Questions: 6

Total No. of Printed Pages:4

Enrollment No.....



Faculty of Engineering
End Sem (Odd) Examination Dec-2019
EN3ES04 Basic Electrical and Electronics Engineering
Programme: B.Tech. Branch/Specialisation: All

Duration: 3 Hrs.

Maximum Marks: 60

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.

- Q.1 i. An ideal voltage source has internal resistance **1**
- (a) Zero ohm (b) 10 ohm (c) 3.33 ohm (d) Infinite
- ii. The circuit whose properties are same in either direction is known as **1**
- (a) Unilateral circuit (b) Bilateral circuit
- (c) Irreversible circuit (d) Reversible circuit
- iii. Power factor of a series RL circuit is **1**
- (a) Leading (b) Lagging (c) Unity (d) None of these
- iv. What happens to the MMF when the magnetic flux decreases? **1**
- (a) Increases (b) Decreases
- (c) Remains constant (d) Becomes zero
- v. Open circuit test is performed to determine **1**
- (a) Core losses (b) Copper losses
- (c) Temperature rise (d) None of these
- vi. Which of the following rule is used to determine the direction of rotation of D.C. motor? **1**
- (a) Coulomb's Law
- (b) Lenz's Law
- (c) Fleming's Right-hand Rule
- (d) Fleming's Left-hand Rule
- vii. If the PIV rating of a diode is exceeded, **1**
- (a) The diode conducts poorly
- (b) The diode is destroyed
- (c) The diode behaves like a zener diode
- (d) None of these

P.T.O.

[2]

- viii. The emitter of a transistor is 1
 (a) Lightly doped (b) Highly doped
 (c) Moderately doped (d) Not doped at all
- ix. 2's complement of 11001011 is 1
 (a) 01010111 (b) 11010100 (c) 00110101 (d) 11100010
- x. How many AND, OR and EXOR gates are required for the 1
 configuration of full adder?
 (a) 1, 2, 2 (b) 2, 1, 2 (c) 3, 1, 2 (d) 4, 0, 1

- Q.2 i. Define and explain active and passive elements. 2
 ii. State and explain Thevenin's theorem as applicable to electrical 3
 circuit.
 iii. Calculate the current in each branch of the network shown in Fig.1 5
 using mesh current method.

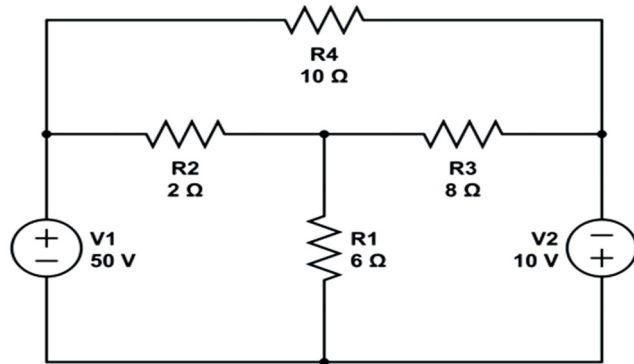


Fig. 1

- OR iv. Use superposition theorem to find current (I) in the network given in 5
 Fig.2

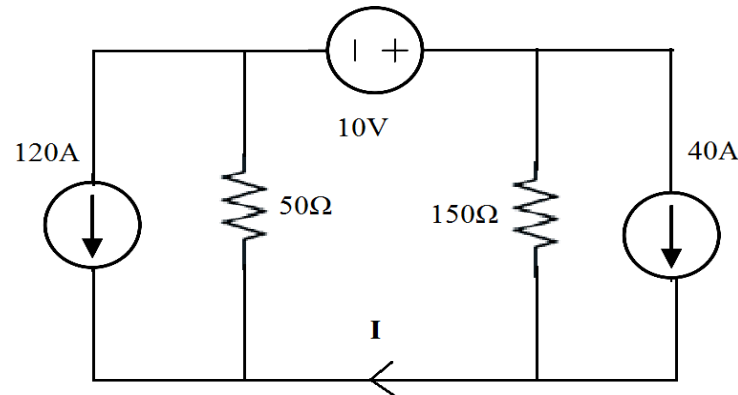


Fig. 2

[3]

- Q.3 i. Compare the magnetic circuit with electric circuit in tabular form. 2
 ii. Define the following terms: 3
 (a) Flux (b) mmf
 (c) Flux density (d) Permeability
 (e) rms value (f) Form factor
- iii. A series circuit has $R=10\Omega$, $L=50\text{mh}$, and $C=100\mu\text{f}$ and is supplied 5
 with 200V, 50Hz. Find:
 (a) Impedance (b) Current
 (c) Active power (d) Power factor
 (e) Voltage drops across capacitance.
- OR iv. A series R-C circuit takes a power of 7kW when connected to 200V, 5
 50Hz supply. The voltage across the resistor is 130V. Calculate:
 (a) Resistance (b) Current
 (c) Power factor (d) Capacitance
 (e) Impedance.
- Q.4 i. Why rotor of a three phase induction motor does not rotate with 2
 synchronous speed?
 ii. What are the different losses in a transformer? Distinguish between 3
 constant losses and variable losses.
 iii. Draw and explain phasor diagram of single phase transformer at 5
 leading power factor load.
- OR iv. A 5kVA, 400/200V, 50Hz. Single phase transformer gave the 5
 following results during no load and short circuit test.
 No load: 400V, 1A, 60W (HV side)
 Short-circuit: 15V, 12.5A, 50W (HV side)
 Calculate:
 (a) No load parameters
 (b) Short-circuit parameters
 (c) Full load efficiency at 0.8 p.f. lagging
 (d) Regulation at full load and 0.8 p.f. lagging
 (e) Iron and copper loss at full load
- Q.5 i. Explain zener diode as a voltage regulator. 2
 ii. Draw and explain voltage-current characteristics of P-N diode. 3

P.T.O.

Marking Scheme

EN3ES04 Basic Electrical and Electronics Engineering

Q.1	i.	An ideal voltage source has internal resistance (a) Zero ohm	1	OR	iv.	with 200V, 50Hz. Find: 1 mark for each (1 mark * 5)	5		
	ii.	The circuit whose properties are same in either direction is known as (b) Bilateral circuit	1		iv.	A series R-C circuit takes a power of 7kW when connected to 200V, 50Hz supply. The voltage across the resistor is 130V. Calculate: 1 mark for each (1 mark * 5)			
	iii.	Power factor of a series RL circuit is (b) Lagging	1						
	iv.	What happens to the MMF when the magnetic flux decreases? (b) Decreases	1						
	v.	Open circuit test is performed to determine (a) Core losses	1	Q.4	i.	Why rotor of a three phase induction motor does not rotate with synchronous speed	2		
	vi.	Which of the following rule is used to determine the direction of rotation of D.C. motor? (d) Fleming's Left-hand Rule	1		ii.	Different losses in a transformer Distinguish b/w constant losses and variable losses	2 marks 1 mark	3	
	vii.	If the PIV rating of a diode is exceeded, (b) The diode is destroyed	1		iii.	Phasor diagram of single phase transformer at leading power factor load. Drawing Explanation	3 marks 2 marks	5	
	viii.	The emitter of a transistor is (b) Highly doped	1		OR	iv.	Single phase transformer gave the following results during no load and short circuit test. Calculate: 1 mark for each (1 mark * 5)	5	
	ix.	2's complement of 11001011 is _____ (c) 00110101	1						
	x.	How many AND, OR and EXOR gates are required for the configuration of full adder? (b) 2, 1, 2	1		Q.5	i.	Zener diode as a voltage regulator.	2	
Q.2	i.	Definition of active elements Definition of passive elements	1 mark 1 mark	2		ii.	Voltage-current characteristics of P-N diode Drawing Explanation	1 mark 2 marks	3
	ii.	Thevenin's theorem as applicable to electrical circuit Statement Explanation	1 mark 2 marks	OR		iv.	Typical output characteristics of a p-n-p transistor in CB configuration. Diagram Explanation Label all variable and indicate active, cut-off and saturation region	1 mark 2 marks 2 marks	5
	iii.	Calculate the current in each branch of the network shown Mesh current Branch current	3 marks 2 marks						
	OR	iv.	Use superposition theorem to find current (I) in the network 1.5 mark for each response (1.5 marks * 3) For sum		4.5 marks 0.5 mark	Q.6	i.	De-Morgan's theorem. Statement Explanation	1 mark 1 mark
Q.3	i.	Compare the magnetic circuit with electric circuit in tabular form. 0.5 mark for each point (0.5 mark *4)	2		ii.		Convert the following numbers into the respective index given: 1 mark for each (1 mark * 3)	3	

OR	iii.	Full adder with its truth table		5
		Diagram	1 mark	
		Explanation	2 marks	
		Derivation the logic expression for sum and carry	2 marks	
	iv.	Explanation of universal gates	3 marks	5
		Implementation of AND gates	2 marks	
