

[4]

- iii. Explain H-parameter model for CC- amplifier with diagram? Also derive expression of input and output impedance for it. **5**
- OR iv. What are the advantages of class B push-pull amplifier? Also discuss circuit arrangement and working of the same with neat diagram. **5**
- Q.6 i. What is transfer gain of an amplifier with and without (negative) feedback? **2**
- ii. What are advantages of negative feedback amplifier? Calculate the gain of a negative feedback amplifier with an internal gain  $A_v=65$  and feedback fraction  $m_v=1/13$  and what will be the gain when  $A_v$  doubles? **3**
- iii. Compare positive and negative feedback? Derive formula for output impedance of current shunt feedback and current series feedback. **5**
- OR iv. Explain circuit arrangement and working of phase shift oscillator using NPN transistor with neat diagram. **5**

\*\*\*\*\*

Total No. of Questions: 6

Total No. of Printed Pages:4

Enrollment No.....



Faculty of Engineering  
End Sem (Odd) Examination Dec-2019  
EC3CO03/EI3CO03 Electronic Devices and Circuits

Programme: B.Tech.

Branch/Specialisation: EC/EI

Duration: 3 Hrs.

Maximum Marks: 60

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.

- Q.1 i. At Room temperature the current in intrinsic semiconductor is due to..... **1**  
(a) Holes (b) Electrons (c) Ions (d) Holes and electrons
- ii. In which of these devices reverse recovery time nearly zero? **1**  
(a) Zener (b) Tunnel (c) Schottky (d) PIN
- iii. A transistor has current gain of 0.99 in CB mode. Its current gain in CC mode ..... **1**  
(a) 100 (b) 99 (c) 1.01 (d) None of these
- iv. In active mode of a Bipolar Junction Transistor the base-collector junction has..... **1**  
(a) Forward resistance (b) Reverse resistance  
(c) Zero bias (d) Zero and forward bias
- v. MOSFET can be used as **1**  
(a) Current controlled capacitor  
(b) Voltage controlled capacitor  
(c) Current controlled inductor  
(d) Voltage controlled inductor
- vi. Saturation region of a JFET is also known as ..... region. **1**  
(a) Pinch-off (b) Analog  
(c) Source (d) Ohmic
- vii. In Cascading Amplifiers, the intermediate stage is... **1**  
(a) CB (b) CC  
(c) CE (d) None of these

P.T.O.

[2]

- viii. In an amplifier, which conducts during the cycle from  $0^\circ$  to  $90^\circ$  and again from  $180^\circ$  to  $270^\circ$ , the amplifier will be termed as... **1**  
 (a) Class A (b) Class B (c) Class C (d) Class AB
- ix. Which of following will not decrease as a result of introduction of negative feedback? **1**  
 (a) Instability (b) Bandwidth  
 (c) Overall gain (d) Distortion
- x. In a Wein bridge Oscillator, the Positive feedback attenuation is **1**  
 (a)  $1/3$  (b)  $1/29$  (c)  $-29$  (d) 3

- Q.2 i. Define mobility and conductivity of charge carrier. **2**  
 ii. What is diode junction capacitance? Calculate dynamic forward and reverse resistance of a PN junction diode. When applied voltage is  $0.25V$  at  $T=27^\circ C$  and  $I_0=2\mu A$ . **3**  
 iii. Explain clipper and clamper circuit? Also determined output waveform of following clipper circuit. If  $v_i$  is a triangular given in Fig. 1 **5**

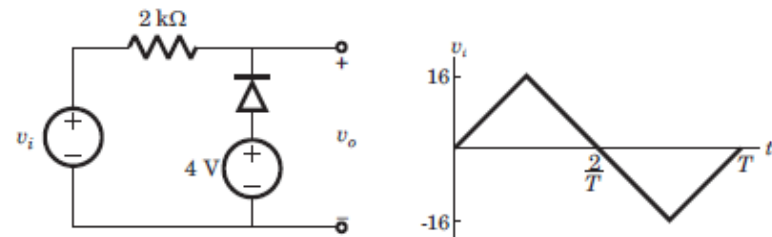


Fig. 1

- OR iv. Explain the following: **5**  
 (a) Tunnel diode and its application  
 (b) Full wave (bridge) rectifier with input and output waveform
- Q.3 i. What is necessity of biasing of Transistor? **2**  
 ii. Explain AC load line with diagram. **3**  
 iii. Describe what is thermal runaway? A base bias circuit in Fig 1, is subjected to an increase in temperature from  $25^\circ C$  to  $75^\circ C$ . If  $\beta = 100$  at  $25^\circ C$  and  $150$  at  $75^\circ C$ , determine the percentage change in Q-point values ( $V_{CE}$  and  $I_C$ ) over this temperature range. Neglect any change in  $V_{BE}$  and the effects of any leakage current. **5**

[3]

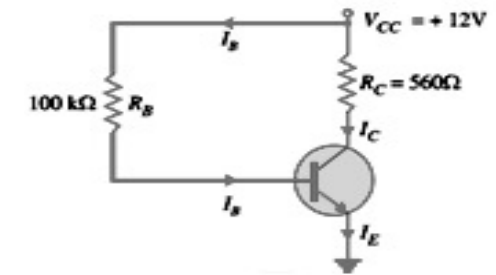


Fig. 1

- OR iv. Draw hybrid-pi model of BJT in CE configuration also discuss, transistor transconductance, input conductance, feedback conductance, base spreading resistance. **5**
- Q.4 i. Compare features of BJT and FET. **2**  
 ii. Explain, how does current flow in N-channel JFET with diagram? **3**  
 iii. What is meant by threshold voltage? Draw and explain drain and transfer characteristics enhancement type MOSFET. **5**
- OR iv. Determine the following for the network of Fig.2 shown. **5**  
 (a)  $V_{GSQ}$  (b)  $I_{DQ}$  (c)  $V_{DS}$  (d)  $V_S$   
 (e)  $V_D$

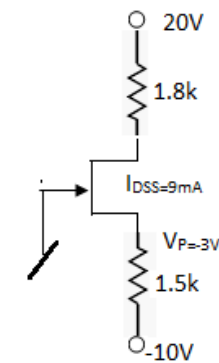


Fig.2

- Q.5 i. Explain the function of coupling capacitor and bypass capacitor. **2**  
 ii. What is small signal amplifier? How are they different from large signal amplifier? **3**

P.T.O.

## Marking Scheme

### EC3CO03/EI3CO03 Electronic Devices and Circuits

Q.1	i.	At Room temperature the current in intrinsic semiconductor is due to..... (d) Holes and electrons	1
	ii.	In which of these devices reverse recovery time nearly zero? (c) Schottky	1
	iii.	A transistor has current gain of 0.99 in CB mode. Its current gain in CC mode ..... (a) 100	1
	iv.	In active mode of a Bipolar Junction Transistor the base-collector junction has..... (b) Reverse resistance	1
	v.	MOSFET can be used as (b) Voltage controlled capacitor	1
	vi.	Saturation region of a JFET is also known as ..... region. (a) Pinch-off	1
	vii.	In Cascading Amplifiers, the intermediate stage is... (c) CE	1
	viii.	In an amplifier, which conducts during the cycle from 0° to 90° and again from 180° to 270°, the amplifier will be termed as... (a) Class A (b) Class B (c) Class C (d) Class AB	1
	ix.	Which of following will not decrease as a result of introduction of negative feedback? (b) Bandwidth	1
	x.	In a Wein bridge Oscillator, the Positive feedback attenuation is (a) 1/3	1
Q.2	i.	Definition of mobility Definition of conductivity of charge carrier	1 mark 1 mark 2
	ii.	Diode junction capacitance Calculate dynamic forward and reverse resistance of a PN junction diode	1 mark 2 marks 3
	iii.	Clipper and clamper circuit Determine output waveform	1 mark 4 marks 5
	OR iv.	Explain the following: (a) Tunnel diode and its application (b) Full wave (bridge) rectifier with input and output waveform	5 2.5 marks 2.5 marks

Q.3	i.	Necessity of biasing of Transistor		2
	ii.	AC load line Diagram	2 marks 1 mark	3
	iii.	Thermal runaway Calculation of $I_B$ and $I_C$ at 25°C Calculation of $I_B$ and $I_C$ at 75°C % change of $I_C$ and $V_{CE}$	1 mark 1 mark 2 marks	5
	OR iv.	Diagram Explanation of all terms 1 mark for each (1 mark * 4)	1 mark 4 marks	5
	Q.4 i.	Compare features of BJT and FET 0.5 mark for each comparison	(0.5 mark * 4)	2
	ii.	Current flow in N-channel JFET Diagram	2 marks 1 mark	3
OR	iii.	Threshold voltage Explanation Diagram	1 mark 2 marks 2 marks	5
	iv.	Determine the following for the network of Fig.2 shown. 1 mark for each calculation	(1 mark * 5)	5
	Q.5 i.	Function of coupling capacitor Function of bypass capacitor	1 mark 1 mark	2
	ii.	Small signal amplifier Difference large signal amplifier	1 mark 2 marks	3
OR	iii.	H-parameter model for CC- amplifier with diagram Derivation of input Derivation of output	2 marks 1.5 marks 1.5 marks	5
	iv.	Diagram and explanation Circuit arrangement Working Diagram	2 marks 1 mark 1 mark 1 mark	5
	Q.6 i.	Transfer gain of an amplifier with (negative) feedback	1 mark	2
		Without (negative) feedback	1 mark	
	ii.	Advantages of negative feedback amplifier 0.5 mark for each (0.5 mark * 2) Calculate the gain of a negative feedback	1 mark 2 marks	3

OR	iii.	Difference b/w positive and negative feedback		<b>5</b>
		0.5 mark for each point (0.5 mark * 2)	1 mark	
		Output impedance of current shunt feedback	2 marks	
		Output impedance of current series feedback	2 marks	
	iv.	Phase shift oscillator using NPN transistor		<b>5</b>
		Circuit arrangement	2 marks	
		Working	2 marks	
		Diagram	1 mark	

\*\*\*\*\*