

Q.5 Attempt any two questions:

- i. Obtain the y parameters for the circuit in figure 12

5

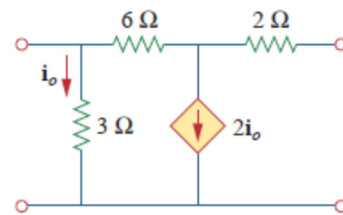


Figure 12

- ii. Derive expression for the h parameter in terms of Z parameter for a two port network. 5
- iii. The ABCD parameters of the two-port network in Figure 13 are 5

$$\begin{bmatrix} 4 & 20 \\ 0.1s & 2 \end{bmatrix}$$

The output port is connected to a variable load for maximum power transfer. Find R_L and the maximum power transferred.

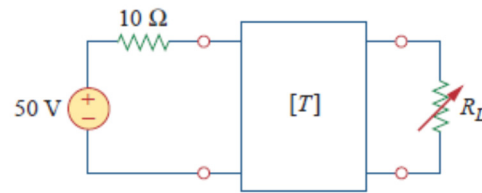


Figure 13

- Q.6 i. What do you mean by positive real function? Write any two properties. 2
- ii. Check the following polynomial is Hurwitz or not. 3

$$P(s) = s^5 + s^4 + 8s^3 + 15s + 8$$

- iii. Find the Foster first form for the driving point impedance function. 5

$$Z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

- OR iv. Synthesise the impedance function and obtain Cauer II realisation: 5

$$Z(s) = \frac{s(s^2 + 3)(s^2 + 5)}{(s^2 + 2)(s^2 + 4)}$$



Programme: B.Tech.

Enrollment No.....

Faculty of Engineering

End Sem (Odd) Examination Dec-2019

EC3CO05 / EI3CO05 Circuit Analysis and Synthesis

Branch/Specialisation: EC / EI

Duration: 3 Hrs.

Maximum Marks: 60

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d.

- Q.1 i. The dependent source in Figure 1 is: 1

- (a) Voltage-controlled current source (b) Voltage-controlled voltage source
(c) Current-controlled voltage source (d) Current-controlled current source

- ii. For the circuit in Figure 2, v_1 and v_2 are related as 1

- (a) $v_1 = 6i + 8 + v_2$ (b) $v_1 = 6i - 8 + v_2$
(c) $v_1 = -6i + 8 + v_2$ (d) $v_1 = -6i - 8 + v_2$

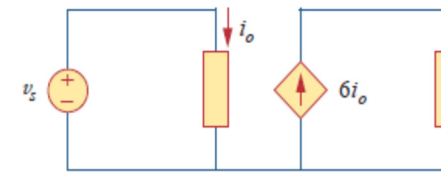


Figure 1

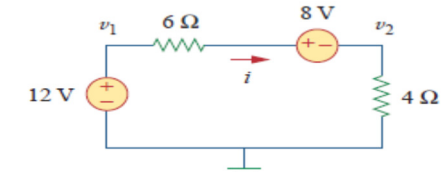


Figure 2

- iii. A load is connected to a network. At the terminals to which the load is connected, $R_{th} = 10 \text{ Ohm}$ and $V_{th} = 40V$. The maximum possible power supplied to the load is: 1

- (a) 160 W (b) 80 W (c) 40 W (d) 1 W

- iv. An RC circuit has $R=2 \text{ Ohm}$ and $C=4F$. The time constant is: 1

- (a) 0.5 S (b) 2 S (c) 4 S (d) 8 S

- v. The current through an RL series circuit with input voltage $v(t)$ is given in the s-domain as: 1

- (a) $V(s) \left[R + \frac{1}{sL} \right]$ (b) $V(s)(R + sL)$ (c) $\frac{V(s)}{R + \frac{1}{sL}}$ (d) $\frac{V(s)}{R + sL}$

- vi. The Laplace transform of $u(t - 2)$ is: 1

- (a) $\frac{1}{s+2}$ (b) $\frac{1}{s-2}$ (c) $\frac{e^{-2s}}{s}$ (d) $\frac{e^{-2s}}{s}$

- vii. What is the condition for reciprocity in terms of h parameters? 1

- (a) $h_{11} = h_{22}$ (b) $h_{12} h_{21} = h_{11} h_{22}$ (c) $h_{12} + h_{21} = 0$ (d) $h_{12} = h_{21}$

- viii. For a symmetrical two port network, 1

- (a) $z_{11} = z_{22}$ (b) $z_{12} = z_{21}$
(c) $z_{11} z_{22} - z_{12}^2 = 0$ (d) $z_{11} = z_{22}$ and $z_{12} = z_{21}$

[2]

- ix. The following property relates to LC impedance or admittance functions: **1**
 (a) The poles and zeros are simple and lie on the $j\omega$ axis.
 (b) There must be either a zero or a pole at origin and infinity.
 (c) The highest (or lowest) power of numerator and denominator differ by unity.
 (d) All of these
- x. The network function $F(s) = \frac{s+2}{(s+1)(s+3)}$ represents an **1**
 (a) RC impedance (b) RL impedance
 (c) RC impedance and RL admittance (d) RC admittance and RL impedance

- Q.2 i. Explain cut sets and tie set. **2**
 ii. Calculate the phasor currents I_1 and I_2 in the circuit of Figure 3 **3**

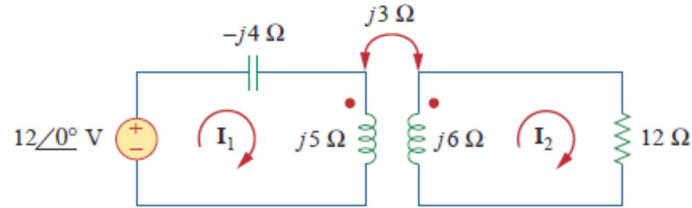


Figure 3

- iii. Use mesh analysis to find the current I_0 in the circuit of Figure 4. **5**
 OR iv. In the circuit of Figure 5 determine the currents i_1 , i_2 , and i_3 **5**

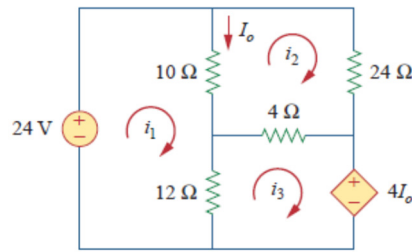


Figure 4

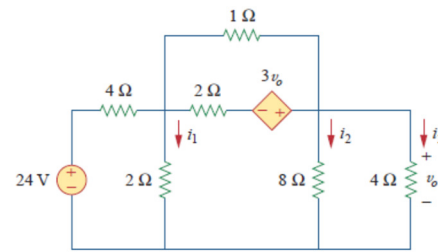


Figure 5

- Q.3 Attempt any two: **5**
 i. Use superposition to find v_x in the circuit of Figure 6 **5**
 ii. The switch in Figure 7 was open for a long time but closed at $t=0$. Determine:
 (a) $i(0^+)$, $v(0^+)$ (b) $\frac{di(0^+)}{dt}$, $\frac{dv(0^+)}{dt}$ (c) $i(\infty)$, $v(\infty)$

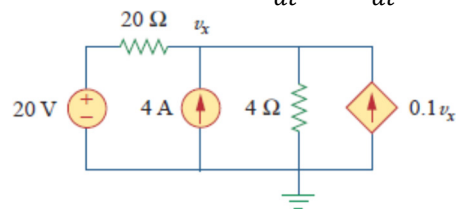


Figure 6

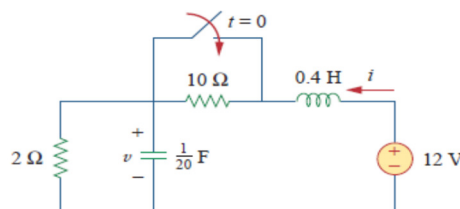


Figure 7

[3]

- iii. The switch in Figure 8 has been in position A for a long time. At $t=0$, the switch moves to B. Determine $v(t)$ for $t>0$ and calculate its value at $t=1$ s and 4 s. **5**

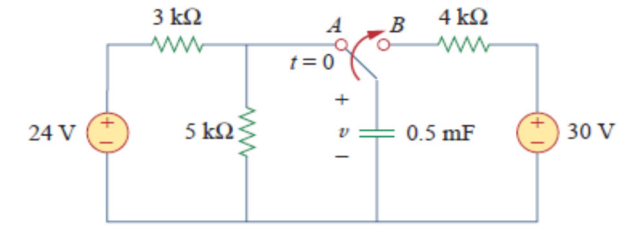


Figure 8

- Q.4 i. Find initial and final value of the function given as: **2**

$$F(s) = \frac{4(s+1)}{s^2+4s+6}$$

 ii. Find the transfer function $H(s) = \frac{I_1(s)}{I_0(s)}$ in the circuit of figure 9. **3**

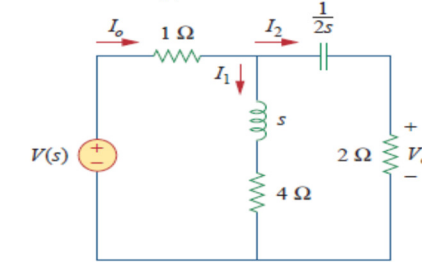


Figure 9

- iii. Find $v_0(t)$ in the circuit of figure 10 using Laplace transform. Assume $v_0(0)=5$ V. **5**

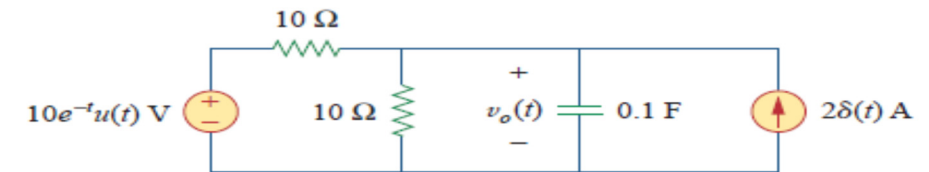


Figure 10

- OR iv. Consider the circuit in figure 11. Find the value of the voltage across the capacitor assuming that the value of $v_s(t) = 10u(t)$ V and assume that at $t=0$, -1A flows through the inductor and +5V is drop across the capacitor. **5**

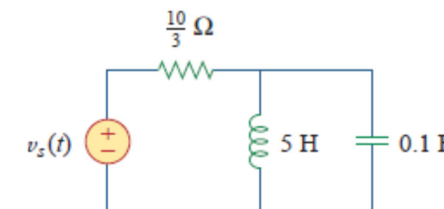


Figure 11

Marking Scheme
EC3CO05 / EI3CO05 Circuit Analysis and Synthesis

Q.1	i.	The dependent source in Figure 1 is:		1
		(d) Current-controlled current source		
	ii.	For the circuit in Figure 2, v_1 and v_2 are related as		1
		(a) $v_1 = 6i + 8 + v_2$		
	iii.	A load is connected to a network. At the terminals to which the load is connected, $R_{th} = 10 \text{ Ohm}$ and $V_{th} = 40V$. The maximum possible power supplied to the load is:		1
		(c) 40 W		
	iv.	An RC circuit has $R=2 \text{ Ohm}$ and $C=4F$. The time constant is:		1
		(d) 8 S		
	v.	The current through an RL series circuit with input voltage $v(t)$ is given in the s -domain as:		1
		(d) $\frac{V(s)}{R+sL}$		
	vi.	The Laplace transform of $u(t - 2)$ is:		1
		(d) $\frac{e^{-2s}}{s}$		
	vii.	What is the condition for reciprocity in terms of h parameters?		1
		(c) $h_{12} + h_{21} = 0$		
	viii.	For a symmetrical two port network,		1
		(a) $Z_{11} = Z_{22}$		
	ix.	The following property relates to LC impedance or admittance functions:		1
		(d) All of these		
	x.	The network function $F(s) = \frac{s+2}{(s+1)(s+3)}$ represents an		1
		(c) RC impedance and RL admittance		
Q.2	i.	Cut sets	1 mark	2
		Tie set	1 mark	
	ii.	Equation	1 mark	3
		Phasor currents I_1 and I_2 1 mark for each (1 mark * 2)	2 marks	
	iii.	Mesh analysis to find the current I_0 in the circuit		5
		Equation	1 mark	
		I_1	1.5 marks	
		I_2	1.5 marks	
		I_0	1 mark	

OR	iv.	In the circuit Determine the currents i_1 , i_2 , and i_3		5
		Equation	2 marks	
		I_1	1 mark	
		I_2	1 mark	
		I_3	1 mark	
Q.3		Attempt any two:		
	i.	Use superposition to find v_x in the circuit of Figure 6		5
		Due to 20V	2 marks	
		Due to 4 A	2 marks	
		Find v_x	1 mark	
	ii.	Determine:		5
		(a) $i(0^+)$, $v(0^+)$	1.5 marks	
		(b) $\frac{di(0^+)}{dt}$, $\frac{dv(0^+)}{dt}$	2 marks	
		(c) $i(\infty)$, $v(\infty)$	1.5 marks	
	iii.	Determine $v(t)$ for $t > 0$	4 marks	5
		Calculate its value at $t = 1 \text{ s}$ and 4 s	1 mark	
Q.4	i.	Find initial	1 mark	2
		Final value of the function	1 mark	
	ii.	Find the transfer function $H(s) = \frac{I_1(s)}{I_0(s)}$ in the circuit		3
	iii.	Find $v_0(t)$ in the circuit of figure 10 using Laplace transform.		5
		5 domain circuit	1 mark	
		For equation	1 mark	
		For $v_0(s)$	1 mark	
		For $v_0(t)$	2 marks	
OR	iv.	Find the value of the voltage		5
		Stepwise marking		
Q.5		Attempt any two questions:		
	i.	Obtain the y parameters for the circuit		5
		Equation	1 mark	
		Y_{11}	1 mark	
		Y_{12}	1 mark	
		Y_{21}	1 mark	
		Y_{22}	1 mark	

	ii.	Derive expression for the h parameter equation Z parameter equation Derivation	1 mark 1 mark 3 marks	5
	iii.	Find R_L and the maximum power transferred. Equation V_{in} R_{in} P_{max}	1 mark 1.5 marks 1.5 marks 1 mark	5
Q.6	i.	Positive real function Any two properties	1 mark 1 mark	2
	ii.	Check the following polynomial is Hurwitz or not. Stepwise marking		3
	iii.	Find the Foster first form for the driving point impedance function. Stepwise marking		5
OR	iv.	Synthesise the impedance function and obtain Cauer II realisation: Stepwise marking		5
