

Enrollment No.....



Faculty of Engineering
End Sem Examination May-2023

OE00003 Industrial Electronics

Programme: B.Tech.

Branch/Specialisation: All

Duration: 3 Hrs.**Maximum Marks: 60**

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d. Assume suitable data if necessary. Notations and symbols have their usual meaning.

- Q.1 i. Which of the following terminals does not belong to the MOSFET? **1**
(a) Drain (b) Gate (c) Base (d) Source
- ii. The dv/dt protection is provided in order to- **1**
(a) Limit the power loss
(b) Reduce the junction temperature
(c) Avoid accidental turn-on of the device
(d) Avoiding sudden large voltage across the load
- iii. The device that exhibits negative resistance region is: **1**
(a) Diac (b) Triac (c) Transistor (d) UJT
- iv. In the process of diode-based rectification, the alternating input voltage is converted into- **1**
(a) An uncontrolled alternating output voltage
(b) An uncontrolled direct output voltage
(c) A controlled alternating output voltage
(d) A controlled direct output voltage
- v. Choppers converts- **1**
(a) AC to DC (b) DC to AC
(c) DC to DC (d) AC to AC
- vi. A type D chopper is a- **1**
(a) Two quadrant type-B chopper
(b) Two quadrant type-A chopper
(c) Two quadrant type-C chopper
(d) None of these

[2]

- vii. In a single-phase half wave inverter how many SCR(s) are/is gated at a time- **1**
 (a) One (b) Two (c) Three (d) none of these
- viii. Inverters converts- **1**
 (a) DC power to DC power (b) DC power to AC power
 (c) AC power to AC power (d) AC power to DC power
- ix. A single-phase half wave voltage controller consists of- **1**
 (a) One SCR is parallel with one diode
 (b) One SCR is anti-parallel with one diode
 (c) Two SCRs in parallel
 (d) Two SCRs in anti-parallel
- x. The single-phase mid-point type cyclo-converter uses _____ number of SCRs. **1**
 (a) 4 (b) 8 (c) 6 (d) None of these
- Q.2 i. Draw the two-transistor analogue of a thyristor. **2**
 ii. What is latching current and holding current for a thyristor? **3**
 iii. Explain the construction and working of a thyristor. Also draw the static VI characteristics of SCR. **5**
- OR iv. Explain the term Delay time, Rise time and Spread time for an SCR. **5**
- Q.3 Attempt any two:
 i. What do you mean by commutation of SCR? Explain Class C and Class D Commutation method of SCR. **5**
 ii. Explain the construction and working of UJT along with its VI characteristics and its applications. **5**
 iii. Explain the working of a single-phase dual convertor with suitable circuit diagram and waveforms. **5**
- Q.4 i. What is chopping period and duty cycle in a chopper? Enlist the various control strategies for varying duty cycle in a chopper. **2**
 ii. Draw and explain the working of Class B chopper with suitable waveforms. **3**
 iii. A DC chopper circuit connected to a 100 V DC source supplies an inductive load having 40mH in series with a resistance of 5 Ω . A freewheeling diode is placed across the load. The load current varies between the limits of 10 A and 12 A. Determine the time ratio of a chopper. **5**

[3]

- OR iv. Explain the construction and working principle of Buck Boost convertor along with its advantages and its application. **5**
- Q.5 Attempt any two:
 i. Draw and explain the working of auxiliary commutated single-phase bridge inverter along with its voltage and current waveforms. **5**
 ii. How PWM control method can be used to control the output voltage of an inverter? List different PWM techniques used in single phase inverter. **5**
 iii. Compare CSI and VSI. Enlist their various industrial applications. **5**
- Q.6 Attempt any two:
 i. What is cyclo-converter? Describe the working of bridge type configuration of single phase to single phase cyclo-converter. **5**
 ii. What is AC voltage controller? Discuss its industrial application along with its merits and demerits. **5**
 iii. Explain working of single-phase full wave AC voltage controller with RL load along with waveforms. **5**

Marking Scheme

OE00003 Industrial Electronics

Q1.

- | | |
|---|---|
| 1. Which of the following terminals does not belong to the MOSFET?
c) Base | 1 |
| 2. The dv/dt protection is provided in order to
c) avoid accidental turn-on of the device | 1 |
| 3. The device that exhibits negative resistance region is:
a) UJT | 1 |
| 4. In the process of diode based rectification, the alternating input voltage is converted into
b) an uncontrolled direct output voltage | 1 |
| 5. Choppers converts
c) DC to DC | 1 |
| 6. A type D chopper is a
a) two quadrant type-B chopper | 1 |
| 7. In a single-phase half wave inverter how many SCR(s) are/is gated at a time
a) one | 1 |
| 8. Inverters converts
b) dc power to ac power | 1 |
| 9. A single-phase half wave voltage controller consists of
b) one SCR is anti parallel with one diode | 1 |

- | | |
|---|---|
| 10. The single phase mid-point type cycloconverter uses _____ number of SCRs. | 1 |
| a) 4 | |

Q2

- | | |
|--|-----|
| a. Draw the two transistor analogue of a thyristor. | 2 |
| b. What is latching current and holding current for a thyristor. | 3 |
| Latching Current | 1.5 |
| holding current | 1.5 |

- | | |
|--|---|
| c. Explain the construction and working of a thyristor. Also draw the static VI characteristics of SCR | 5 |
|--|---|

Construction	1
Working	2
Characteristics	2

OR

- | | |
|---|---|
| d. Explain the term Delay time, Rise time and Spread time for an SCR. | 5 |
| Delay time | 1 |
| Rise time | 2 |
| Spread time | 2 |

Q3.

- | | |
|---|---|
| a. What do you mean by commutation of SCR? Explain Class C and Class D Commutation method of SCR. | 5 |
|---|---|

Commutation of SCR	1
Class C Method	2
Class D Method	2

- | | |
|--|---|
| b. Explain the construction and working of UJT along with its VI characteristics and its applications. | 5 |
|--|---|

Construction	1
Working of UJT	1
VI characteristics	2

Applications. 1

- c. Explain the working of a single phase dual convertor with suitable circuit diagram and waveforms. 5

Working 2

Circuit diagram 2

Waveforms 1

Q4

- a. What is chopping period and duty cycle in a chopper? Enlist the various control strategies for varying duty cycle in a chopper. 2

Chopping period .5

Duty cycle .5

List of various control strategies 1 2

- b. Draw and explain the working of Class B chopper with suitable waveforms. 3

Construction 1

Working 1

Waveform 1

A dc chopper circuit connected to a 100 V DC source supplies an inductive load having 40mH in series with a resistance of 5 Ω . A freewheeling diode is placed across the load. The load current varies between the limits of 10 A and 12 A. Determine the time ratio of a chopper. 5

OR

- c. Discuss the construction and working principle of Buck Boost convertor along with its advantages and its application 5

Construction 2

Working principle 2

Advantages and its application 1

Q5

- a. Draw and explain the working of auxiliary commutated single phase bridge inverter along with its voltage and current waveforms. 5

Construction 2

Working 2

Waveform 1

- b. How PWM control method can be used to control the output voltage of an inverter. List different PWM techniques used in single phase inverter. 5

Explanation 3

List of PWM techniques 2

- c. Compare CSI and VSI. Enlist their various industrial applications. 5

CSI 2

VSI 2

Application 1

Q6

- a. What is cycloconverter? Describe the working of bridge type configuration of single phase to single phase cycloconverter. 5

Explanation 2

Working of bridge type configuration of single phase to single phase cycloconverter. 3

- b. What is AC voltage controller? Discuss its industrial application along with its merits and demerits. 5

AC voltage controller 3

Its industrial application 1

Its merits and demerits. 1

- c. Explain working of single phase full wave ac voltage controller with RL load along with waveforms. 5

Working 3

Waveforms 2.
