

Enrollment No.....



Faculty of Engineering
End Sem Examination Dec 2024

EN3ES11 Principles of Electrical Engineering

Programme: B.Tech.

Branch/Specialisation: CSBS


Duration: 3 Hrs.**Maximum Marks: 60**

Note: All questions are compulsory. Internal choices, if any, are indicated. Answers of Q.1 (MCQs) should be written in full instead of only a, b, c or d. Assume suitable data if necessary. Notations and symbols have their usual meaning.

		Marks	BL	PO	CO	PSO
Q.1	i. Which of the following correctly describes an ideal voltage source?	1	01	01-02	01	
	(a) It has infinite internal resistance					
	(b) It provides a constant current across the load					
	(c) It has zero internal resistance					
	(d) It varies voltage with current changes					
	ii. In a circuit with a 12 V battery and three series connected resistors of 3 Ω , 4 Ω , and 5 Ω , the total power consumed will be-	1	01	01-02	01	
	(a) 2 W					
	(b) 4 W					
	(c) 8 W					
	(d) 12 W					
	iii. Norton's Theorem states that any linear two-terminal network can be represented by:	1	02	01	02	
	(a) A voltage source and series resistor					
	(b) A current source and parallel resistor					
	(c) A dependent source and resistor					
	(d) A voltage source and parallel resistor					
	iv. The Superposition Theorem applies to circuits which are-	1	02	01	02	
	(a) Linear and bilateral					
	(b) Nonlinear and unilateral					
	(c) Only resistive					
	(d) Only capacitive					

[2]

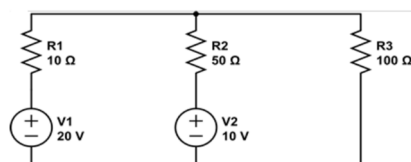- v. The peak factor for a sinusoidal AC waveform is: **1** 01 01, 03, 06
(a) 1.11 (b) 1.414 (c) 1.732 (d) 2.0
- vi. In AC circuits, the power factor is defined as the ratio of: **1** 01 01, 03, 06
(a) Apparent power to active power
(b) Active power to reactive power
(c) Active power to apparent power
(d) Reactive power to apparent power
- vii. When a dielectric material is placed between the plates of a capacitor, the capacitance: **1** 02 01, 07 04
(a) Decreases (b) Increases
(c) Remains the same (d) Becomes zero
- viii. The magnetic flux of magnetic circuit is analogous to _____ of electric circuit. **1** 02 01 05
(a) Voltage (b) Inductance
(c) Resistance (d) Current
- ix. A thermocouple is used to measure: **1** 02 01, 07 04
(a) Pressure (b) Temperature
(c) Voltage (d) Humidity
- x. Which of the following earthing is used in residential buildings? **1** 02 01 05
(a) Plate earthing (b) Chemical earthing
(c) Strip earthing (d) Both (a) and (b)
- Q.2 i. State Kirchhoff's Current Law (KCL) and Kirchhoff's Voltage Law (KVL). **2** 02 01-02 01
ii. Define passive and active circuit elements. Give examples of each. **3** 01 01-02 01
iii. Find the current through each branch using mesh analysis method- **5** 03 01 02



- OR iv. Explain all types of dependent and independent sources with their symbol. **5** 02 01-02 01

[3]

- Q.3 i. Write down the statement of Superposition theorem. **2** 01 01 02
ii. State and prove the maximum power transfer theorem with a suitable example. **8** 02 01 02
OR iii. Derive the formula for Δ to Y and Y to Δ transformation. **8** 02 01 02
- Q.4 i. Define the following terms: **4** 02 01, 03, 06
(a) Active power (b) Reactive power
(c) Apparent power (d) Power factor
ii. Draw & explain the voltage triangle, impedance triangle and power triangle of an R – L A.C. circuit. **6** 03 01, 03, 06
OR iii. Drive the relation between line and phase quantity of a three-phase delta-connected balanced load system. **6** 03 01, 03, 06
- Q.5 i. What are composite capacitors? How do they differ from regular capacitors? **3** 02 01, 07 04
ii. Explain the working principle of a single-phase transformer and derive its EMF equation. **7** 03 01, 07 04
OR iii. State Faraday's law of electromagnetic induction. Also discuss self and mutual inductance. **7** 03 01, 07 04
- Q.6 Attempt any two:
i. Write short note on piezoelectric and thermo-couple transducers. **5** 03 01 05
ii. Explain different types of wiring systems. **5** 03 01 05
iii. Explain the types of earthing. Why earthing is necessary? **5** 03 01 05

Marking Scheme EN3ES11 (T) Principles of Electrical Engineering (T)			
Q.1	i)	(c) It has zero internal resistance	1
	ii)	(d) 12 W	1
	iii)	(b) A current source and parallel resistor	1
	iv)	(a) Linear and bilateral	1
	v)	(b) 1.414	1
	vi)	(c) Active power to apparent power	1
	vii)	(b) Increases	1
	viii)	(d) Current	1
	ix)	(b) Temperature	1
	x)	(d) Both (A) and (B)	1
Q.2	i.	State Kirchhoff's Current Law (KCL) and Kirchhoff's Voltage Law (KVL). Each Law statement (1*2)	2 -2 marks
	ii.	Define passive and active circuit elements. Give examples of each. Each definition (1.5*2)	3 -2 marks
	iii.	Find the current through each branch using mesh analysis.	5
		Equation of each mash 1 mark (1 mark *2)	-2 mark
		Current in R ₁ branch = 0.3076 A	-1 mark
		Current in R ₂ branch = 0.1384 A	-1 mark
		Current in R ₃ branch = 0.1692 A	-1 mark
	OR iv.	Explain all types of dependent and independent sources with their symbol. Independent sources with symbol Dependent sources with symbol	5 -2 mark -3 mark

Q.3	i.	Write the statement of the Superposition theorem.	2
		Statement	-2 mark
	ii.	State and prove the Maximum power transfer theorem with a suitable example for a DC circuit.	8
		Statement	-2 mark
		Proof with suitable example	-6 mark
	OR iii.	Explain star-to-delta and delta to star transformation.	8
Q.4		Star to delta	-4 mark
		Delta to star	-4 mark
	i.	Define the following terms: Each Definition is one mark	4 -4 mark
	ii.	Explain the RMS value and maximum value in sinusoidal voltage. How RMS value 0.707 times to maximum value.	6
		Definition of RMS value and maximum value	-4 mark
		Derivation of RMS value to maximum value	-2 mark
	OR iii.	Drive the relation between line and phase quantity of a three-phase delta-connected balanced load system.	6
		Diagram for star and delta connection (1 mark *2)	-2 marks
		relation for delta connected system	-4 marks
	Q.5 i.	What are composite capacitors, and how do they differ from regular capacitors?	3
Q.5		Definition of composite capacitor	-2 mark
		Difference	-1 mark
	ii.	Explain the working principle of a single-phase transformer and derive its EMF equation.	7
		Principle of single phase transformer	-4 mark
		Emf equation	-3 mark
	OR iii.	State Faraday's law of electromagnetic induction. And discuss self and mutual inductance.	7
		Statement of Faraday's law	-2 mark
		Self and mutual inductance	-5 mark
	Q.6	Attempt any two:	

[2]

- | | | |
|------|--|-----------|
| i. | Piezoelectric and thermo-couple transducers | 5 |
| | Piezoelectric transducers | -2.5 mark |
| | Thermo-couple transducers | -2.5 mark |
| ii. | Explain different types of wiring systems. | 5 |
| | Name of different types of wiring system | -2 marks |
| | Explanation of all | -3 marks |
| iii. | Explain types of earthing and why it is necessary. | 5 |
| | types of earthing | -3 marks |
| | Why it is necessary | -2 marks |

[3]