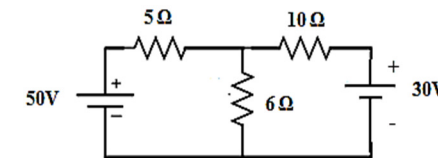


| | | | | | | |
|-------|---|-------------------|----------|-------|----------|----|
| | (c) Power factor | (d) None of these | | | | |
| v. | The co-efficient of coupling between two isolated coils is- | | 1 | 01 | 01 | 01 |
| | (a) 1 | (b) 0.5 | (c) 0.75 | (d) 0 | | |
| vi. | Permeability in a magnetic circuit corresponds to _____ in an electric circuit. | | 1 | 01 | 01 | 01 |
| | (a) Resistance | (b) Resistivity | | | | |
| | (c) Conductivity | (d) Conductance | | | | |
| vii. | The primary winding of a transformer has a 120V AC supply. What is the value of secondary voltage if the transformation ratio is 1.5? | | 1 | 03 | 01 02 | 04 |
| | (a) 120V | (b) 80V | | | | |
| | (c) 180V | (d) 220V | | | | |
| viii. | Which of the following part is used in construction of DC machine but not in AC machine? | | 1 | 01 | 01 | 01 |
| | (a) Armature winding | (b) Field winding | | | | |
| | (c) Commutator | (d) Shaft | | | | |
| ix. | Which of the following is not a component of thermal power plant? | | 1 | 01 | 01 | 01 |
| | (a) Condenser | (b) Cooling tower | | | | |
| | (c) Turbine | (d) Fuel tank | | | | |
| x. | Calculate the number of units of electricity used if a bulb of 1000W is kept on for 5 hours. | | 1 | 03 | 01 02 | 04 |
| | (a) 1 unit | (b) 0.1 unit | | | | |
| | (c) 5 unit | (d) 0.5 unit | | | | |

| | | | | | | |
|-----|------|--|---|----|----------|----|
| Q.2 | i. | Write down the statement of Ohm's law and using ohm's law solve the following: If the current flowing through a 4Ω resistor is 2A, what will be the voltage across the given resistor? | 2 | 03 | 01 02 | 04 |
| | ii. | Differentiate between the followings: (a) Ideal and practical sources (b) Active and passive elements | 3 | 02 | 01 02 | 01 |
| | iii. | Find out the equivalent resistance between terminals a & b of the following network using star-delta transformation: | 5 | 03 | 01 02 | 04 |

OR iv. Find the current through 6Ω resistor of the network shown below using nodal analysis method.



| | | | | | | |
|-----|------|---|----------|----|----|----|
| Q.3 | i. | Define the following terms related to AC: | 2 | 01 | 01 | 01 |
| | | (a) R.M.S Value | | | | |
| | | (b) Average value | | | | |
| | | (c) Form Factor | | | | |
| | | (d) Peak Factor | | | | |
| | ii. | For an A.C single phase R- L- C circuit: | 8 | 03 | 01 | 04 |
| | | (a) Draw the Voltage triangle, Impedance triangle & Power triangle. | | | 02 | |
| | | (b) Find the power factor of the circuit, if resistance (R) is 5Ω , Inductive reactance (X_L) is 15Ω and Capacitive reactance (X_C) is 10Ω . | | | | |
| OR | iii. | For a 3-phase star connected supply system: | 8 | 02 | | 02 |
| | | (a) Draw the circuit diagram and phasor diagram. | | | 01 | |
| | | (b) With the help of phasor diagram, deduce the relation between line quantities and phase quantities. | | | | |

Q.4 i. Two coils, A of 12,500 turns and B of 16,000 turns, lie in parallel plane so that 60% of flux produced in A links coil B. It is found that a current of 5A in A produces a flux of 0.6mWb while the same current in B produces 0.8mWb. Determine (a) Mutual inductance
(b) Co-efficient of coupling

Scheme of Marking

Basic Electrical Engineering (T) - EN3ES17 (T)

| | | | |
|-----|-------|---|---|
| Q.1 | i) | (b) An independent voltage source in series with the equivalent resistance | 1 |
| | ii) | (d) Current dependent voltage source | 1 |
| | iii) | (c) Power Factor | 1 |
| | iv) | (d) 220V, 50Hz | 1 |
| | v) | (d) 0 | 1 |
| | vi) | (c) Conductivity | 1 |
| | vii) | (c) 180V | 1 |
| | viii) | (c) Commutator | 1 |
| | ix) | (d) Fuel tank | 1 |
| | x) | (c) 5 unit | 1 |
| Q.2 | i. | Statement (1 Mark), Voltage = 8V (1 Mark) | 2 |
| | ii. | (a) First difference (1mark) + second difference (0.5 mark) | 3 |
| | | (b) First difference (1mark) + second difference (0.5 mark) | |
| | iii. | Transformation formula (1 mark), solution- (3.5 marks), Equivalent resistance answer- (0.5mark) | 5 |
| OR | iv. | KCL equation- 2 marks, determination of node potential-2 marks, Calculation of branch current-1 mark | 5 |
| Q.3 | i. | Each definition- 0.5 mark | 2 |
| | ii. | Voltage triangle- 2marks, Impedance triangle- 2marks, Power triangle- 2 marks, Power factor calculation- 2marks | 8 |
| OR | iii. | Circuit diagram-2 mark, Phasor diagram-3marks, Deduce the relationship -3marks | 8 |

| | | | |
|-----|------|---|---|
| Q.4 | i. | Mutual inductance calculation- 1 mark, Co-efficient of Coupling calculation – 1 mark Self-Inductance Value – 1 mark | 3 |
| | ii. | Each definition – 1 mark | 7 |
| OR | iii. | B-H curve explanation- 2 marks, Hysteresis loop explanation- 3.5 marks, residual magnetism, magnetic saturation, coercive force each 0.5 mark 0.5 mark * 3 – 1.5 marks | 7 |
| Q.5 | i. | Circuit diagram- 1mark, principle-1 mark, explanation- 2marks | 4 |
| | ii. | Sketch- 2marks, explanation- 4 marks | 6 |
| OR | iii. | Sketch- 2marks, explanation- 4 marks | 6 |
| Q.6 | | | |
| | i. | Single line diagram- 3marks, explanation- 2marks | 5 |
| | ii. | Block diagram-3marks, Function of components- 2marks | 5 |
| | iii. | KWH for three loads -3marks, total units for 31days-01 mark, electric bill-01 mark | 5 |

Solution


BEE

EN3ES17


Q.2 (i) $R = 4\Omega$, $I = 2A$.

$$V = IR = 2 \times 4 = \boxed{8V}$$

(iii)

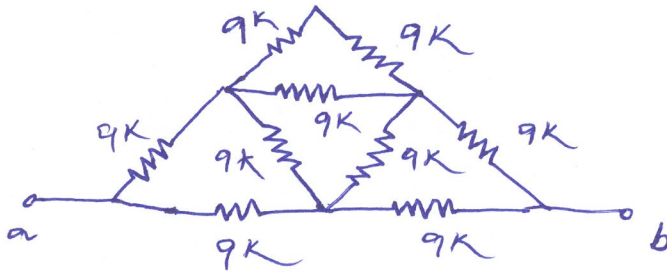


\Rightarrow $9K$ series with $9K$.

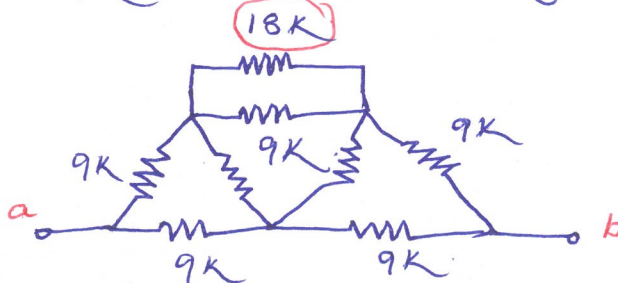

\Rightarrow $18K$ & $9K$ are in parallel
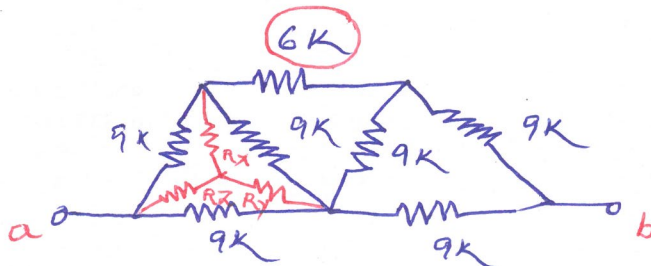
$$R_{eq} = \frac{18 \times 9}{18 + 9} = 6K\Omega$$




\Rightarrow Applying Δ -Y transformation

$$R_X = \frac{9 \times 9}{27} = 3K\Omega$$

$$R_Y = \frac{9 \times 9}{27} = 3K\Omega$$

$$R_Z = \frac{9 \times 9}{27} = 3K\Omega$$


\Rightarrow

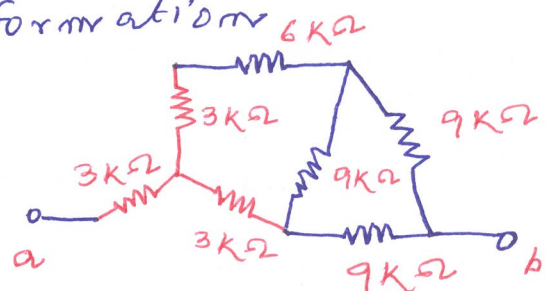

\Rightarrow $6K$ & $3K$ are in series.



Diagram 1: A circuit with a 3K resistor in series with a parallel combination of 12K and 6K resistors, followed by another 3K resistor. The terminals are labeled 'a' and 'b'.
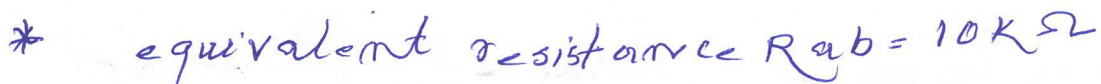
$$R_{eq} = \frac{12 \times 6}{12 + 6} = 4 \text{ K}\Omega$$


(iv)

The circuit diagram consists of a top horizontal wire and a bottom horizontal wire. On the left, a 50V DC source is connected between the top and bottom wires. On the right, a 30V DC source is connected between the top and bottom wires. Between these two sources, there is a central vertical branch. The top of this branch is connected to the top wire through a 5Ω resistor, with current I_1 indicated by a red arrow pointing right. This is followed by a node labeled with a circled 1 and the text 'OR'. From this node, a 6Ω resistor is connected vertically to the bottom wire, with current I_3 indicated by a red arrow pointing down. Also from this node, a 10Ω resistor is connected to the right wire, with current I_2 indicated by a red arrow pointing left.

At node-1, applying KCL

$$I_1 + I_2 = I_3 \quad \dots \quad (1)$$

$$\Rightarrow \frac{50 - V_1}{5} + \frac{30 - V_1}{10} = \frac{V_1}{6}$$

$$\Rightarrow \frac{100 - 2V_1 + 30 - V_1}{10} = \frac{V_1}{6} \Rightarrow \frac{130 - 3V_1}{10} = \frac{V_1}{6}$$

$$\Rightarrow 780 - 18V_1 = 10V_1 \Rightarrow 28V_1 = 780 \Rightarrow V_1 = \frac{780}{28} = \boxed{27.857}$$

Now current through 6Ω resistor

$$I_3 = \frac{V_1}{6} = \frac{27.857}{6} = \boxed{4.642 \text{ A}}$$

Q.3 (ii) (b) $R = 5\Omega$, $X_L = 15\Omega$, $X_C = 10\Omega$

$$\therefore Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{5^2 + (15 - 10)^2} \\ = \sqrt{25 + 25} = \sqrt{50} = 7.071\Omega$$

$$\therefore \text{power factor } \cos\phi = \frac{R}{Z} = \frac{5}{7.071} = \boxed{0.707 \text{ (lag)}}$$

Q.4 (c)

$$\begin{matrix} \text{A} & \text{B} \\ N_1 = 12,500 & N_2 = 16,000 \end{matrix}$$

$$L_1 = \frac{N_1 \phi_1}{I_1} = \frac{12,500 \times 0.6 \times 10^{-3}}{5} \text{ H} \\ = 7.5 \text{ H} = \boxed{1.5 \text{ H}}$$

$$L_2 = \frac{N_2 \phi_2}{I_1} = \frac{16,000 \times 0.8 \times 10^{-3}}{5} = \boxed{2.56 \text{ H}}$$

$$M = \frac{N_2 \times 60\% \text{ of } \phi_1}{I_1} = \frac{16,000 \times \frac{60}{100} \times 0.6 \times 10^{-3}}{5} \\ = \boxed{1.152 \text{ H}}$$

co-efficient of coupling

$$K = \frac{M}{\sqrt{L_1 L_2}} = \frac{1.152}{\sqrt{1.5 \times 2.56}} = \boxed{0.5878}$$

Q.6 (iii) (a) 3 bulbs, 30W, 5 hours

Total energy consumed per day

$$= \frac{3 \times 30}{1000} \times 5 \text{ KWH} = \boxed{0.45 \text{ KWH}}$$

(b) 4 tube lights, 50W, 8 hr

Total energy consumed / day

$$= \frac{4 \times 50}{1000} \times 8 = \boxed{1.6 \text{ KWH}}$$

(c) 1 Fridge, 300W, 24 hr

Total energy consumed / day

$$= \frac{1 \times 300}{1000} \times 24 = \boxed{7.2 \text{ KWH}}$$

Total energy consumed for all loads per day = $(0.45 + 1.6 + 7.2) = \boxed{9.25 \text{ KWH}}$

For 31 days total energy consumed

$$= 31 \times 9.25 = 286.75 \text{ KWH} = \boxed{286.75 \text{ units}}$$

$$\text{Electric bill} = 2 \times 286.75 = \boxed{\text{Rs } 573.5}$$